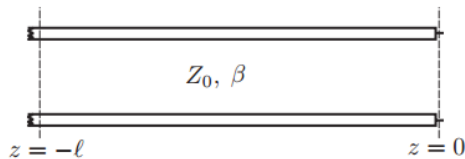


# Today's Plan (9/20/2017)

- S-parameter Review
- S-parameter Calculation (Examples)
- Why S-parameter?
- Matching Network Design on Smith Chart
- Hints on hw3.4

# S-Parameter Basics

In phasor domain (ac analysis)



Recall what can exist on a cable

$$v(z) = V^+ e^{-\gamma z} + V^- e^{\gamma z}$$


$$i(z) = \frac{V^+}{Z_0} e^{-\gamma z} - \frac{V^-}{Z_0} e^{\gamma z}$$

$$\gamma = j\beta = j2\pi/\lambda$$

$$\begin{pmatrix} \frac{V_1^-}{\sqrt{Z_1}} \\ \frac{V_2^-}{\sqrt{Z_2}} \\ \frac{V_3^-}{\sqrt{Z_3}} \end{pmatrix} = \begin{pmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{pmatrix} \begin{pmatrix} \frac{V_1^+}{\sqrt{Z_1}} \\ \frac{V_2^+}{\sqrt{Z_2}} \\ \frac{V_3^+}{\sqrt{Z_3}} \end{pmatrix}$$

Backward Terms


Forward Terms

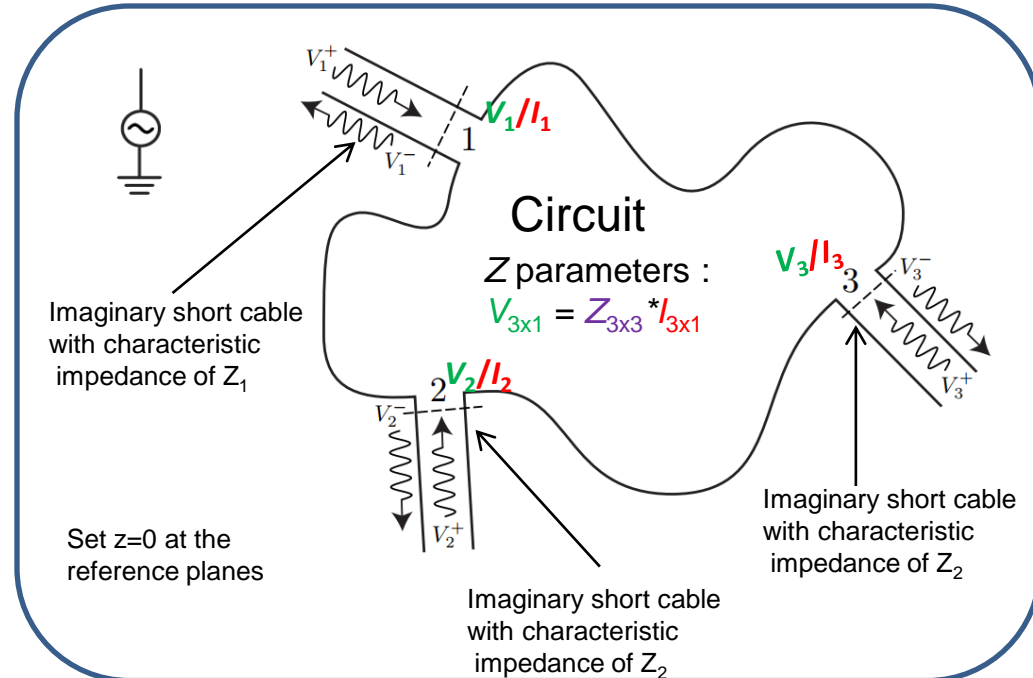

- S parameters:  $[V_i^-/(Z_i^{0.5})]_{3 \times 1} = S_{3 \times 3} * [V_i^+/(Z_i^{0.5})]_{3 \times 1}$
- $V_i = V_i^+ + V_i^-$  ;  $I_i = V_i^+/Z_i - V_i^-/Z_i$   
 $\Rightarrow V_i^+ = (V_i + I_i Z_i)/2$  ;  $V_i^- = (V_i - I_i Z_i)/2$   
 $\Rightarrow V_i^+/(Z_i^{0.5}) = [V_i/(Z_i^{0.5}) + I_i(Z_i^{0.5})]/2$  ;  $V_i^-/(Z_i^{0.5}) = [V_i/(Z_i^{0.5}) - I_i(Z_i^{0.5})]/2$   
 $\Rightarrow S_{3 \times 3} = (Z_{3 \times 3} - [Z_i]_{3 \times 3})(Z_{3 \times 3} + [Z_i]_{3 \times 3})^{-1}$
- **S parameters depend on the used reference impedance**


# Simple One-Port Example

What is the S-parameter of a capacitor **under reference impedance of  $Z_0$**  ?

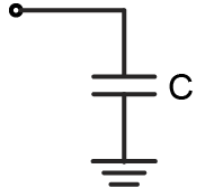

Method 1:

From definition

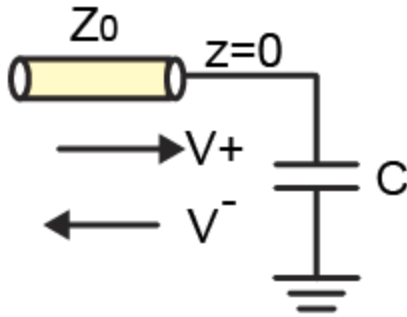

$$V^+ + V^- = (V^+/Z_0 - V^-/Z_0) * (1/j\omega C)$$

$$\Rightarrow S_{11} = V^-/V^+ = [(j\omega C)^{-1} - Z_0] / [(j\omega C)^{-1} + Z_0]$$

One port  $S_{11} = (Z_L - Z_0) / (Z_L + Z_0)$  depends on the selected  $Z_0$

$$v(z) = V^+ e^{-\gamma z} + V^- e^{\gamma z}$$

$$i(z) = \frac{V^+}{Z_0} e^{-\gamma z} - \frac{V^-}{Z_0} e^{\gamma z}$$

Note: if  $z = a \neq 0$ ,

use  $\frac{V^+ e^{-\gamma a}}{Z_0}$  as the new  $V^+$  and  $\frac{V^- e^{\gamma a}}{Z_0}$  as the new  $V^-$   
the calculated  $S_{11}$  does not change

Method 2:

Converted from Z-parameter



$$\mathbf{S}_{3 \times 3} = (\mathbf{Z}_{3 \times 3} - [\mathbf{Z}_i]_{3 \times 3})(\mathbf{Z}_{3 \times 3} + [\mathbf{Z}_i]_{3 \times 3})^{-1}$$

$$S_{1 \times 1} = (Z_{1 \times 1} - [Z_i]_{1 \times 1})(Z_{1 \times 1} + [Z_i]_{1 \times 1})^{-1} = (Z_{in} - Z_0) / (Z_{in} + Z_0)$$

# Simple Two-Port Example

What is the S-parameter of a series resistor  
under reference impedance of  $Z_0$  ?


Method 1:  
From definition

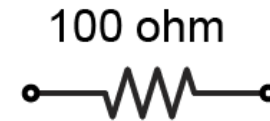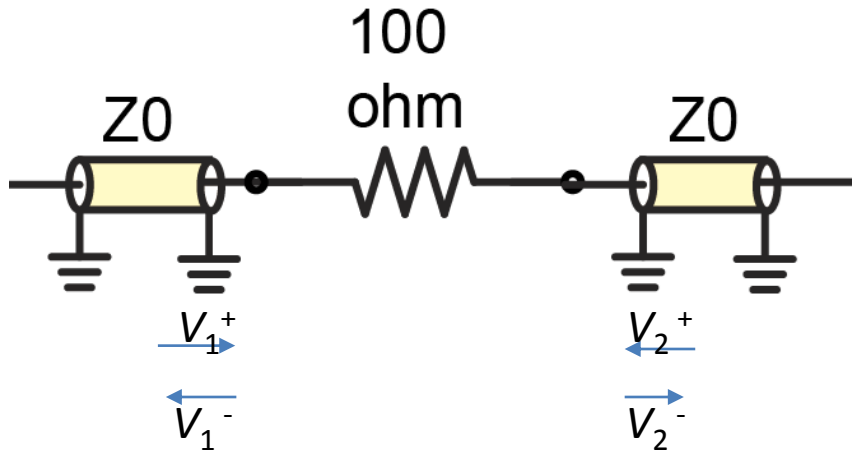

$$\begin{pmatrix} V_1^- \\ V_2^- \end{pmatrix} = \begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} \begin{pmatrix} V_1^+ \\ V_2^+ \end{pmatrix}$$

$$S_{11} = V_1^- / V_1^+ \text{ if } V_2^+ = 0$$
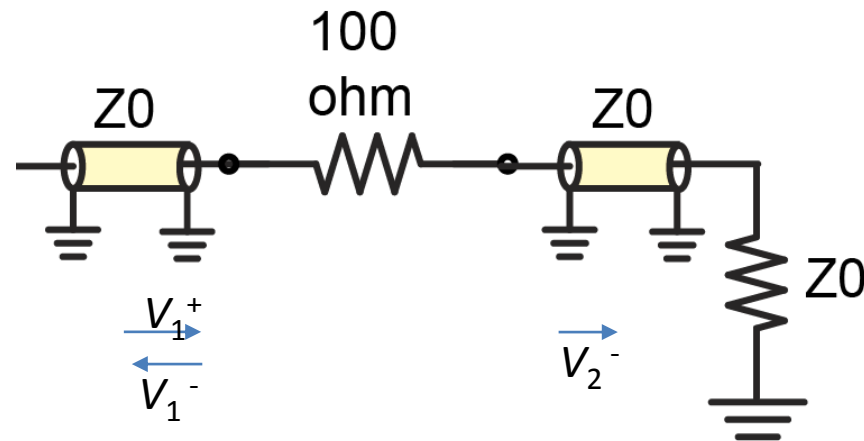
$$S_{21} = V_2^- / V_1^+ \text{ if } V_2^+ = 0$$



$$(V_1^+ + V_1^-) - 100(V_1^+ / Z_0 - V_1^- / Z_0) = V_2^-$$

$$(V_1^+ / Z_0 - V_1^- / Z_0) = V_2^- / Z_0$$

$$(2 \text{ eqs, } 3 \text{ variables}) \Rightarrow S_{11} = 50 / (Z_0 + 50); S_{21} = Z_0 / (Z_0 + 50)$$

$S_{11}$  can be calculated rapidly by seeing  $Z_L = 100 + Z_0$


# Simple Two-Port Example

Method 2:

Converted from Z-parameter


$$S = (Z - [Z_i])(Z + [Z_i])^{-1}$$

100 ohm


$$Z = \begin{pmatrix} \infty & \infty \\ \infty & \infty \end{pmatrix} \quad Z_i = \begin{pmatrix} Z_0 & 0 \\ 0 & Z_0 \end{pmatrix}$$

$$S = ([Y_i] - Y) * ([Y_i] + Y)^{-1}$$


100 ohm


$$Y = \begin{pmatrix} 0.01 & -0.01 \\ -0.01 & 0.01 \end{pmatrix}$$
$$Y_i = \begin{pmatrix} 1/Z_0 & 0 \\ 0 & 1/Z_0 \end{pmatrix}$$

$$\Rightarrow S_{11} = 50/(Z_0 + 50); S_{21} = Z_0/(Z_0 + 50)$$

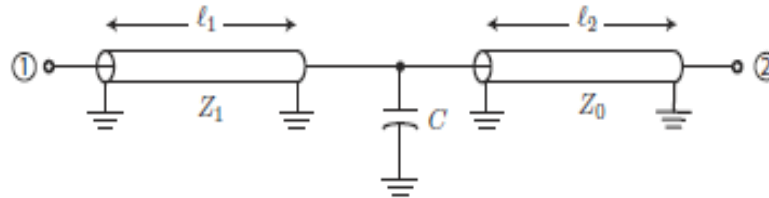
# Midterm-Level Two-Port Example

What is the S-parameter of the below two-port circuit  
under reference impedance of  $Z_0$ ?



$$S_{11} = V_1^- / V_1^+ \text{ if } V_2^+ = 0$$
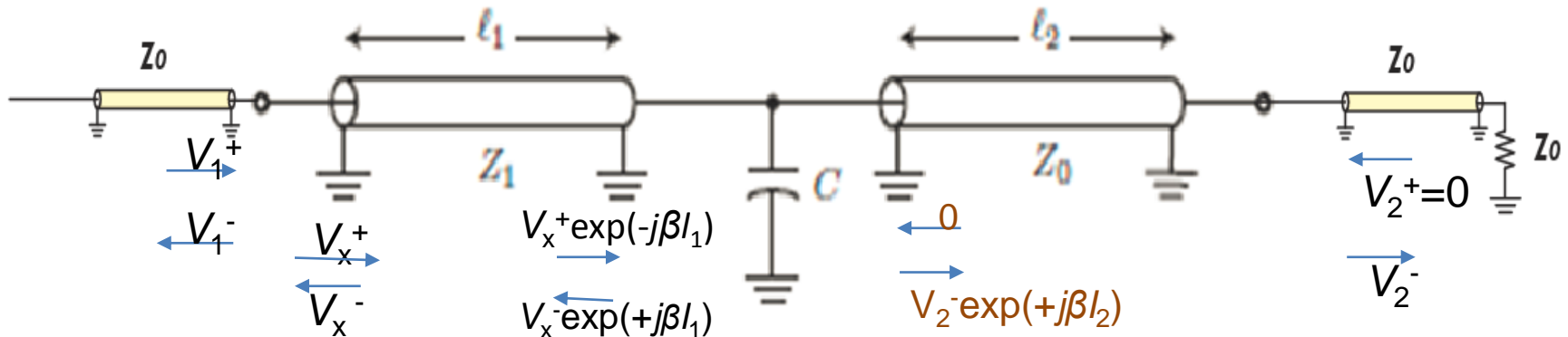
$$S_{21} = V_2^- / V_1^+ \text{ if } V_2^+ = 0$$



1.  $V_1^+ + V_1^- = V_x^+ + V_x^-$
2.  $V_1^+ / Z_0 - V_1^- / Z_0 = V_x^+ / Z_1 - V_x^- / Z_1$
3.  $V_x^+ \exp(-j\beta l_1) = V_x^+ \exp(-j\beta l_1) \rho_L$ , where  $\rho_L = (Z_0 // (j\omega C)^{-1} - Z_1) / (Z_0 // (j\omega C)^{-1} + Z_1)$
4.  $V_x^- \exp(+j\beta l_1) + V_x^+ \exp(-j\beta l_1) = V_2^- \exp(+j\beta l_1)$


(4 eqs, 5 variables:  $V_1^+, V_1^-, V_x^+, V_x^-, V_2^-$ )  $\Rightarrow S_{11}$  and  $S_{21}$  can be obtained

# Why S-Parameters ?

- *A.* S-parameter has a higher immunity when a cable is connected, if  $Z_{0,\text{Spara}} = Z_{0,\text{Cable}}$
- *B.* S-parameter has a straightforward connection to the power flow in a microwave system



# Why S-Parameters (A)

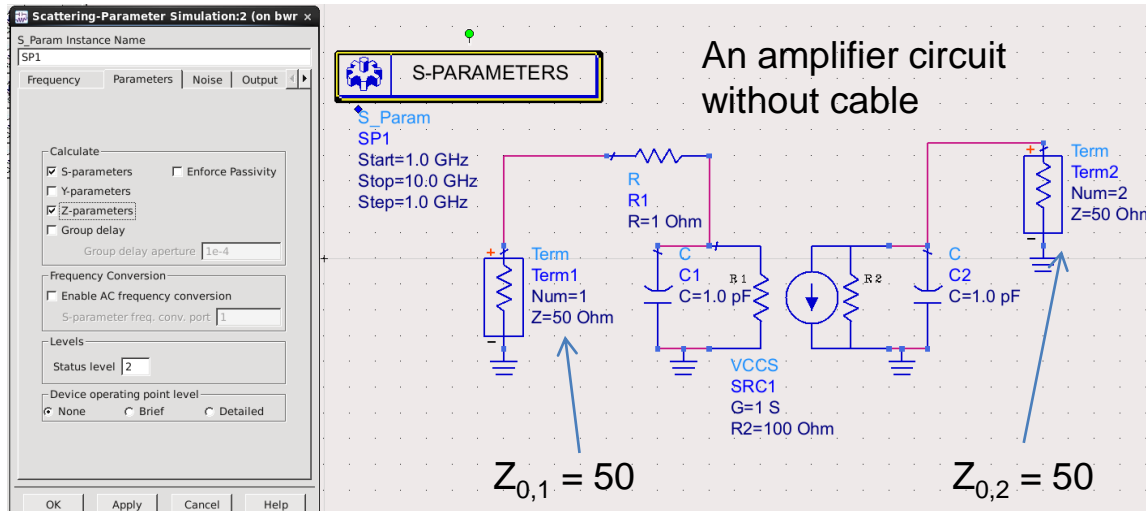

$$\begin{pmatrix} V_1^- \\ V_2^- \end{pmatrix} = \begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} \begin{pmatrix} V_1^+ \\ V_2^+ \end{pmatrix}$$

$$\begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$

**Z parameter**

freq	Z			
	Z(1,1)	Z(1,2)	Z(2,1)	Z(2,2)
1.000 GHz	159.158 / -89.640	1.278E-16 / 56.162	1.348E4 / 57.858	84.673 / -32.142

**S parameter**  
**Z<sub>0</sub> = 50**

freq	var("S")			
	(1,1)	(1,2)	(2,1)	(2,2)
1.000 GHz	0.996 / -34.880	0.000 / 0.000	62.139 / 150.403	0.385 / -43.971



**S parameter**  
**Z<sub>0</sub> = 60**

freq	var("S")			
	(1,1)	(1,2)	(2,1)	(2,2)
1.000 GHz	0.996 / -41.311	0.000 / 0.000	68.166 / 145.7...	0.334 / -56.562

- Both Z-parameters and S-parameters are complex numbers and are functions of frequency
- Only one Z-matrix for a given circuits at a frequency
- S parameters depend on the used reference impedance



# An amplifier circuit with cable

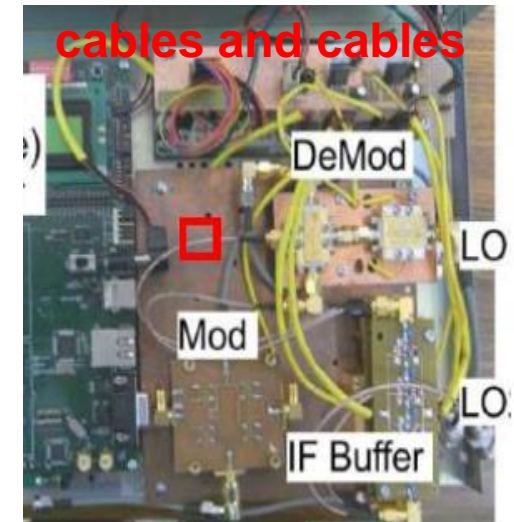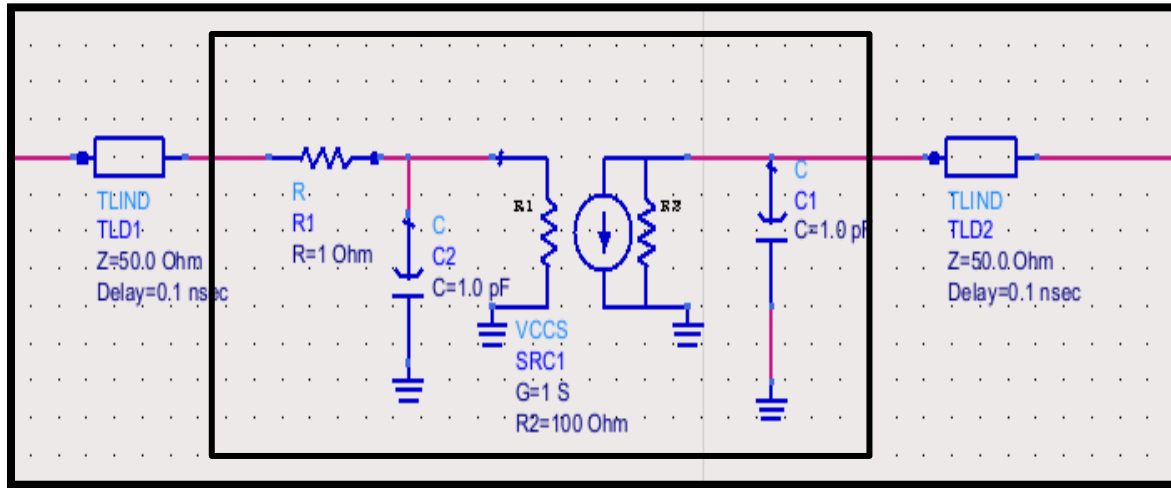

No cable

Add the two cable with  $Z_0$  of 50

**Z-parameter**

$$\begin{pmatrix} 159.2 \angle -89.6^\circ & 0 \\ 13480 \angle 58^\circ & 84.7 \angle -32^\circ \end{pmatrix} \xrightarrow{\text{Changes a lot}} \begin{pmatrix} 37.1 \angle -89.8^\circ & 0 \\ 3179 \angle 25.4^\circ & 36.9 \angle -39.1^\circ \end{pmatrix}$$

**S-parameter**  
 $Z_0 = 50$


$$\begin{pmatrix} 0.996 \angle -34.9^\circ & 0 \\ 62.1 \angle 150.4^\circ & 0.385 \angle -43.9^\circ \end{pmatrix} \xrightarrow{\text{Looks very similar}} \begin{pmatrix} 0.996 \angle -106.9^\circ & 0 \\ 62.1 \angle 78.4^\circ & 0.385 \angle -116.0^\circ \end{pmatrix}$$

**S-parameter**  
 $Z_0 = 60$

$$\begin{pmatrix} 0.996 \angle -41.3^\circ & 0 \\ 68.2 \angle 145.7^\circ & 0.334 \angle -56.5^\circ \end{pmatrix} \xrightarrow{\text{Changes}} \begin{pmatrix} 0.997 \angle -116.6^\circ & 0 \\ 58.9 \angle 71.8^\circ & 0.426 \angle -128.6^\circ \end{pmatrix}$$
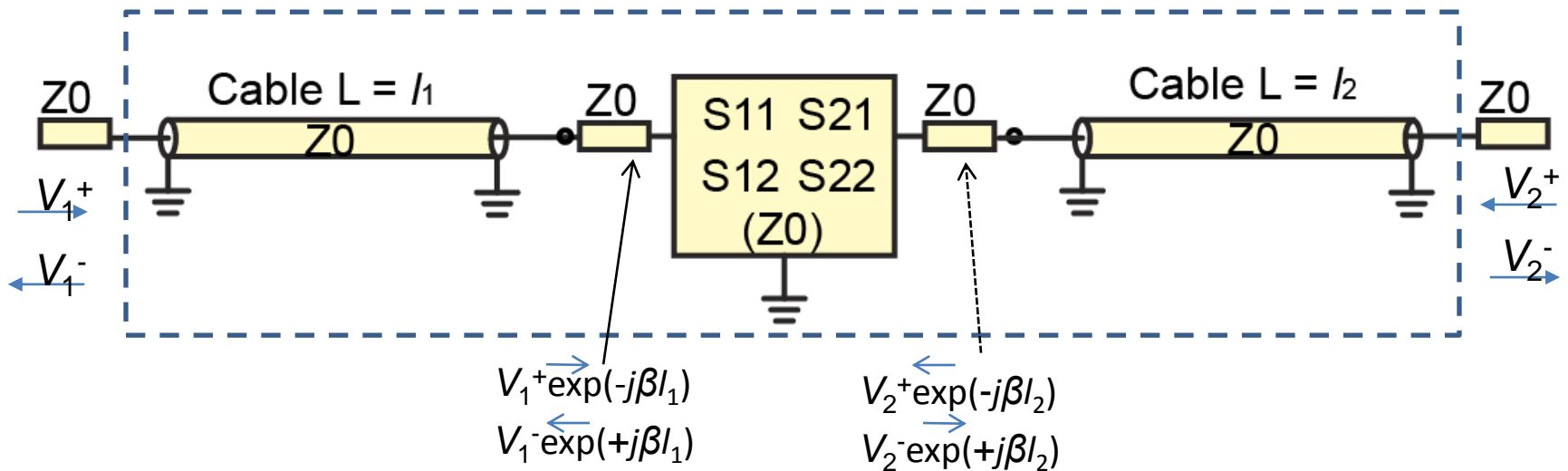
# Simple Proof

S-parameter magnitude do not change when cables are connected, if  $Z_{0,\text{Spara}} = Z_{0,\text{Cable}}$



$$\begin{pmatrix} V_1^- \exp(+j\beta h) \\ V_2^- \exp(+j\beta h) \end{pmatrix} = (S_{\text{no cable}}) \begin{pmatrix} V_1^+ \exp(-j\beta h) \\ V_2^+ \exp(-j\beta h) \end{pmatrix}$$




$$\begin{pmatrix} V_1^- \\ V_2^- \end{pmatrix} = (S_{\text{with cable}}) \begin{pmatrix} V_1^+ \\ V_2^+ \end{pmatrix}$$



$$(S_{\text{with cable}}) = \begin{pmatrix} \exp(-j\beta h) & 0 \\ 0 & \exp(-j\beta h) \end{pmatrix} (S_{\text{no cable}}) \begin{pmatrix} \exp(-j\beta h) & 0 \\ 0 & \exp(-j\beta h) \end{pmatrix} = \begin{pmatrix} S_{11} \exp[-j\beta(2h)] & S_{12} \exp[-j\beta(h+h)] \\ S_{21} \exp[-j\beta(h+h)] & S_{22} \exp[-j\beta(2h)] \end{pmatrix}$$
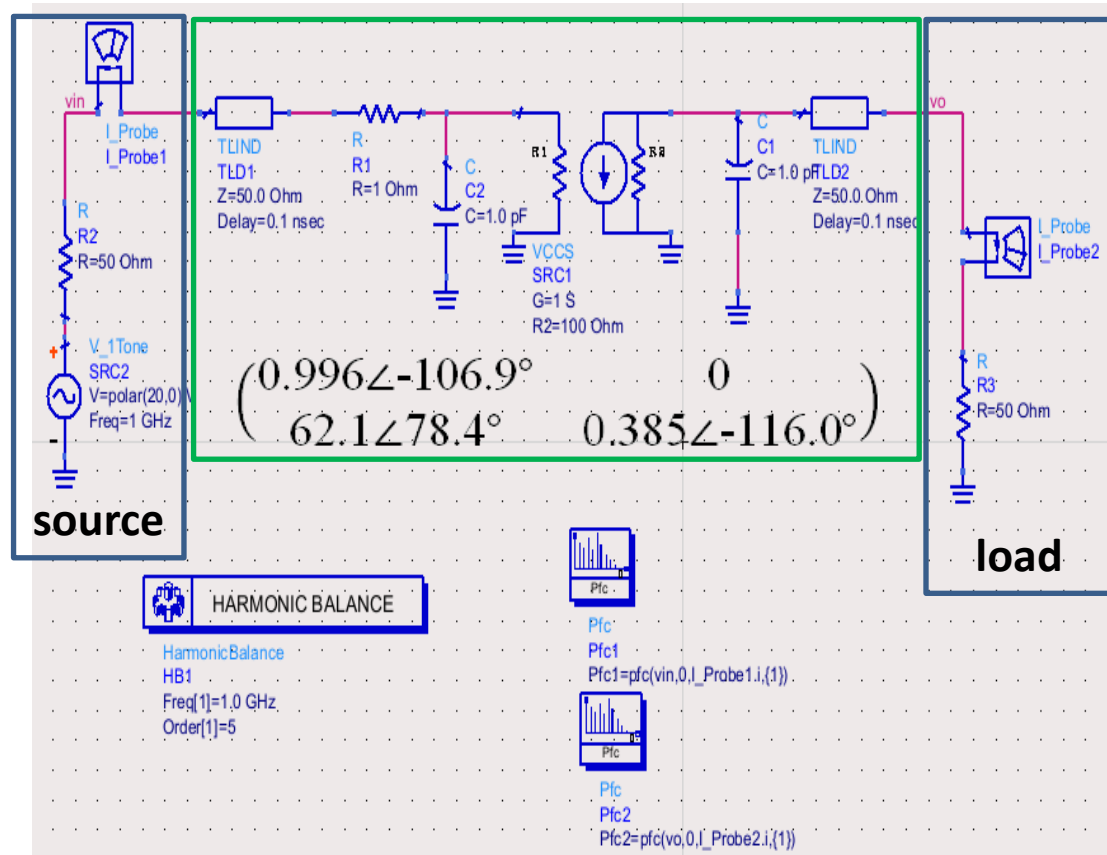
# Why S-Parameters ? (B)

S-parameter has a straightforward connection to the power flow in a microwave system



- In microwave systems, load and source impedances are usually  $50\Omega$  (why?)

- In this case, the source can provide maximum power of **1 W**

Power to the load:

$$1 * |S_{21}|^2 = 3856$$

- Power into the circuit:

$$1 * (1 - |S_{11}|^2) = 1 - 0.996^2 = 0.0072$$

( $S_{11} = 0.996$  indicates most power from the source is reflected)

- **Matching:** Create a  $50\text{-}\Omega$  load impedance for the source so all the  $1\text{-W}$  power can be delivered into the circuit

# Typical Commercial Amplifier S-parameters

ZX60-183-S+

BROADBAND AMPL / SMA / RoHS

Connector Type: SMA



Connector types may vary. Please refer to datasheet for details.

**Mini-Circuits®**

ISO 9001 ISO 14001 AS9100 Certified

RF/Microwave Components & Systems, DC to 50 GHz

Quantity	Unit Price
1 - 4	\$239.95
5 - 9	\$219.95
10 or more	\$209.95

$$10\log(|S_{21}|)$$

$$10\log(|S_{21}|/|S_{12}|)$$

$$(1+|S_{11}|)/(1-|S_{11}|)$$

$$(1+|S_{22}|)/(1-|S_{22}|)$$

will learn in later lectures

FREQUENCY (MHz)	GAIN (dB)	DIRECTIVITY	VSWR IN (:1)	VSWR OUT (:1)	POWER OUT @ 1 dB COMPR. (dBm)	IP3 (dBm)	NF (dB)
6000.00	24.24	43.74	1.13	1.23	17.80	27.78	7.40
7000.00	24.13	41.84	1.06	1.31	18.44	27.98	7.03
8000.00	24.19	38.28	1.26	1.47	18.49	27.72	6.90
9000.00	23.91	36.50	1.57	1.62	18.73	27.47	7.08


- Notice that the amplifier module is designed with  $|S_{11}|$  and  $|S_{22}|$  close to zero
- $|S_{11}| \sim 0$  means the module has a input impedance of  $50\Omega$  **when the load is  $50\Omega$**
- $|S_{22}| \sim 0$  means the module has a output impedance of  $50\Omega$  **when the source is  $50\Omega$**

Recall:  $S_{11} = V_1^-/V_1^+$  if  $V_2^+ = 0$ ;  $S_{21} = V_2^-/V_1^+$  if  $V_2^+ = 0$

# Impedance Matching Using Smith Chart


How can I extract the maximum available power (1 W) from the source ?

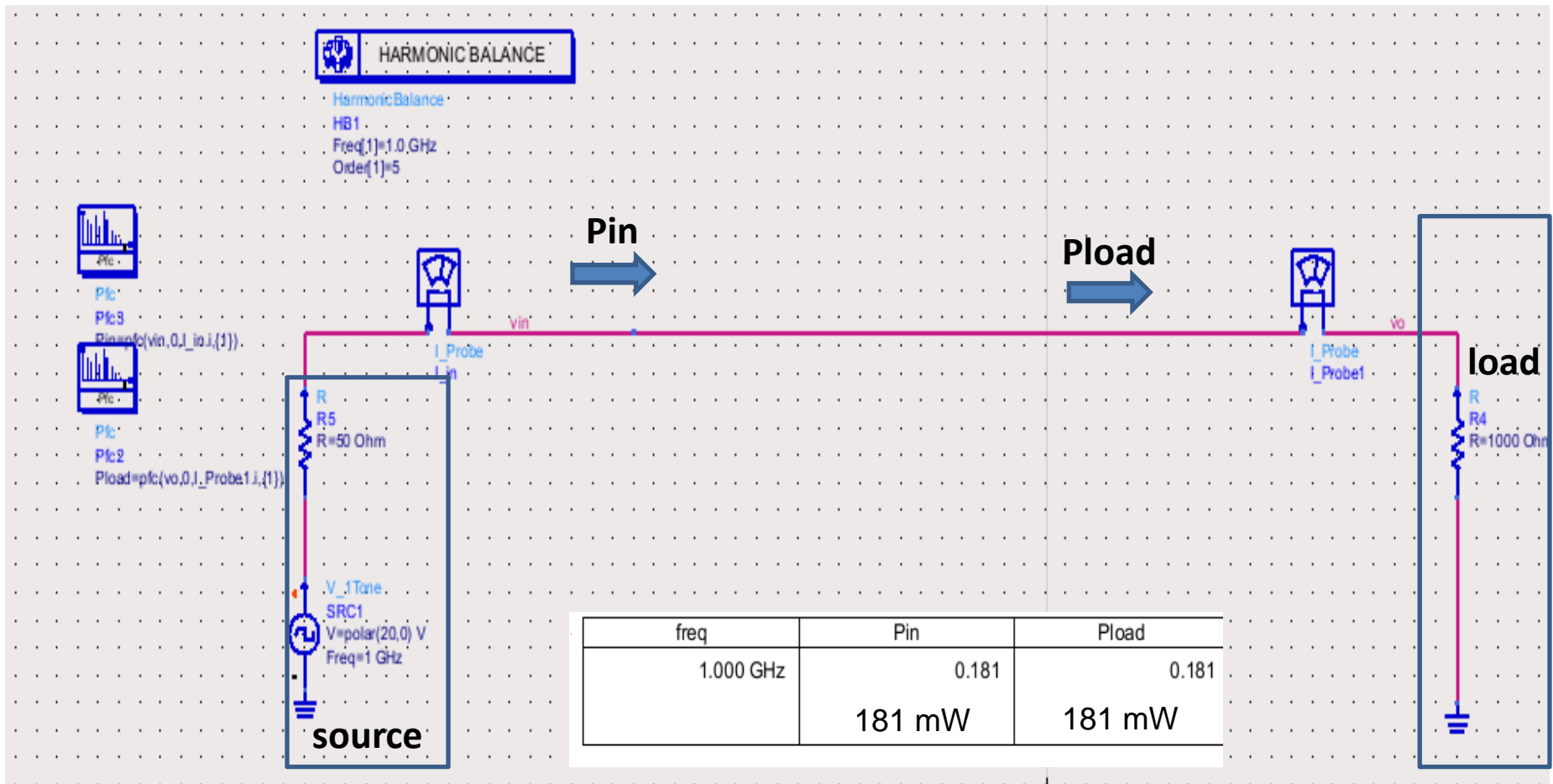**\*\*\*The source can deliver a maximum power of 1 W\*\*\***


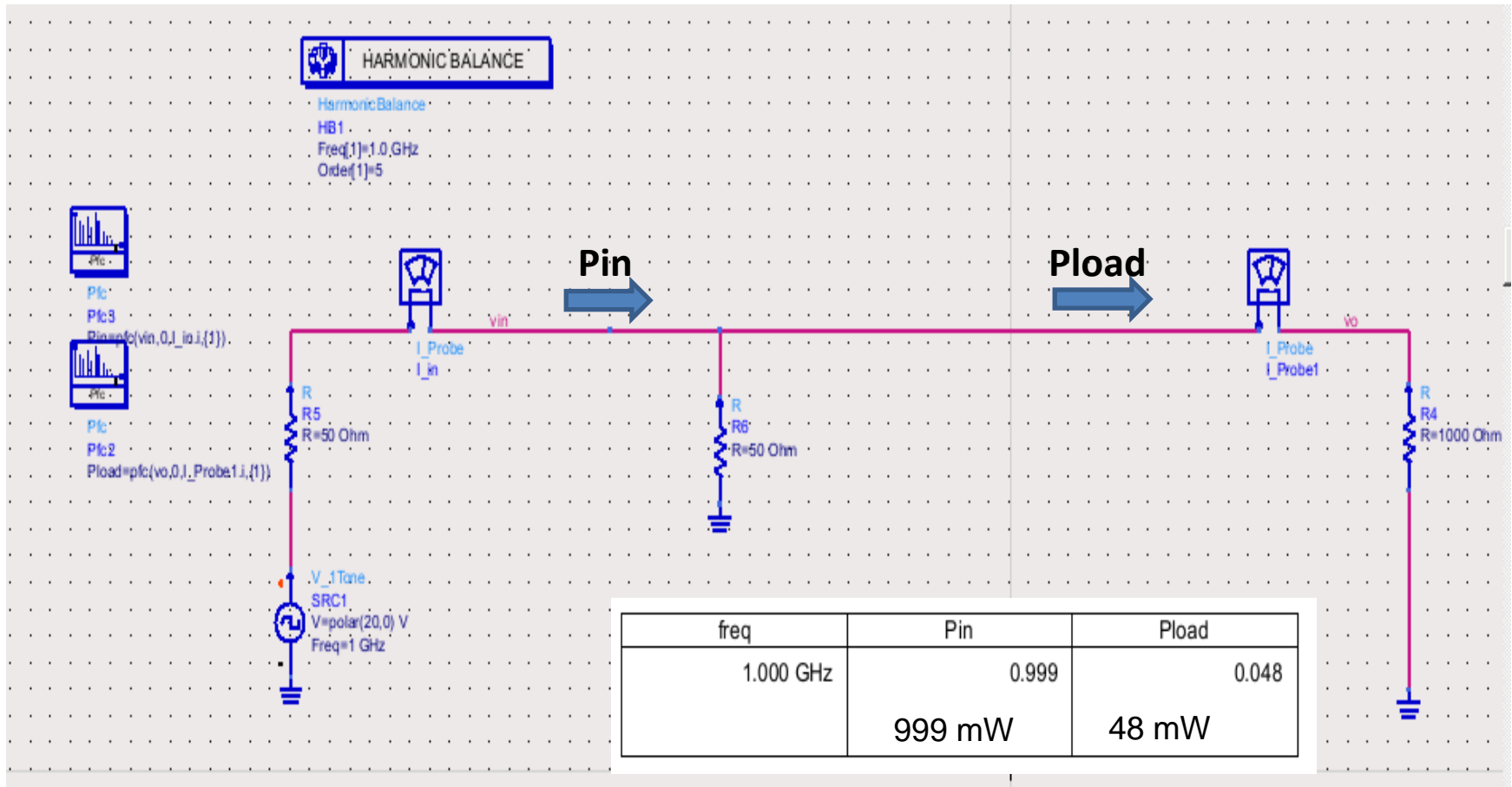
# Impedance Matching Using Smith Chart



Put a 50 ohm shunt resistor so the source see a ~50 ohm load



More power is extracted from the source (999 mW).... But...

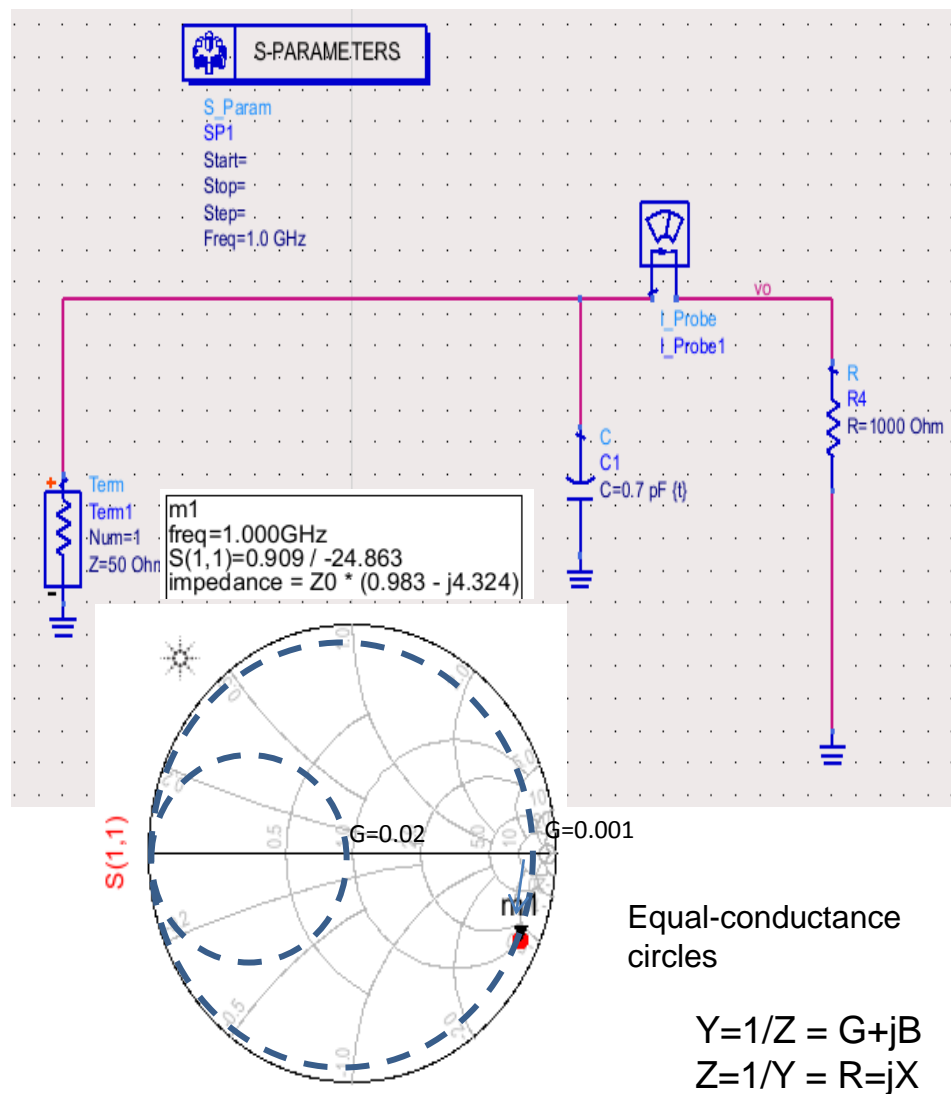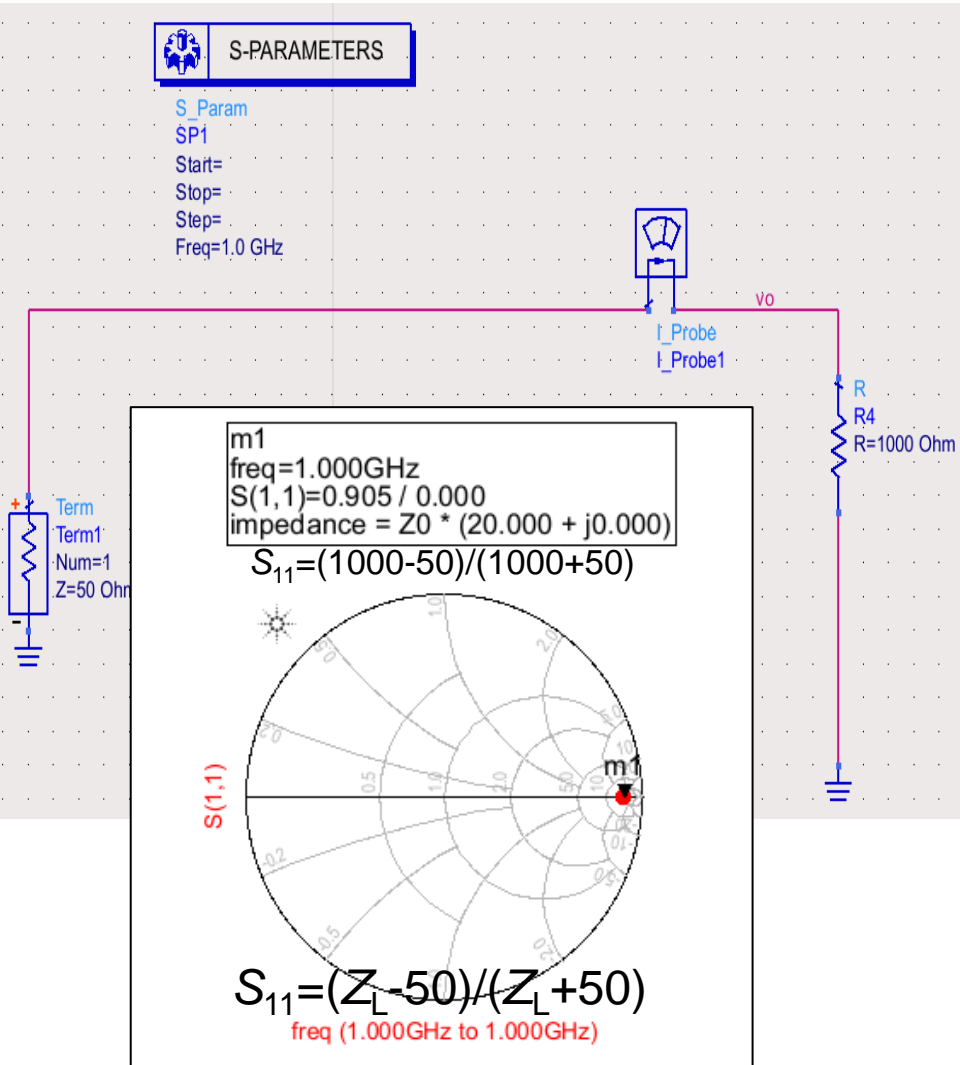
# Impedance Matching Using Smith Chart

- Present a 50-Ω impedance to source to extract the highest power using (low-loss) matching
- The 50-Ω input impedance does not vary when a cable is introduced between circuit and source



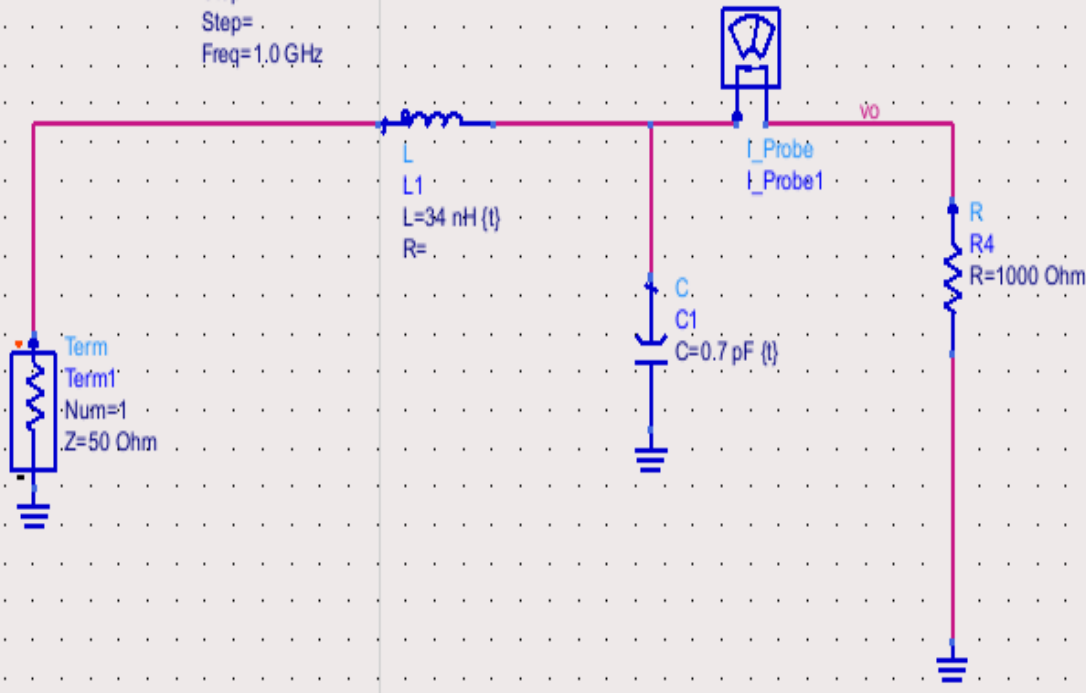
## S-PARAMETERS

S\_Param  
SP1  
Start=  
Stop=  
Step=  
Freq=1.0 GHz



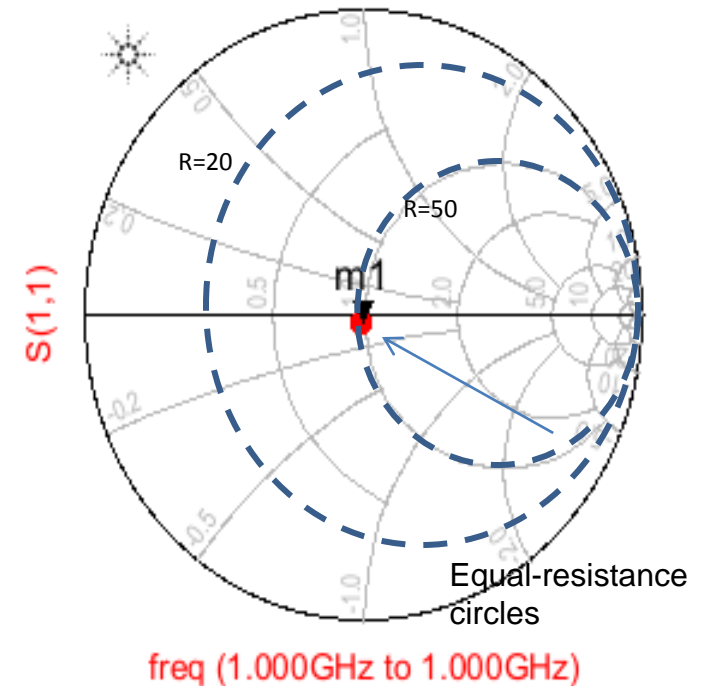m1  
freq=1.000GHz  
S(1,1)=0.027 / -106.817  
impedance = Z0 \* (0.983 - j0.051)



- Shunt-series matching
- First step: Move S11 on Smith Chart (along the equal-conductance circle) to a point on the equal-resistance circle with  $R = 50$
- Second step: Move S11 on Smith Chart (along the equal-resistance circle) to  $S_{11} = 0$
- The shunt component can be an inductor, but then the series one must be a capacitor






## HARMONIC BALANCE

HarmonicBalance

HB1

Freq[1]=1.0.GHz

Order[1]=5

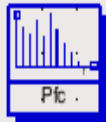

Pfc

Pfc3


Pin=pfc(vin,0,I\_in.i,{1}).



Pfc

Pfc2

Pload=pfc(vo,0,I\_Probe1.i,{1}).

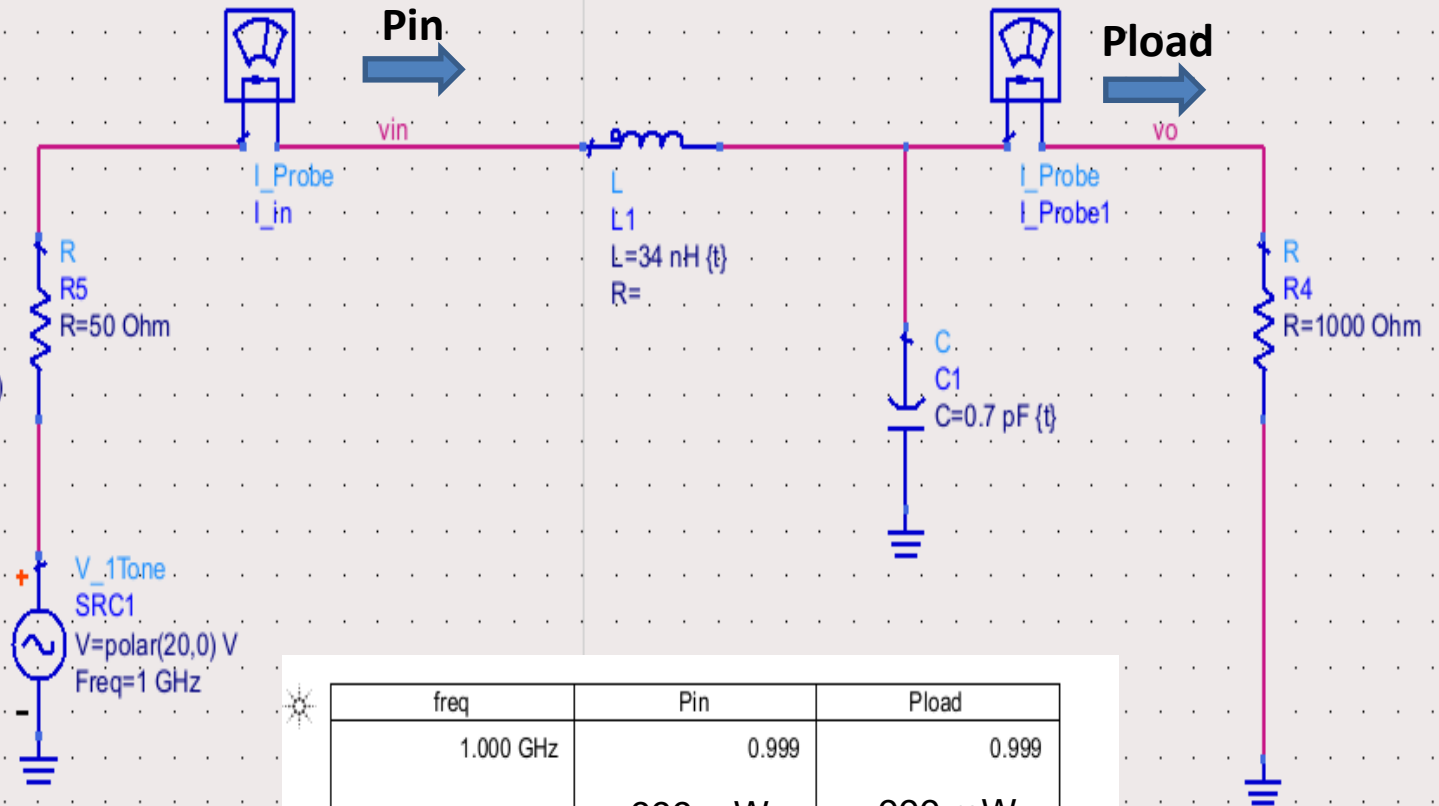

freq	Pin	Pload
1.000 GHz	0.999	0.999
	999 mW	999 mW

Great! Now the maximum power (1 W) is delivered to the load

# Hints for HW3.4

- Refer to

**EECS 117 Lecture 6: Lossy Transmission Lines and the Smith Chart**

<http://rfic.eecs.berkeley.edu/~niknejad/ee117/pdf/lecture6.pdf>

I suggest using microstrip line for the transmission line and use ADS linecal

T-line quarter-wave resonator:  $Q = \beta/2\alpha = \pi/(\lambda\alpha)$

$\alpha$  (without skin effect) =  $R'/Z_0$ ,

$R' = 0.025/\text{width}$  and  $Z_0$  is a function of line width and substrate thickness (10  $\mu\text{m}$ )

\*Maybe there is an optimal width and  $Z_0$  for the best  $Q^*$

If you want to use meander T-line, assume the distance between two parallel lines is 40  $\mu\text{m}$

LC tank resonator:  $Q = \omega L/R_L$ , where  $R_L$  is the series resistance of the inductor

Loop inductor:

$$L_{\text{loop}} \approx \mu_0 \mu_r \left( \frac{D}{2} \right) \cdot \left( \ln \left( \frac{8 \cdot D}{d} \right) - 2 \right)$$

