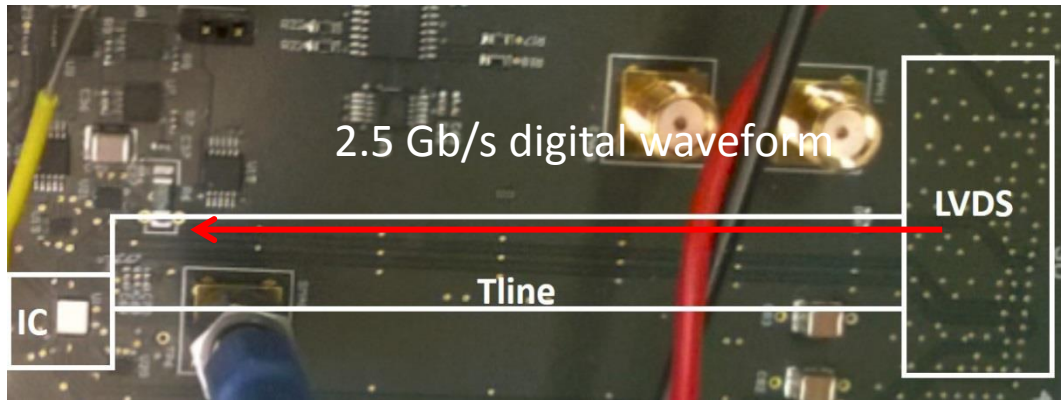


142/242 Discussion (9/6/2017)


- (1) Review transmission line behavior in time-domain
- (2) An example (reflection, energy)
- (3) HW 2.3, 2.4

Transmission Line in Circuits

T-line in time domain to connect components




Desired Waveform

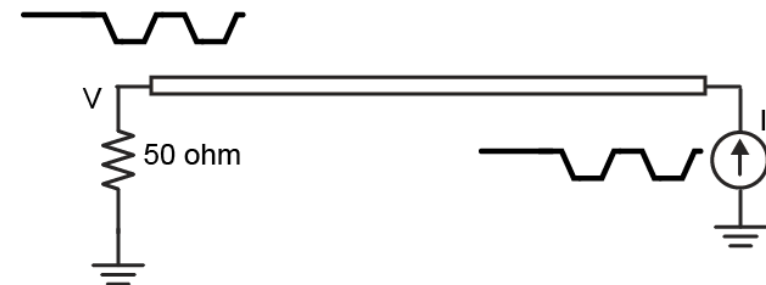


Things get nasty if $Z_0 \neq 50 \text{ ohm}$

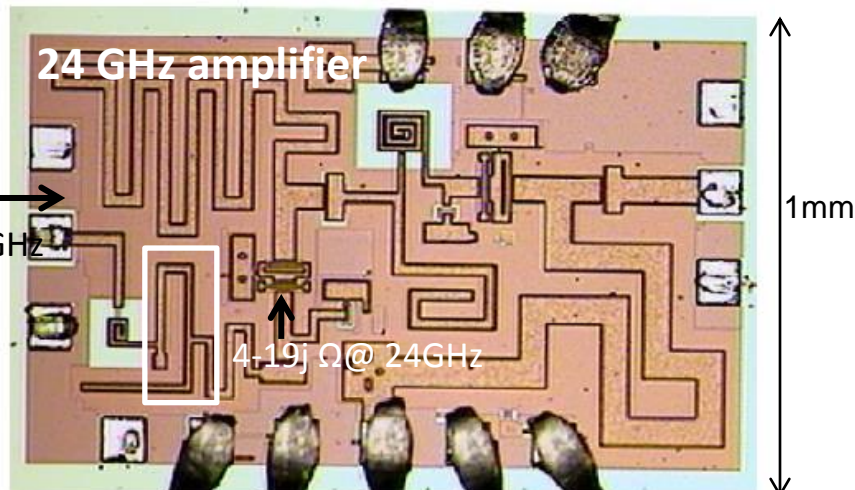T-line in frequency domain (**narrow-band** impedance matching to 50 ohm)



Again, why 50Ω ?

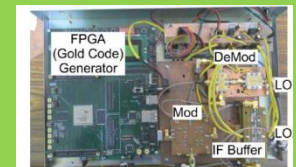


Most systems are less compact and need coaxial cables for the connection. 50-Ω cables are the best

⇒ Components are designed with 50-Ω input impedance

⇒ Now your T-line on PCB has also to be design with $Z_0 = 50$

Transmission Line Theory

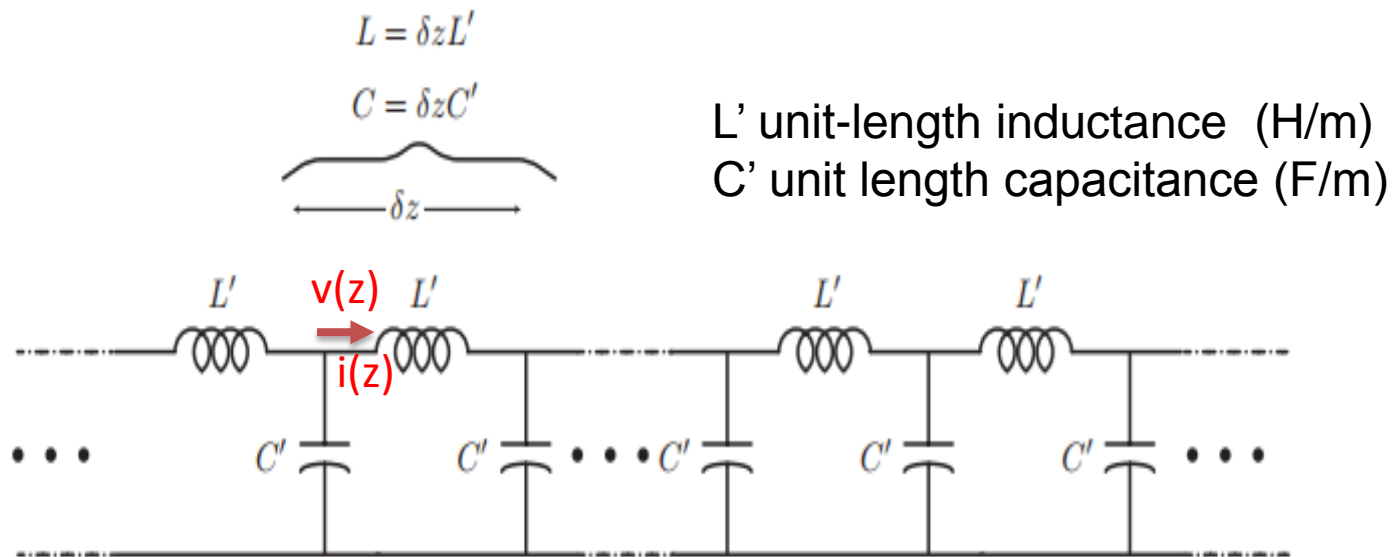

Solve KCL and KVL

$$\begin{aligned}
 -\frac{\partial i}{\partial z} &= C' \frac{\partial v}{\partial t} \\
 -\frac{\partial v}{\partial z} &= L' \frac{\partial i}{\partial t}
 \end{aligned}
 \Rightarrow
 \begin{aligned}
 \frac{\partial^2 v}{\partial z^2} &= L' C' \frac{\partial^2 v}{\partial t^2} \\
 \frac{\partial^2 i}{\partial z^2} &= L' C' \frac{\partial^2 i}{\partial t^2}
 \end{aligned}$$

First Sol Second Sol
Forward backward

$$\begin{aligned}
 V(z,t) &= \boxed{f^+(z - v \times t)}_{v^+} + \boxed{f^-(z + v \times t)}_{v^-} \\
 I(z,t) &= \boxed{f^+(z - v \times t)/Z_0}_{i^+} - \boxed{f^-(z + v \times t)/Z_0}_{i^-}
 \end{aligned}$$

$$Z_0 = \sqrt{\frac{L'}{C'}} \quad v = \sqrt{\frac{1}{L' C'}}$$

- **Characteristic Impedance (Z_0) is the voltage-current ratio for the wave solutions (not node solution)**
- Why a wide transmission line has a lower Z_0 ?

ADS Transmission Line Calculator

Tools => LineCal: A useful tool in ADS to calculate T-line Z_0

Dielectric Constant: E_r \uparrow Z_0 \downarrow λ_{eff} \downarrow

Substrate Thickness: H \uparrow Z_0 \uparrow λ_{eff} ?

Trace Width: W \uparrow Z_0 \downarrow λ_{eff} \downarrow

LineCalc/untitled (on bwr-cr720-3.eecs.berkeley.edu)

File Simulation Options Help

Component
Type: MLIN ID: MLIN: MLIN_DEFAULT

Substrate Parameters
ID: MSUB_DEFAULT

Parameter	Value	Units
Er	9.600	N/A
Mur	1.000	N/A
H	10.000	mil
Hu	3.9e+34	mil
T	0.150	mil
Cond	4.1e7	N/A
TanD	0.000	N/A
Rough	0.000	mil
DielectricLossModel	1.000	N/A
FreqForEpsrTanD	1.0e9	N/A
LowFreqForTanD	1.0e3	N/A
HighFreqForTanD	1.0e12	N/A

Physical
W: 25.000 mil
L: 100.000 mil

Synthesize Analyze


Electrical
Z0: 47.250 Ohm
E_Eff: 230.000 deg

Calculated Results
K_Eff = 6.400
A_DB = 0.070
SkinDepth = 0.000

Diagram: A 3D perspective view of a microstrip line on a substrate. The substrate has a thickness H . The microstrip has a width W and a length L . The top surface of the substrate is labeled 1 and the bottom surface is labeled 2.

Equation: $360^\circ \times \text{Length} / \lambda_{\text{eff}} = 360^\circ \times L \times \text{frequency} / v$

Example

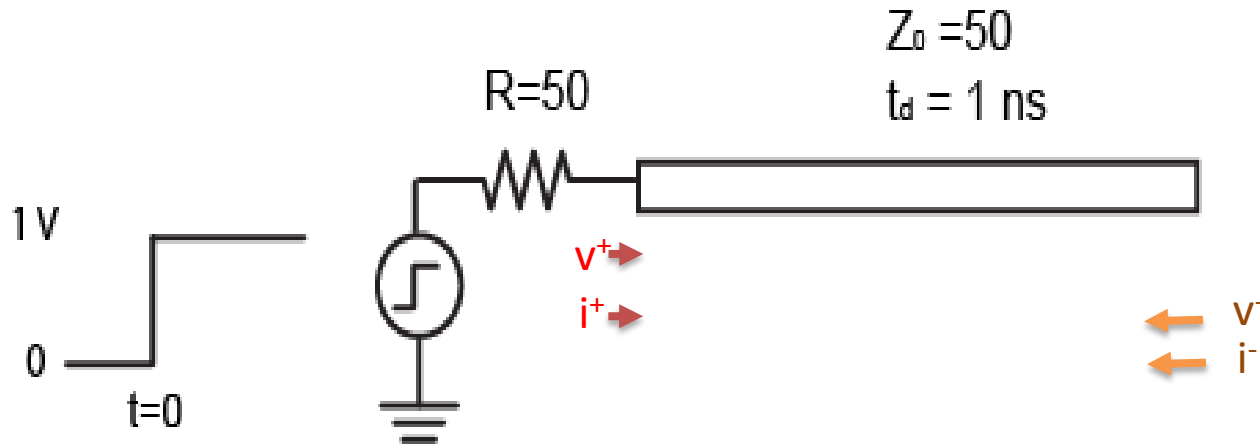

At $t=0$, a forward traveling voltage/current wave is excited

- What are the values of v^+ and i^+ ?

$$V^+ = 0.5, I^+ = 0.01$$

- What will happen at $t = 1 \text{ ns}$?

backward wave is excited to satisfy boundary condition

- What are the value of v^- and i^- ?



$$0.01 - I^- = 0 \Rightarrow I^- = 10\text{mA} \Rightarrow V^- = 0.5$$

- Will a new forward traveling wave be generated by v^- and i^- ?

No! no new wave has to be generated to satisfy the boundary condition, so the bounce stops

Now, You might understand why the T-line (cable) should have a load impedance of Z_0


Example: Time-Domain Diagram

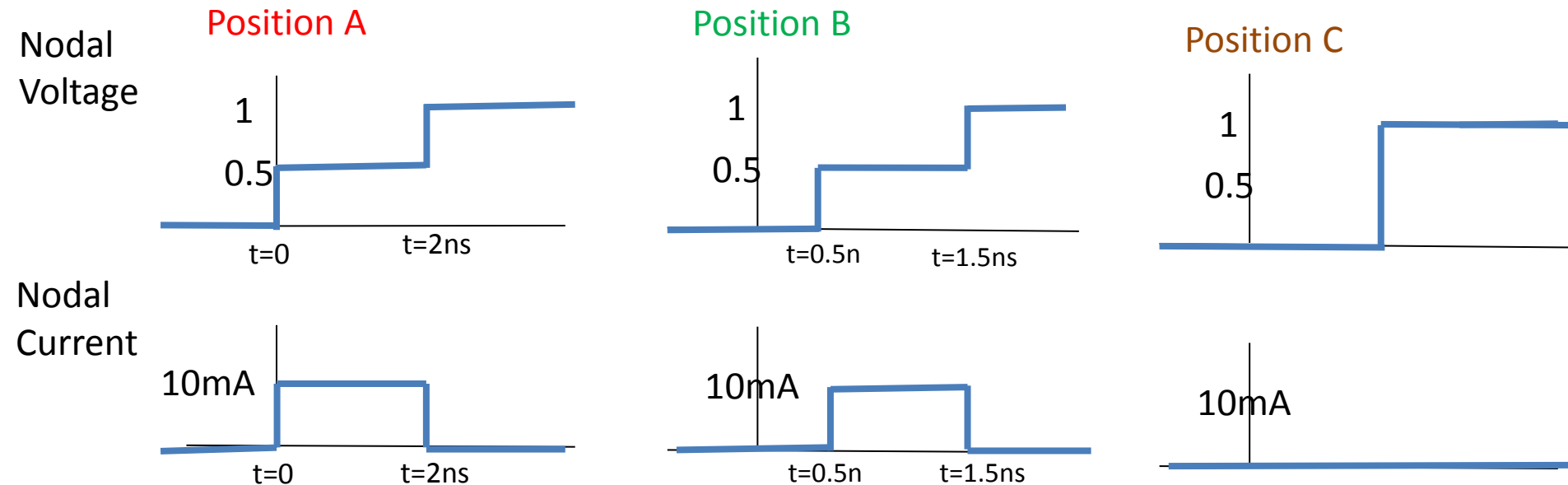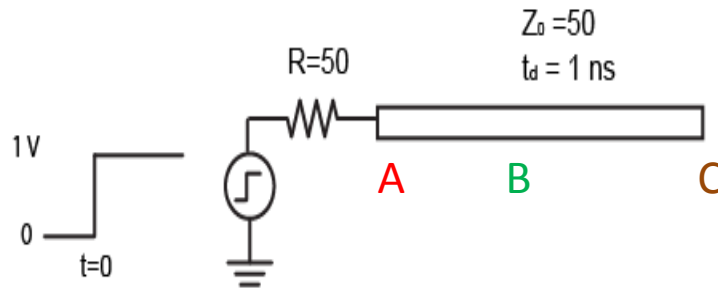




What is the energy stored on the transmission line?

- (1) Source energy – Energy dissipated on resistor = $10\text{mA} \cdot 1\text{V} \cdot 2\text{ns} - 10\text{mA} \cdot 10\text{mA} \cdot 50 \cdot 2\text{ns} = 20\text{pJ} - 10\text{pJ} = 10\text{pJ}$
- (2) $(1/2)CV^2 = (1/2) \times C \times 1^2 = 10\text{pJ}$ $C = C' \cdot L = (1/Z_0 v) \cdot (v \cdot t_d) = t_d / Z_0 = 20\text{e-12}$




Example: Simulation in ADS

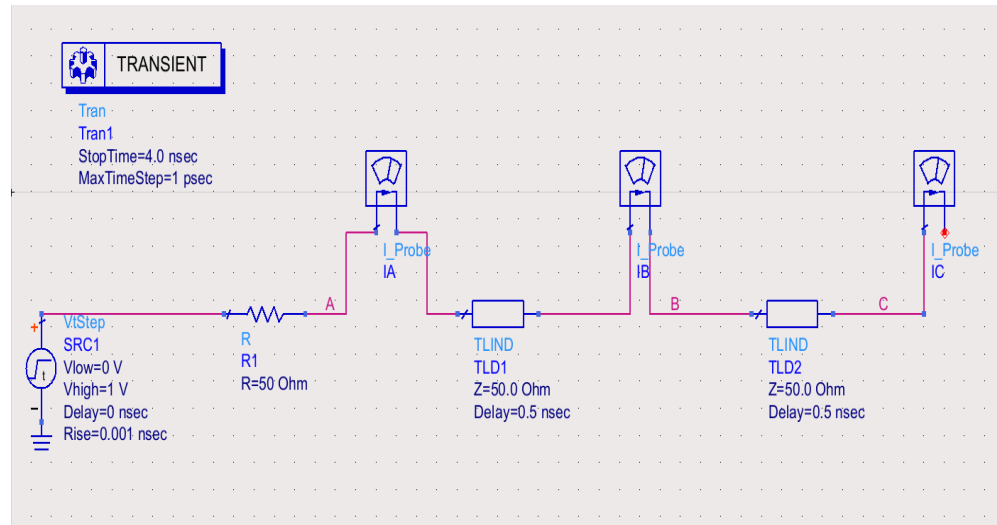

Nodal
Voltage

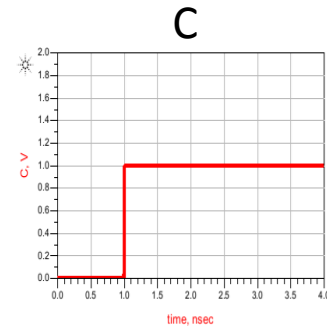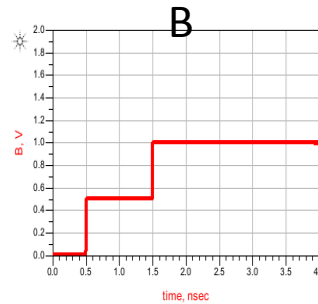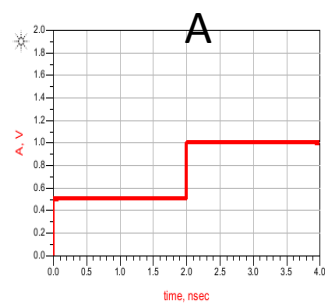

Nodal
Current

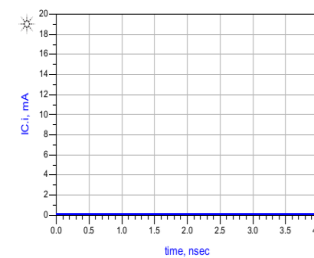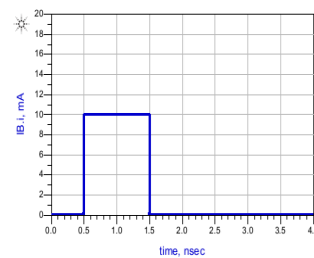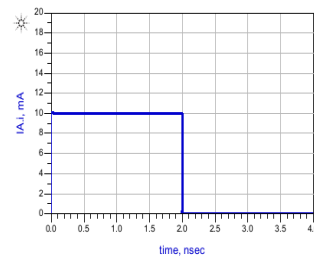

HW2.4


4. A step voltage source is connected to a transmission line, as shown above.

- (a) Draw the time-domain response of the current flowing through the voltage source.
- (b) Using the time-domain response to calculate the total energy delivered by the voltage source and the total energy consumed on the resistor. What is the energy stored on the transmission line at $t = \infty$ s?
- (c) Express the total capacitance of the transmission line by the line parameters Z_0 and t_d .



example

- (d) Repeat parts (a)-(b) but with the source resistance changed to $2Z_0$.




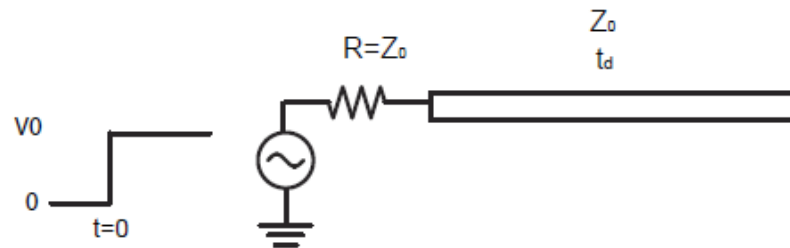
- (e) Calculate the energy stored on the transmission line at $t = \infty$ s. Is there a way to bypass the tedious sum of infinite geometric series?



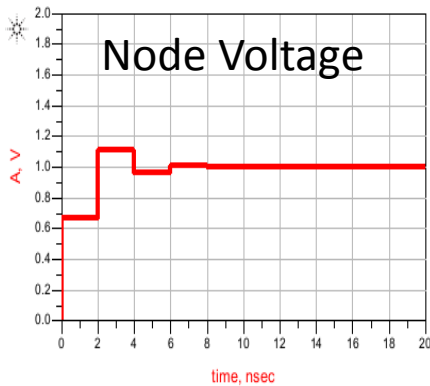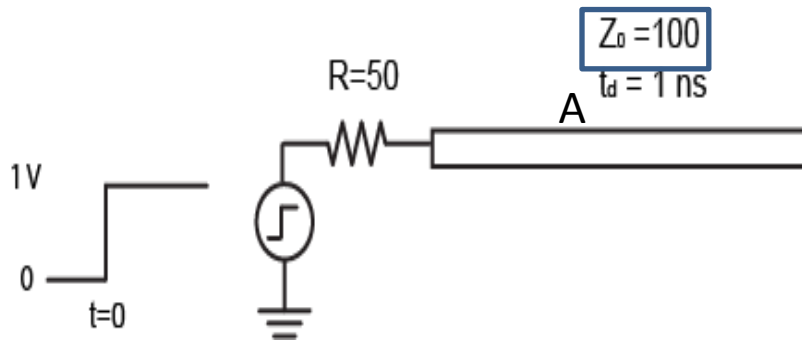- 1. Calculate the total energy from the source then take away the total energy consumed on the resistor
- 2. Directly use the steady-state voltage and the total capacitor ($C_{\text{total}} = t_d/Z_0$)



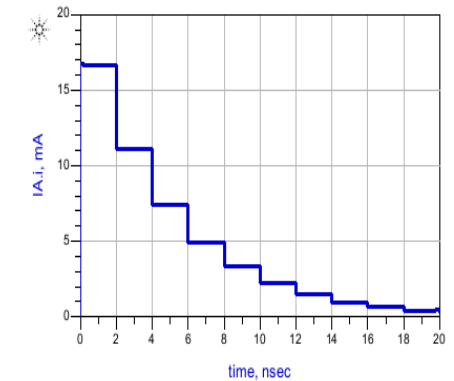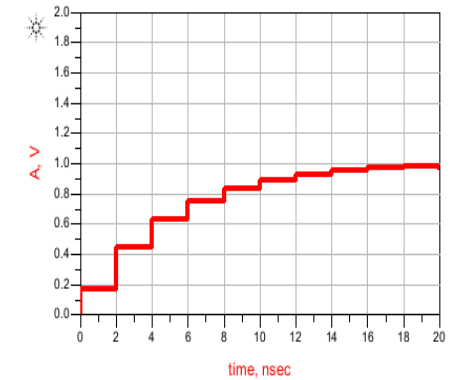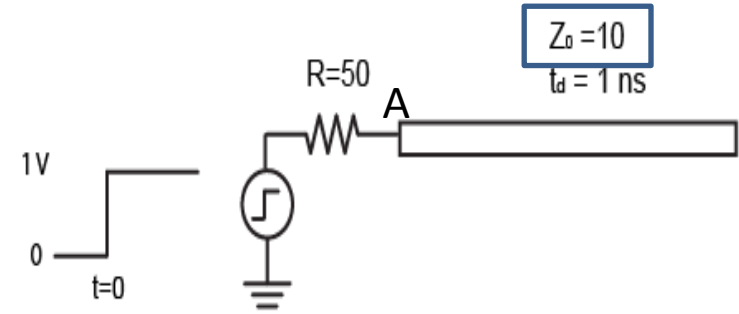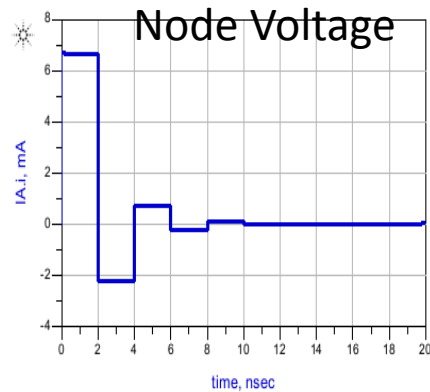
$$\begin{aligned}
 V_1^+ &= 0.66 & I_1^+ &= 6.6\text{mA} \\
 V_1^- &= 0.66 & I_1^- &= 6.6\text{mA} \\
 V_2^+ &= -0.22 & I_2^+ &= -2.2\text{mA} \\
 V_2^- &= -0.22 & I_2^- &= -2.2\text{mA} \\
 V_3^+ &= 0.07 & I_2^+ &= 0.07 \text{ mA}
 \end{aligned}$$



Resemble RC charging curves

Use ADS to verify your calculation!!!


HW2.3

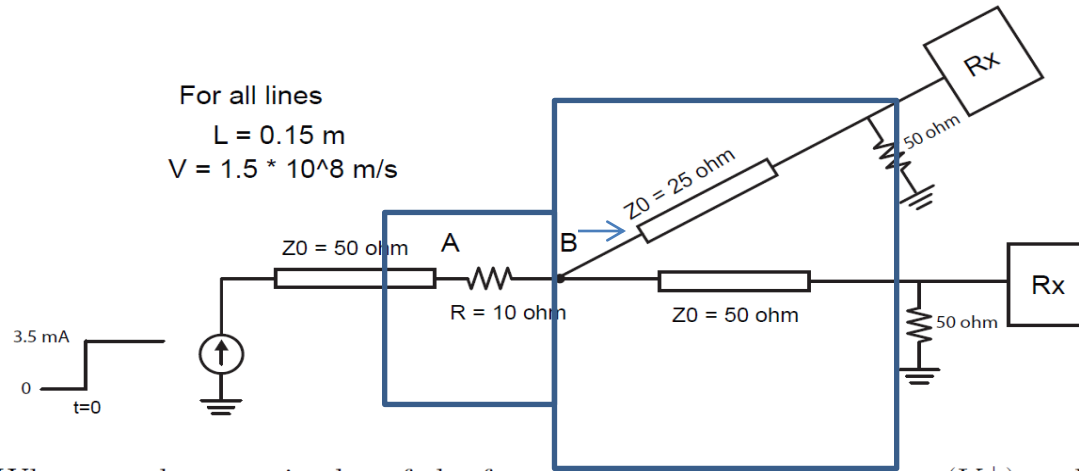


- What are the magnitudes of the forward traveling voltage wave (V^+) and the backward traveling wave (V^-) at A and B, at $t = 1.5 \text{ ns}$.
- Repeat part (a) but at time $t = 3.5 \text{ ns}$.
- Repeat part (a) but at time $t = \infty$ (steady state). Is there a way to bypass the tedious sum of infinite geometric series?

New Stuffs

A resistor in series !!!
 Parallel T-lines !!!

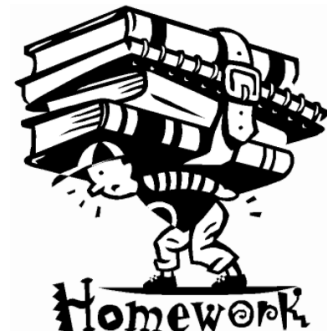

HW2.3

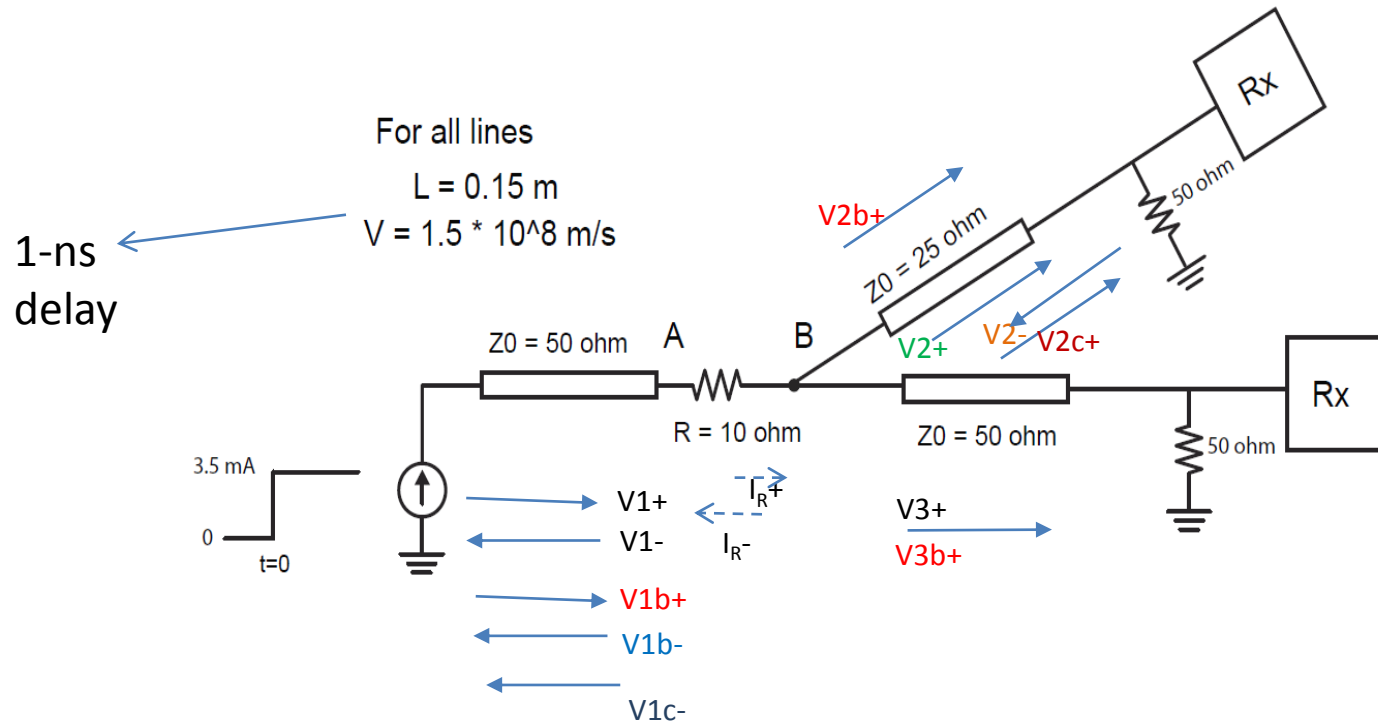

At 1 ns:

$$V1^+ = 175 \text{ mV}, V1^- = 175 \cdot (26.7 - 50) / (26.7 + 50) = 175 \cdot -0.30 = -53 \text{ mV}$$

$$I_{R^+} = 175 / 50 + 53 / 50 = 4.56 \text{ mA}$$

$$V2^+ = V3^+ = V1^+ + V1^- - 10 \cdot I_{R^+} = 77.4 \text{ mV}$$

At 3.5 ns:

$V1^-$ has created a new forward traveling wave: $V1b^+ = V1^- = -53 \text{ mV}$

$V1b^+$ has created $V2b^+$ and $V3b^+$ (as $V1^+$ creating $V2^+$ and $V3^+$)

$$\Rightarrow V2b^+ = V3b^+ = -23.4$$

$$V1b^- = 16 \text{ mV}$$

$V2^+$ has created a new backward wave: $V2^- = 25.8 \text{ mV}$

$V2^-$ has created $V2c^+$: $V2c^+ = 25.8 \cdot (60 / 50 - 25) / (60 / 50 + 25) = 1 \text{ mV}$

$$I_{R^-} = (25.8 - 1) / 25 \cdot (50 / 110) = 0.48 \text{ mA}$$

$$V1c^- = V2^+ + V2c^+ - 10 \cdot I_{R^-} = 22 \text{ mV}$$

At Point A:

$$V^+ = 175 (V1^+) + -53 (V1b^+) = 122 \text{ mV}$$

$$V^- = -53 (V1^-) + 16 (V1b^-) + 22 (V1c^-) = -15 \text{ mV}$$


At Point B:

$$V^+ = 77.4 (V2^+) + -23.4 (V2b^+) + -1 (V2c^+) = 53 \text{ mV}$$


$$V^- = 25.8 \text{ mV} (V2^-)$$

HW2.3




Check it in simulation

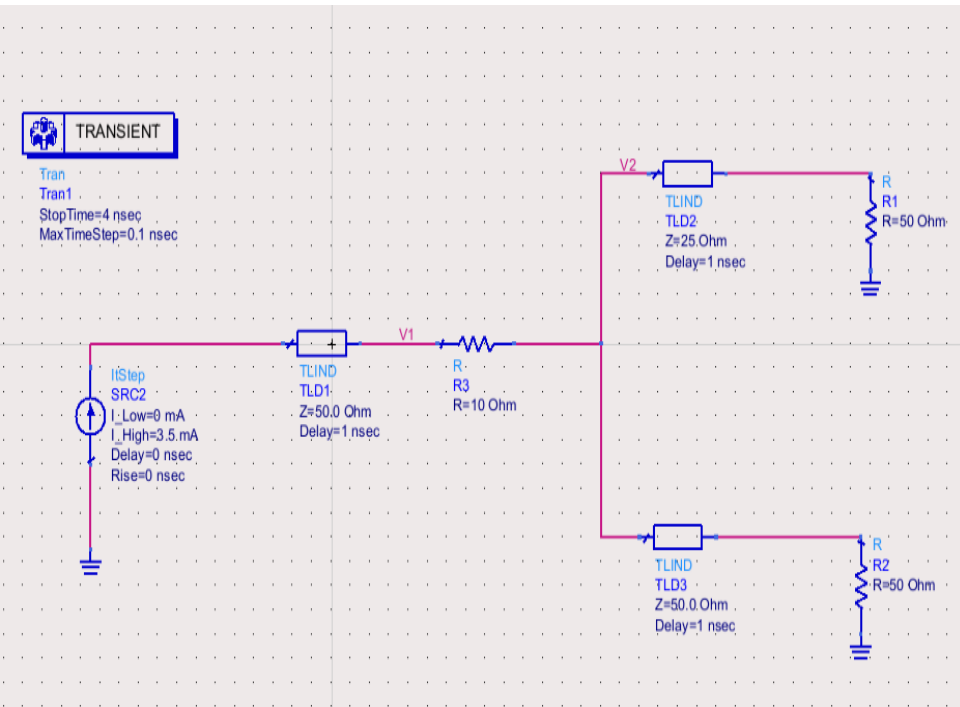

V1 Node

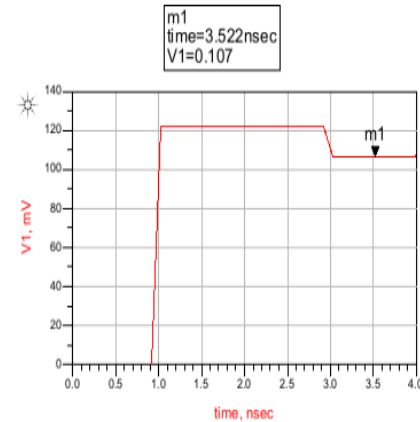

V2 Node

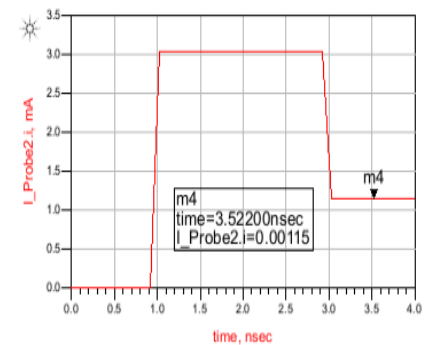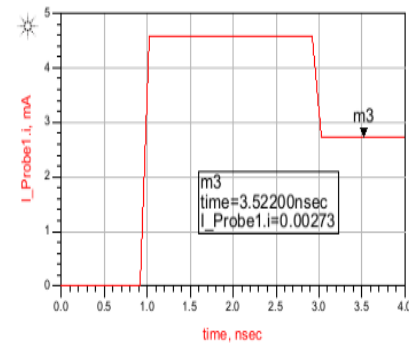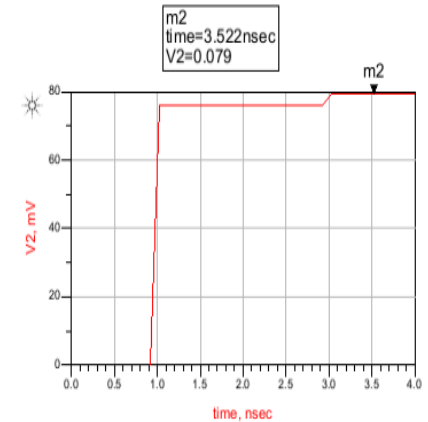

Only Nodal **V** and **I** can be measured(or Simulated)

$$V^+ + V^- = V$$

$$V^+/Z_0 - V^-/Z_0 = I$$



$$V^+, V^-$$