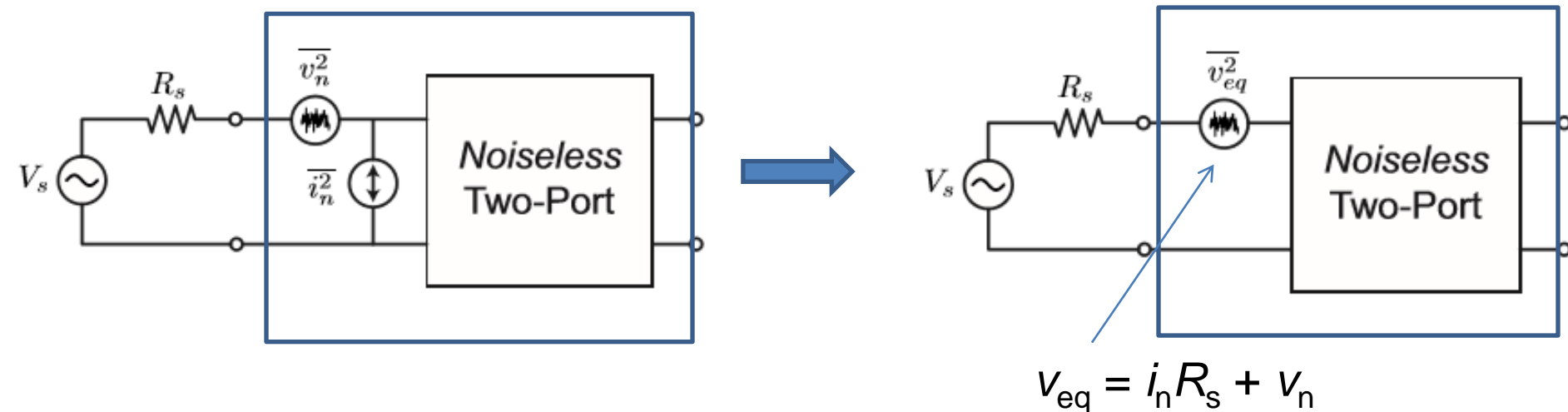


Today's Agenda (Oct. 18)

- Hw7: Noise Modeling, NF Calculation
- Noise Circle and Ga Circle
- Review on Some Important Concepts in Two-port Theory (HW6)



$$\overline{v_{eq}^2} = \overline{v_n^2} + \overline{i_n^2} R_s^2 + 2 R_s \langle v_n i_n \rangle$$

$\langle v_{eq}^2 \rangle$ depends on R_s

$$NF_{R_s} = 1 + \langle v_{eq}^2 \rangle / \langle v_{n,s}^2 \rangle = 1 + \langle v_{eq}^2 \rangle / 4kTR_s \Rightarrow \langle v_{eq,R_s}^2 \rangle = 4kT R_s (NF_{R_s} - 1)$$


$\langle v_{eq,R_s}^2 \rangle$ can be calculated if NF_{R_s} is given

$\langle v_{eq,R_s2}^2 \rangle$ is unknown without knowing NF_{R_s2}

Ex. A circuit has $NF = 10$ dB with $50\text{-}\Omega$ R_s . What is the new NF if the source resistance becomes $100\text{ }\Omega$? I don't know

Source Impedance For The Best NF

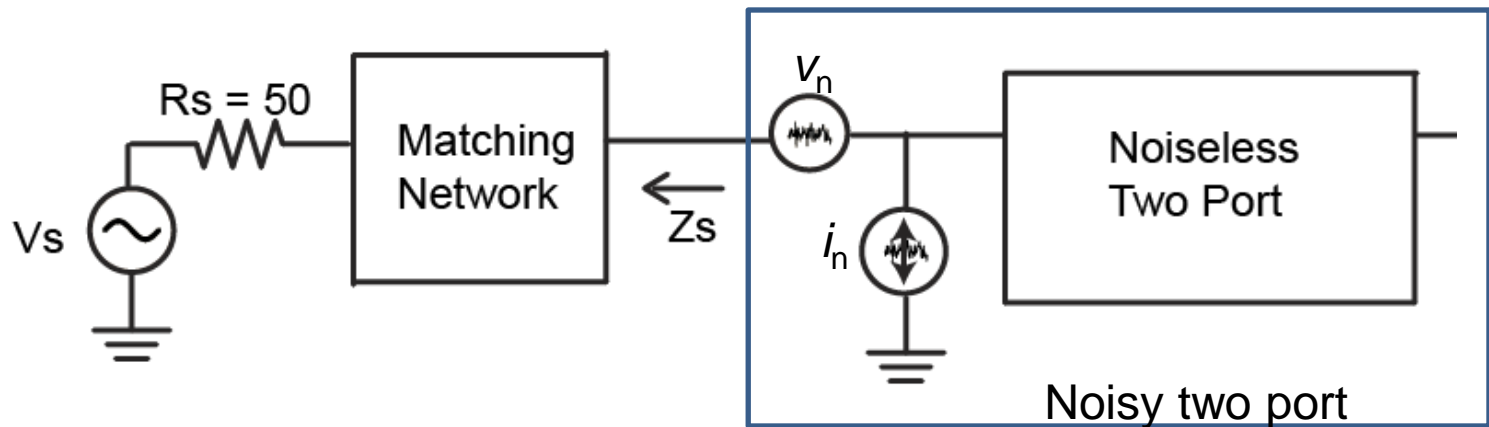- R_s can be matched to a complex $Z_s = R_{Zs} + jX_{Zs}$
- Assume $i_n = i_c + i_u$ $i_c = Y_c V_n$ and $\langle i_u V_n \rangle = 0$




$$V_{eq} = V_n(1 + Y_c Z_s) + Z_s i_u$$

$$NF_{Rs} = 1 + \langle V_{eq}^2 \rangle / 4kTR_{Zs} = 1 + \langle V_n^2 \rangle |1 + Y_c Z_s|^2 / 4kTR_{Zs} + \langle i_u^2 \rangle |Z_s|^2 / 4kTR_{Zs}$$

$$= 1 + \frac{R_n |1 + Y_c Z_s|^2}{R_{Zs}} + \frac{G_u |Z_s|^2}{R_{Zs}}$$
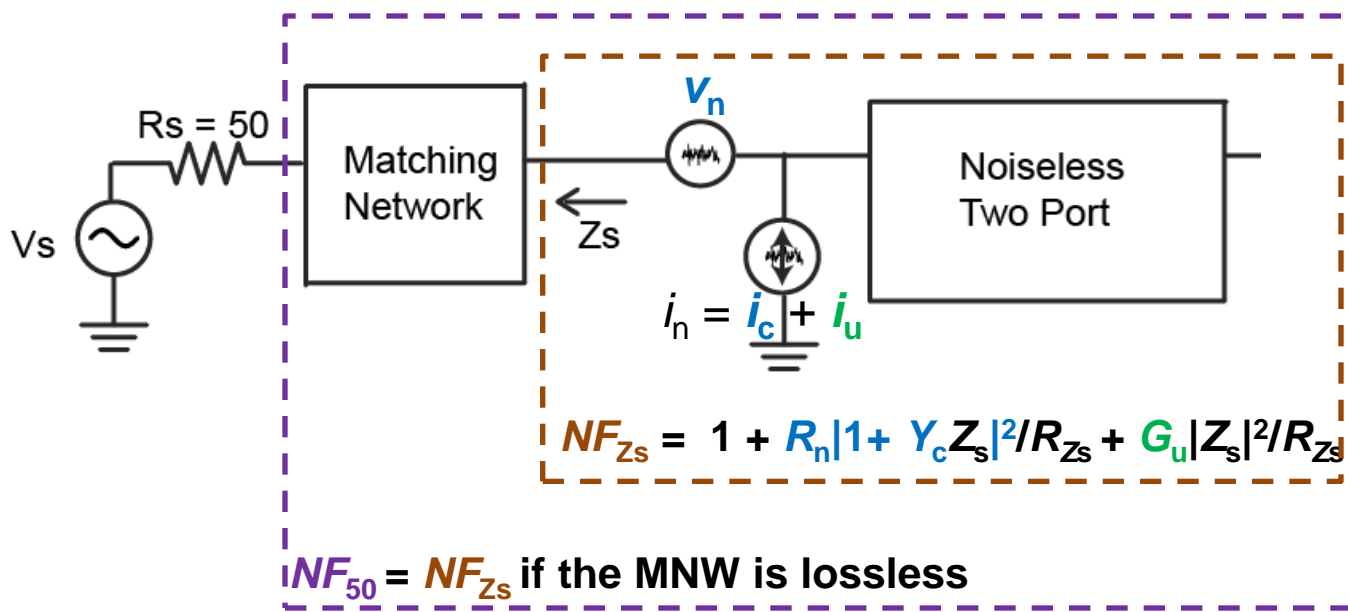
$$\langle V_n^2 \rangle = 4kTR_n \text{ and } \langle i_u^2 \rangle = 4kTG_u$$



Simplified case with $Y_c = 0$ (noise voltage and source are uncorrelated)

$$NF_{Z_s} = 1 + R_n/R_{Z_s} + G_u|Z_s|^2/R_{Z_s},$$

$$NF_{\min} = 1 + 2(R_n G_u)^{0.5} \quad \text{with} \quad Z_s = (R_n/G_u)^{0.5} + 0j$$

No simplification

$$NF_{Z_s} = 1 + R_n|1 + Y_c Z_s|^2/R_{Z_s} + G_u|Z_s|^2/R_{Z_s}$$

$$Y_c = G_c + jB_c, \quad Z_s = (G_s + jB_s)^{-1}$$

$$B_{\text{opt}} = B_s = -B_c$$



$$G_{\text{opt}} = G_s = \sqrt{\frac{G_u}{R_n} + G_c^2}$$

- The minimum achievable noise figure is



$$F_{\min} = 1 + 2G_c R_n + 2\sqrt{R_n G_u + G_c^2 R_n^2}$$

$$F = F_{\min} + \frac{R_n}{G_s} |Y_s - Y_{\text{opt}}|^2$$

NF of a Lossy Transmission Line (1/3)

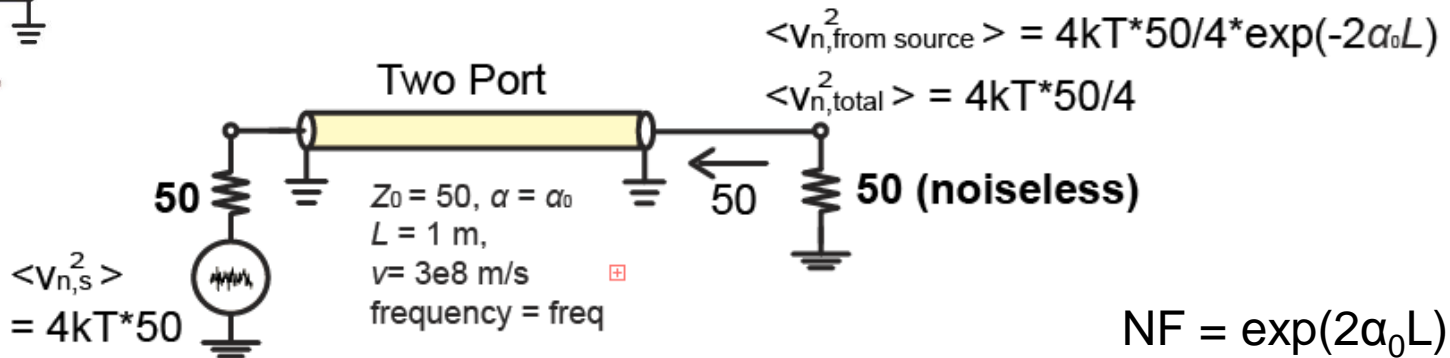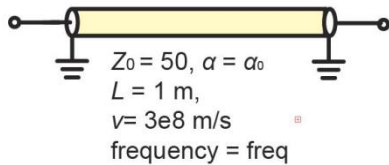



Simulation

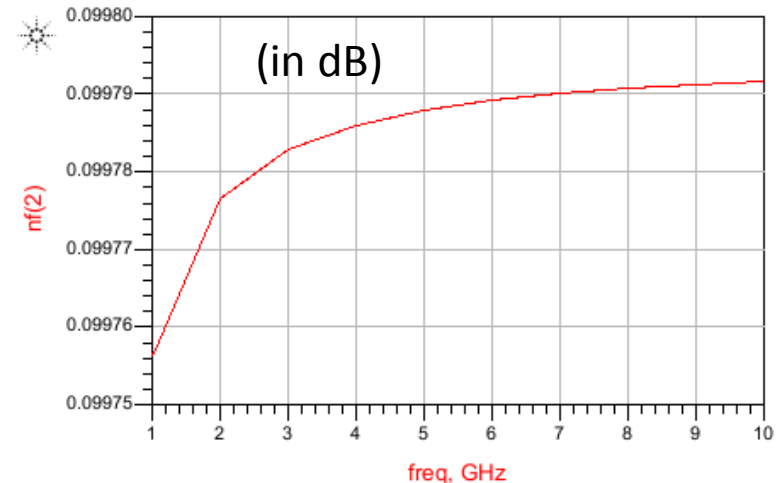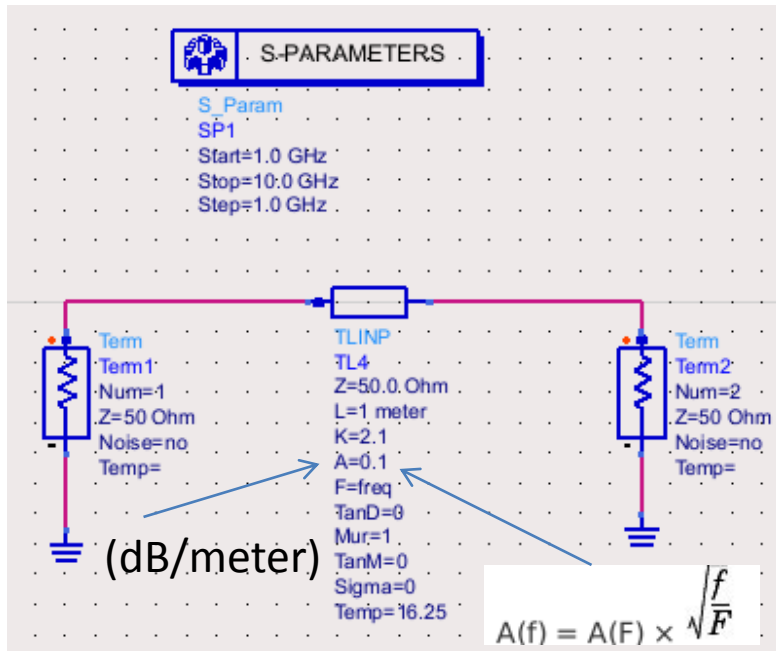


$$\begin{aligned}
 dB[exp(-\alpha_0)] &= A = -0.1 \\
 \alpha_0 &= 0.0115 \\
 exp(2\alpha_0L) &= 1.023 \\
 NF &= 0.099 \text{ dB}
 \end{aligned}$$

NF of a Lossy Transmission Line (2/3)

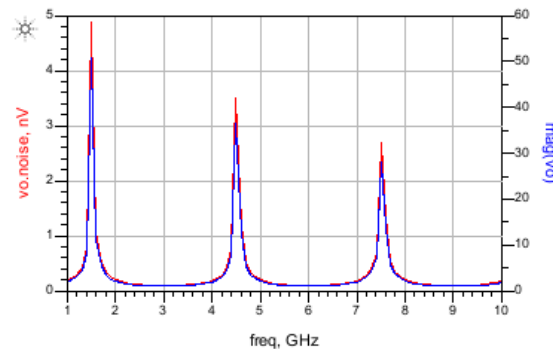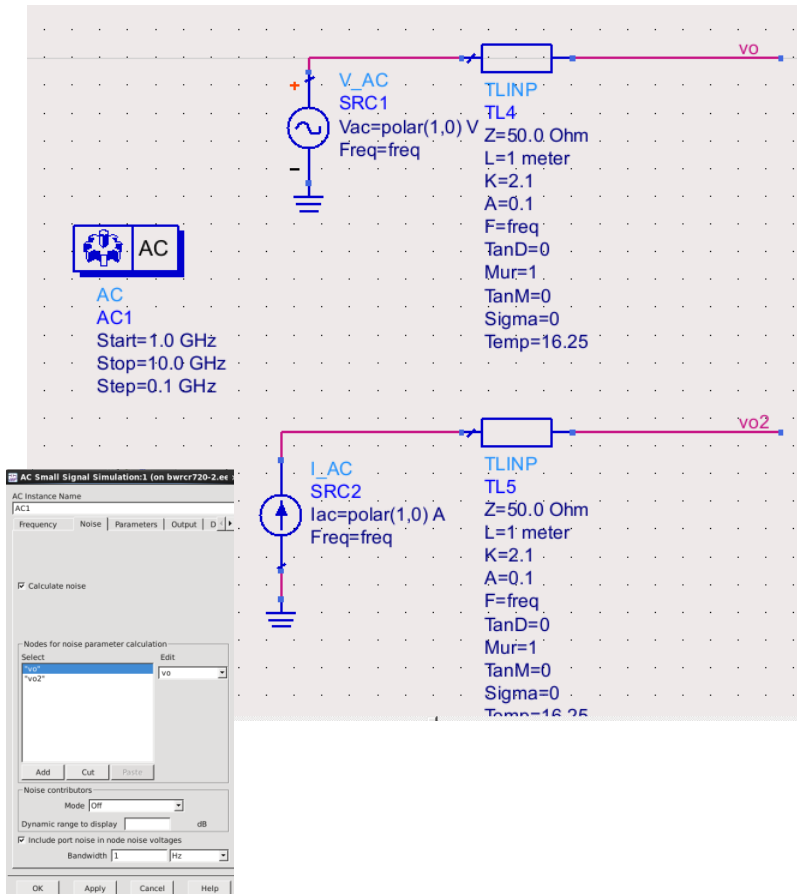Calculate NF by input referred voltage and noise sources (very difficult)



freq	vo.noise/vo
1.000 GHz	9.523E-11 / -1.105
1.100 GHz	9.537E-11 / 178.576
1.200 GHz	9.552E-11 / -1.929
1.300 GHz	9.566E-11 / 177.118
1.400 GHz	9.579E-11 / -5.436
1.500 GHz	9.591E-11 / 144.159
1.600 GHz	9.601E-11 / -172.609
1.700 GHz	9.610E-11 / 3.372
1.800 GHz	9.617E-11 / -177.849
1.900 GHz	9.622E-11 / 1.552
2.000 GHz	9.626E-11 / -178.811
2.100 GHz	9.627E-11 / 0.942
2.200 GHz	9.628E-11 / -179.241
2.300 GHz	9.626E-11 / 0.616
2.400 GHz	9.624E-11 / -179.502

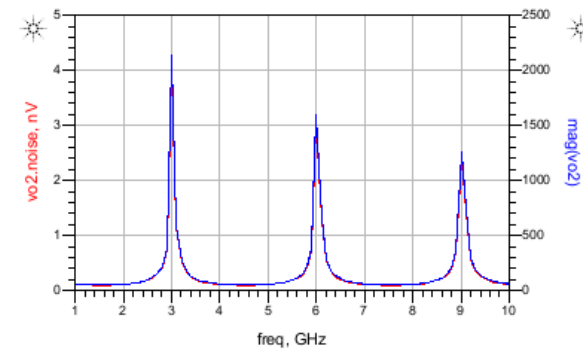

freq	vo2.noise/vo2
1.000 GHz	1.932E-12 / -89.585
1.100 GHz	1.929E-12 / 90.325
1.200 GHz	1.926E-12 / -89.757
1.300 GHz	1.923E-12 / 90.167
1.400 GHz	1.921E-12 / -89.905
1.500 GHz	1.918E-12 / 90.025
1.600 GHz	1.916E-12 / -90.045
1.700 GHz	1.915E-12 / 89.884
1.800 GHz	1.913E-12 / -90.190
1.900 GHz	1.912E-12 / 89.731
2.000 GHz	1.911E-12 / 90.355
2.100 GHz	1.911E-12 / 89.549
2.200 GHz	1.911E-12 / -90.563
2.300 GHz	1.911E-12 / 89.303
2.400 GHz	1.912E-12 / -90.864


NF of a Lossy Transmission Line (3/3)

Assume the input referred noise current and noise voltage are uncorrelated


$$\overline{v_{eq}^2} = \overline{v_n^2} + \overline{i_n^2} R_s^2 \quad \text{NF}_{Rs} = 1 + \langle v_{eq}^2 \rangle / \langle v_{n,s}^2 \rangle$$

Eqn $\text{NF} = 1 + (\text{mag}(\text{vo2.noise}/\text{vo2} \cdot 50)) \cdot (\text{mag}(\text{vo2.noise}/\text{vo2} \cdot 50)) / 4 / 1.38\text{e-}23 / 290 / 50 + (\text{mag}(\text{vo.noise}/\text{vo})) \cdot (\text{mag}(\text{vo.noise}/\text{vo})) / 4 / 1.38\text{e-}23 / 290 / 50$

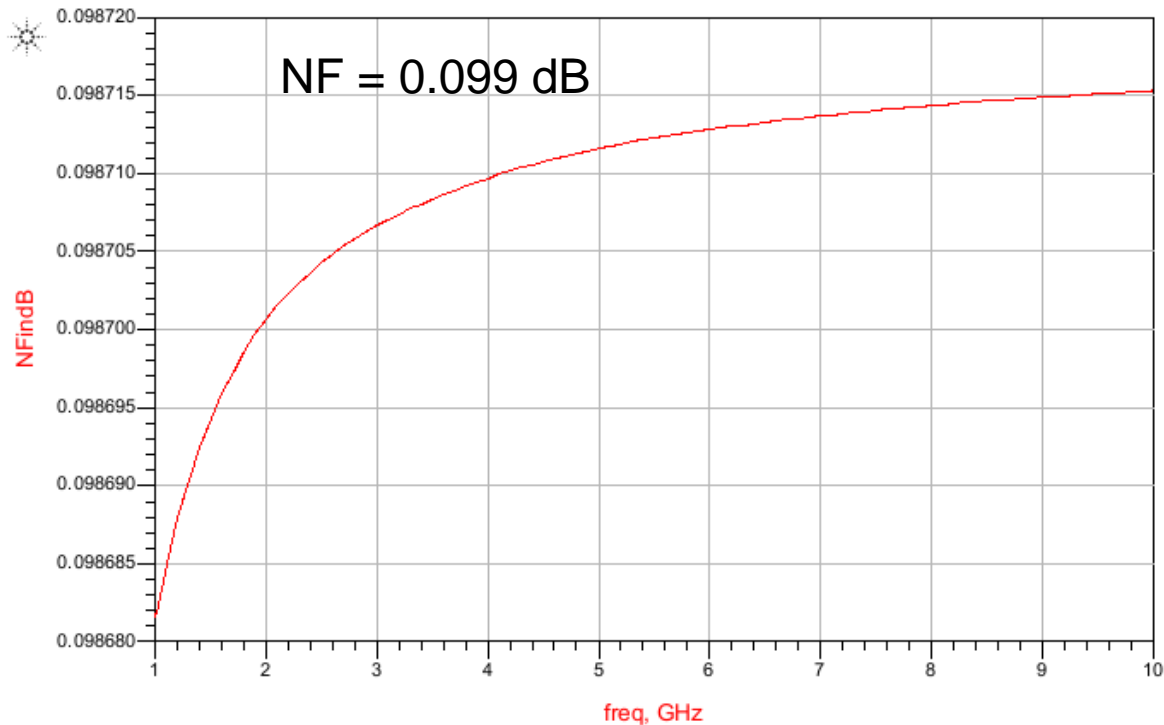Eqn $\text{NFindB} = 10 \cdot \log(\text{NF})$





Noise Modeling Example

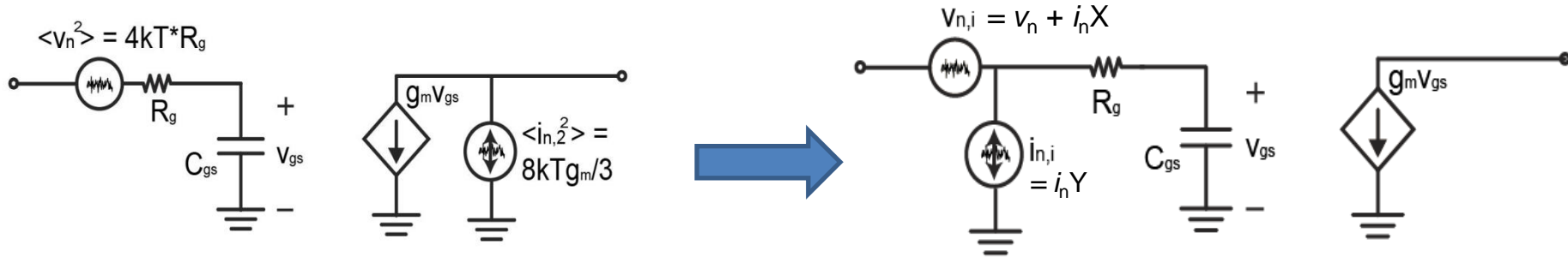


- Straightforwardly, $v_{n,i}$ and $i_{n,i}$ are partially correlated
- Test of concept: what is the v_{gs} noise when the input is short-circuited?
- NF is determined only by Z_s
- Z_s for the best NF does not achieve the best (transducer) power gain
- Recall: (transducer) power gain is determined by both Z_s and Z_L
(What is the maximum gain of this circuit?)

Noise Circle Simulation

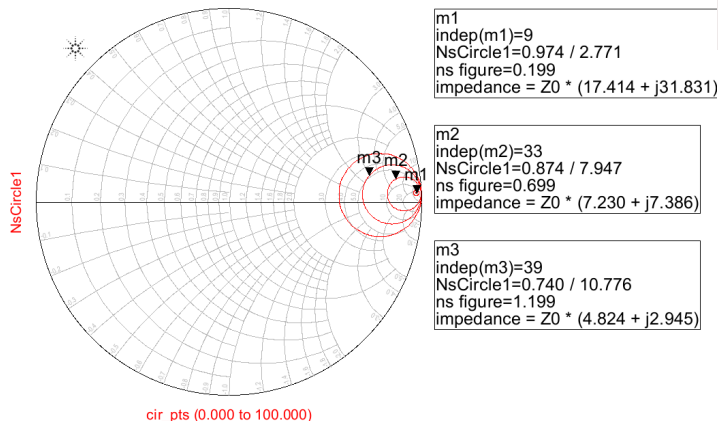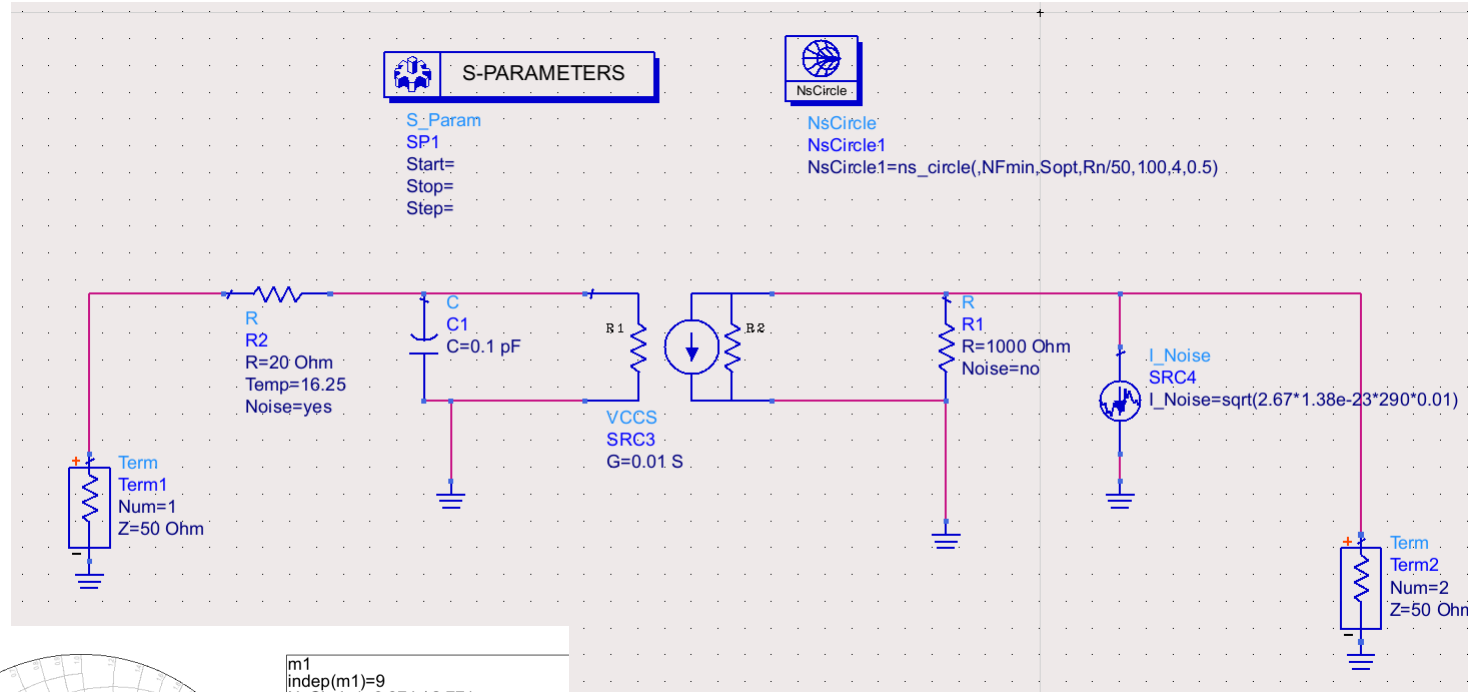We know that different source impedances (Z_s) correspond to different NF
The NF contour can be plotted versus the source impedance on the Smith Chart



freq	NFmin	Rn	Sopt
1.000 GHz	0.199	86.687	0.974 / 2.771

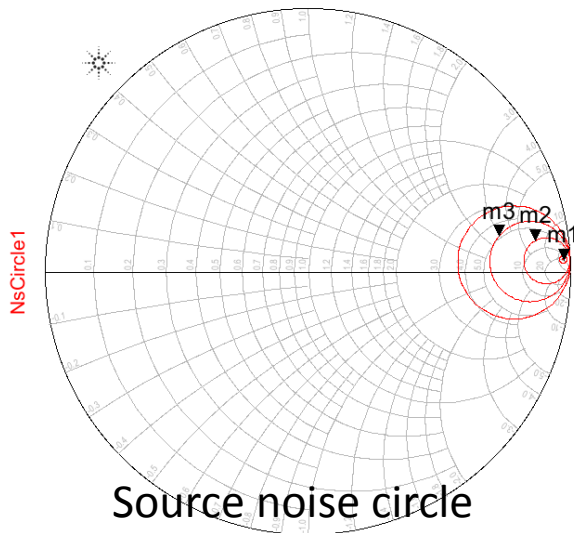


cir_pts (0.000 to 100.000)

m1
 $\text{indep}(m1)=9$
 $\text{NsCircle1}=0.974 / 2.771$
 $\text{ns figure}=0.199$
 $\text{impedance} = Z_0 * (17.414 + j31.831)$

m2
 $\text{indep}(m2)=33$
 $\text{NsCircle1}=0.874 / 7.947$
 $\text{ns figure}=0.699$
 $\text{impedance} = Z_0 * (7.230 + j7.386)$

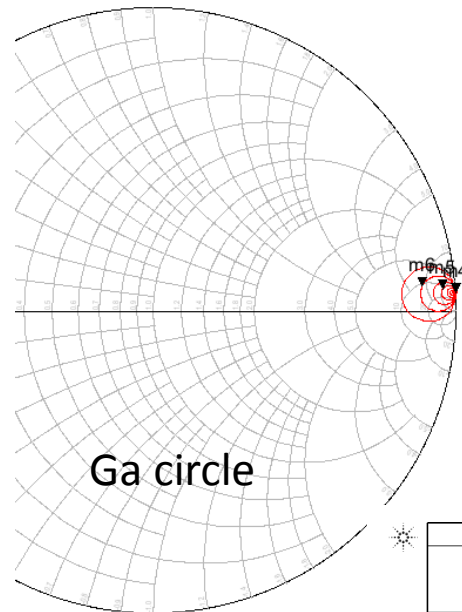m3
 $\text{indep}(m3)=39$
 $\text{NsCircle1}=0.740 / 10.776$
 $\text{ns figure}=1.199$
 $\text{impedance} = Z_0 * (4.824 + j2.945)$



cir_pts (0.000 to 51.000)

m4
 $\text{indep}(m4)=51$
 $\text{GaCircle1}=0.999 / 3.598$
 $\text{gain}=35.005$
 $\text{impedance} = Z_0 * (0.400 + j31.831)$

m5
 $\text{indep}(m5)=21$
 $\text{GaCircle1}=0.957 / 4.417$
 $\text{gain}=23.005$
 $\text{impedance} = Z_0 * (11.145 + j19.611)$

m6
 $\text{indep}(m6)=22$
 $\text{GaCircle1}=0.891 / 5.379$
 $\text{gain}=19.005$
 $\text{impedance} = Z_0 * (10.440 + j8.432)$

freq	MaxGain1
1.000 GHz	35.005

S-PARAMETERS

S_Param
 SP1
 Start=
 Stop=
 Step=



NsCircle
 NsCircle1
 $\text{NsCircle1}=\text{ns_circle}(\text{NFmin}, \text{Sopt}, \text{Rn}/50, 100, 4, 0.5)$



GaCircle
 GaCircle1
 $\text{GaCircle1}=\text{ga_circle}(\text{S}, 51, 10, 2)$




MaxGain
 MaxGain1
 $\text{MaxGain1}=\text{max_gain}(\text{S})$

From the Noise and Ga circles:
 Design with $Z_s = 500$


Can achieve :

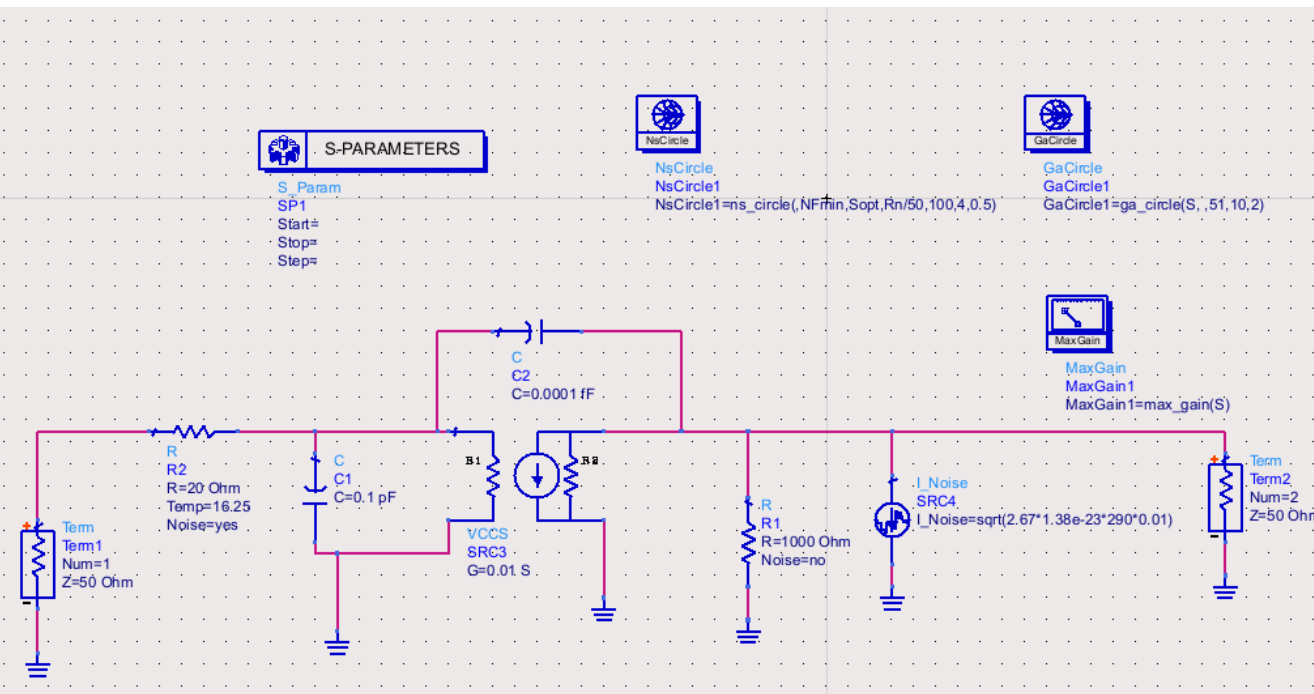0.7dB NF (not the best)
 17 dB transducer power gain
 (not the best)



S-PARAMETERS


S-Param
SP1
Start=
Stop=
Step=

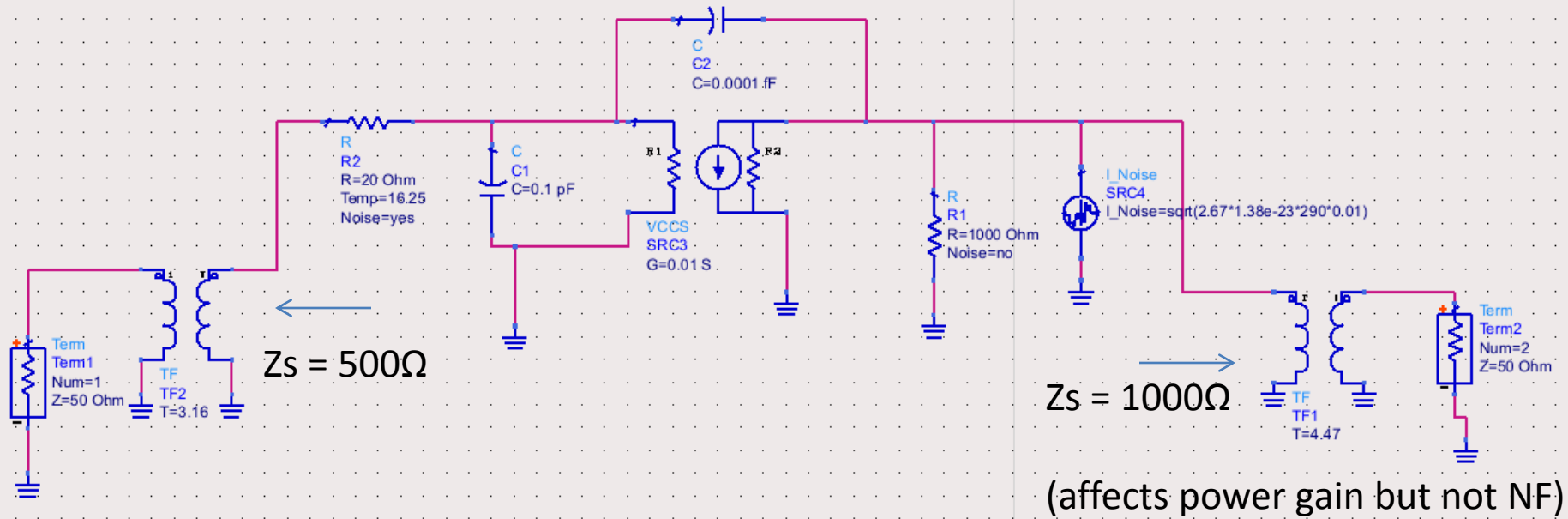

freq	nf(2)	dB(S(2,1))	dB(S(1,1))	dB(S(2,2))
1.000 GHz	0.748	16.544	-0.062	-66.425

very bad input matching


HW6: System Pole Location

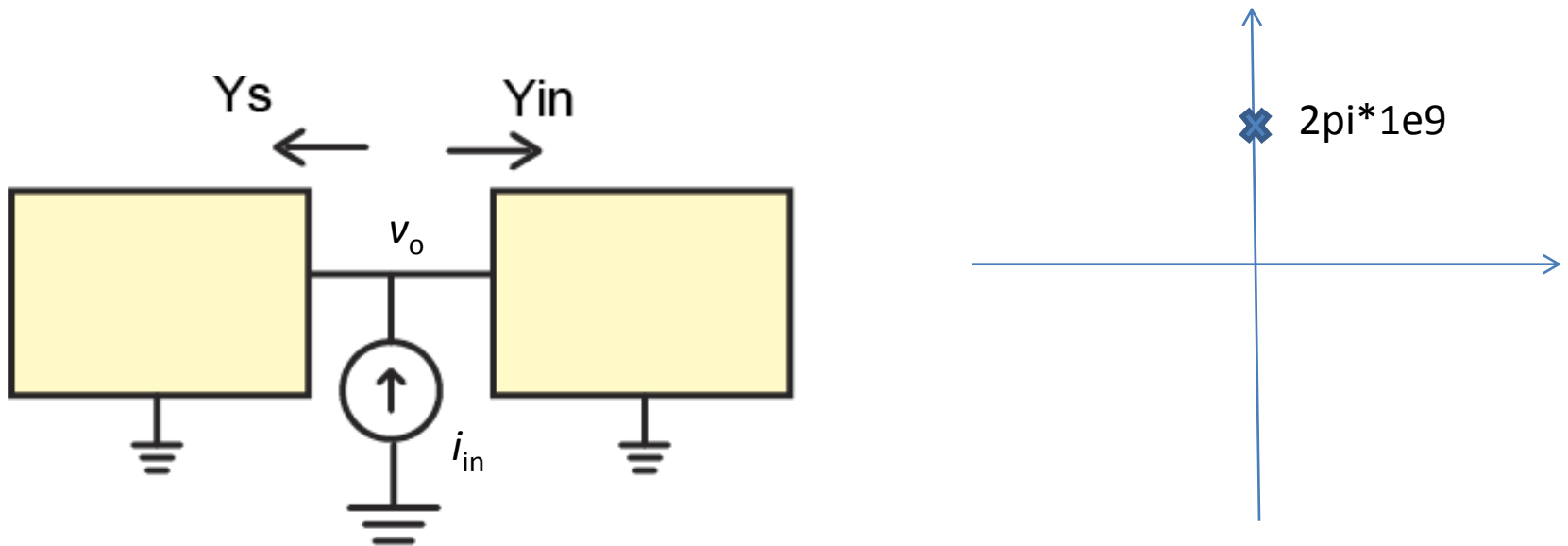

System pole at $s = j2\pi \cdot 1 \text{ GHz}$ means v_o/i_{in} is infinite if the current is at 1 GHz.

$$v_o/i_{in} \text{ at } 1 \text{ GHz} = (1/Y_{in}) + (1/Y_s) = \text{infinite} \Rightarrow Y_{in} + Y_s = 0 \text{ at } 1 \text{ GHz}$$

Voltage Gain and Transducer Power Gain

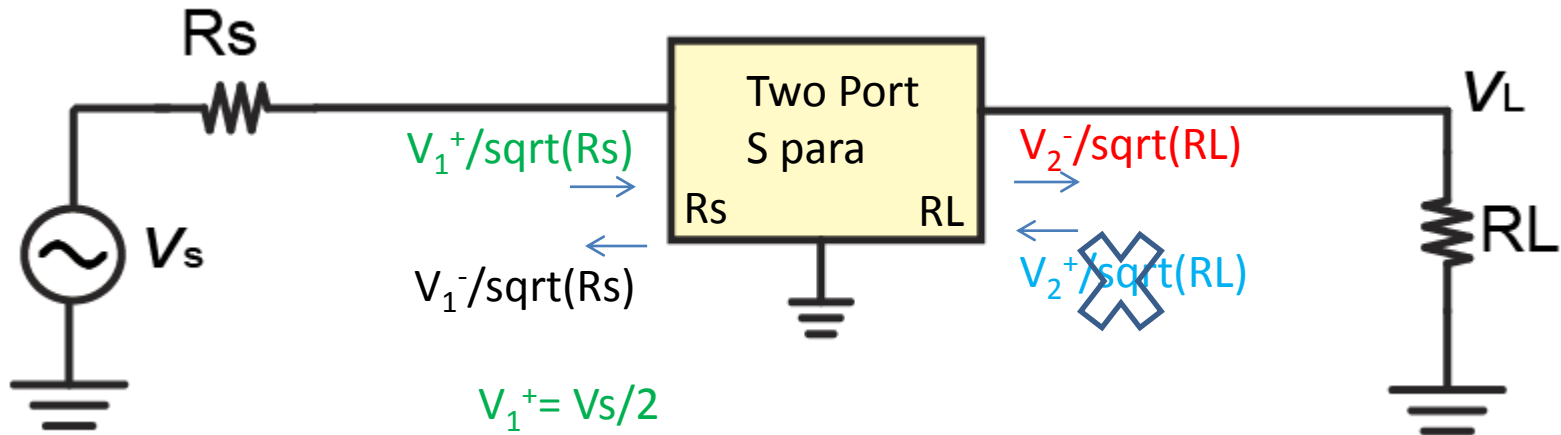

Voltage Gain
 $= V_L / V_s$

(Transducer) Power Gain

$$= 2P_L / 2P_{avs}$$

$$= (|V_L|^2 / 2R_L) / (|V_s|^2 / 8R_s)$$


$$= |V_L / V_s|^2 \times (4R_s / R_L)$$

$$= |S_{21}|^2 \text{ (source reference = } R_s \text{ load reference = } R_L)$$

$$\Rightarrow \text{Voltage gain is not } |S_{21}|$$

Maximum Transducer Power Gain and Stability

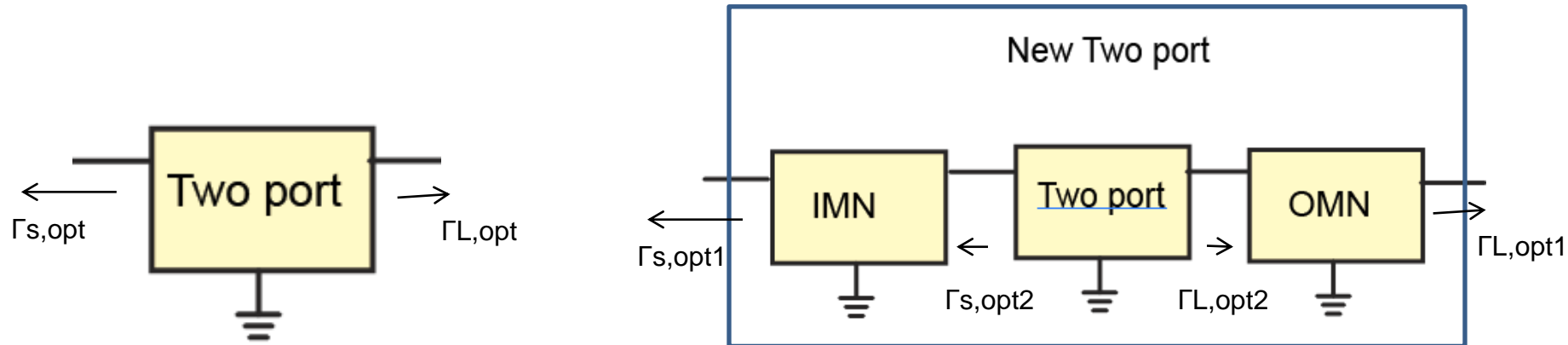When you add lossless input and output matching networks to a two port, the **maximum gain** and **k** of the new two port do not change!



k does not change

$$G_{max} = \frac{Y_{21}}{Y_{12}} (K - \sqrt{K^2 - 1})$$

Need to prove Y_{21}/Y_{12} of a two port does not change
when adding series or parallel inductor/capacitor
(easy)