

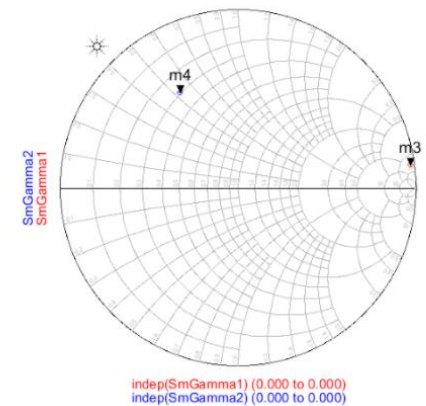
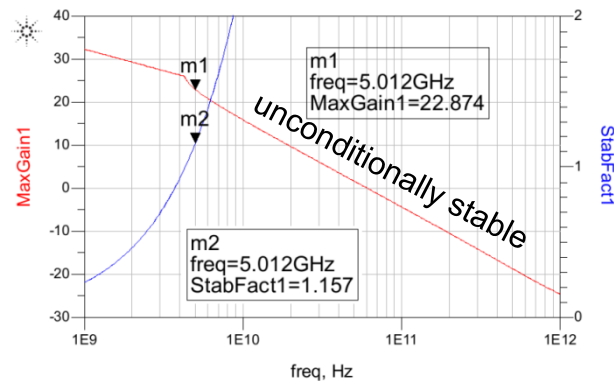


Today's Agenda (Oct. 11)

- Hw6: Design of a 5-GHz Microwave Amplifier
- Noise Figure Review (Cascade Circuits)
- ADS Examples for Noise Simulation in Linear Ckt

Design of a Microw. Amplifier

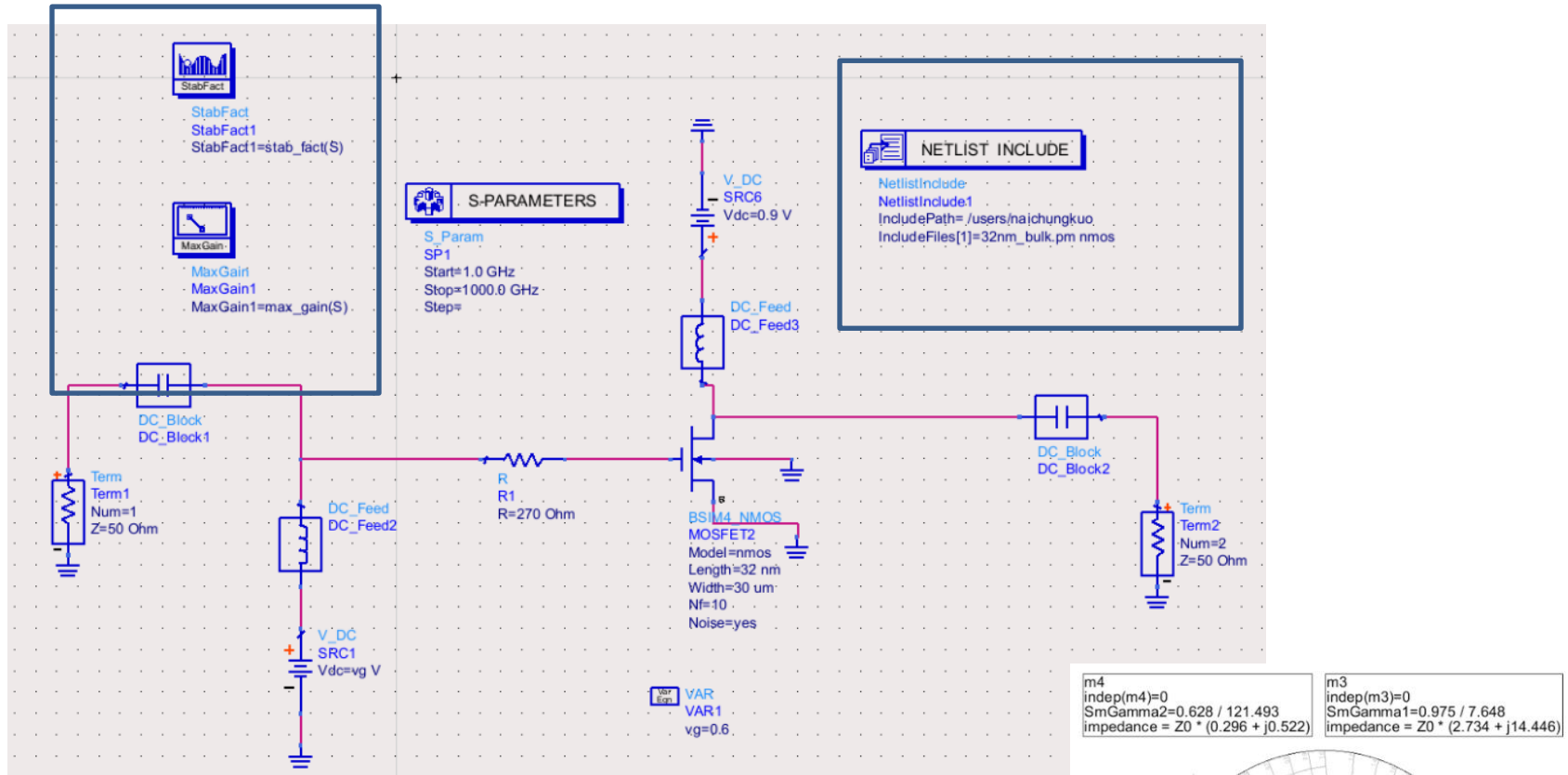

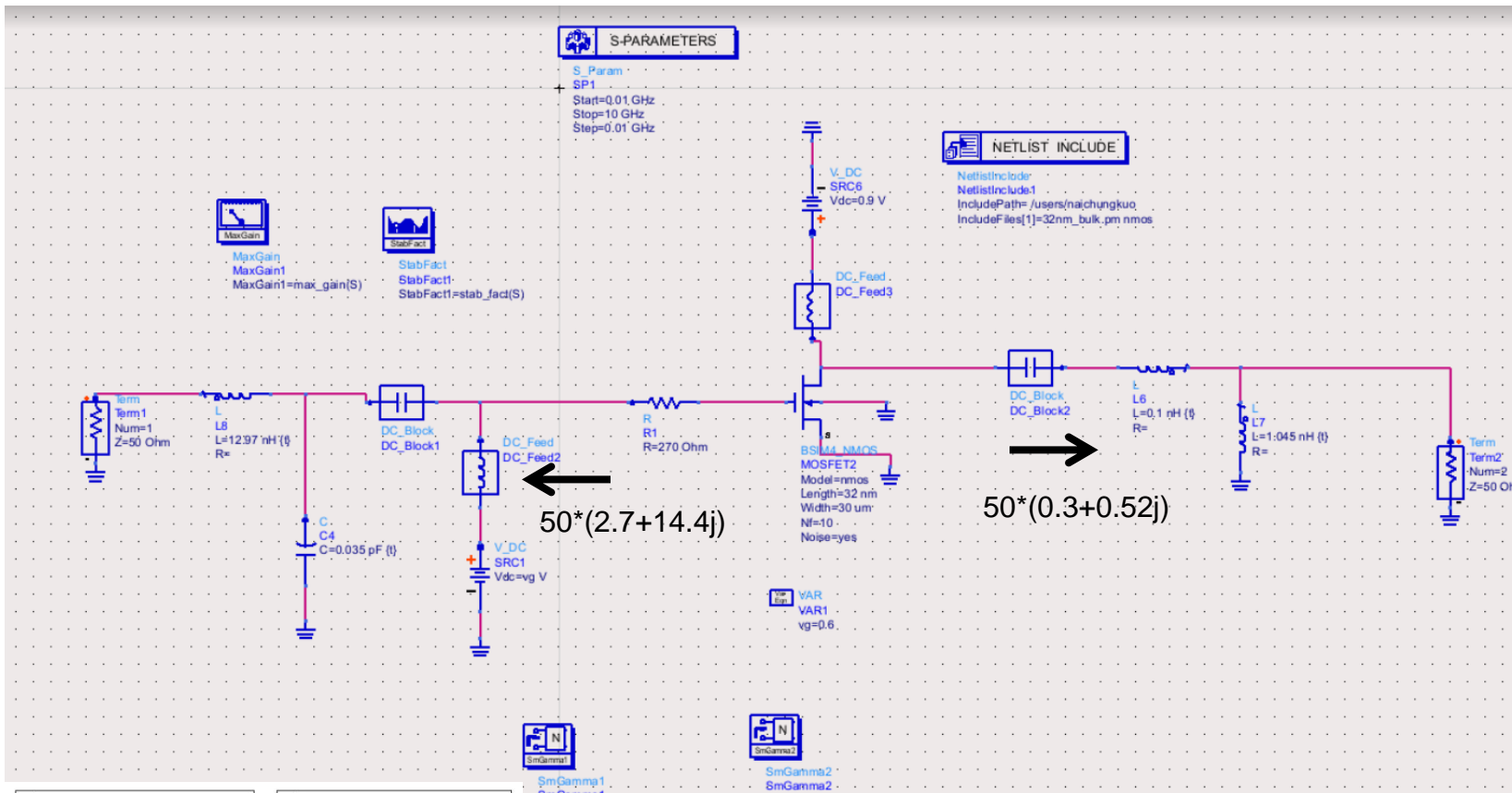


m4
indep(m4)=0
SmGamma2=0.010 / 60.399
impedance = Z0 * (1.009 + j0.017)

m3
indep(m3)=0
SmGamma1=0.086 / -169.352
impedance = Z0 * (0.843 - j0.027)

SmGamma1
SmGamma1
SmGamma1=sm_gamma1(S)


SmGamma2
SmGamma2
SmGamma2=sm_gamma2(S)

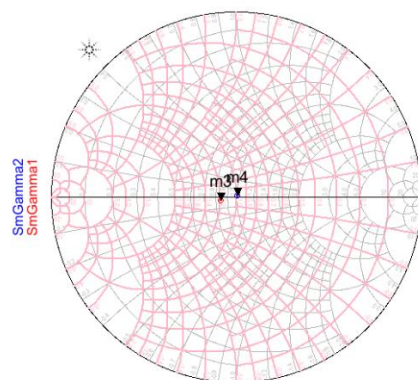

indep(SmGamma1) (0.000 to 0.000)
indep(SmGamma2) (0.000 to 0.000)

m5
freq=5.000GHz
dB(S(2,1))=22.876

m6
freq=5.000GHz
StabFact1=1.155

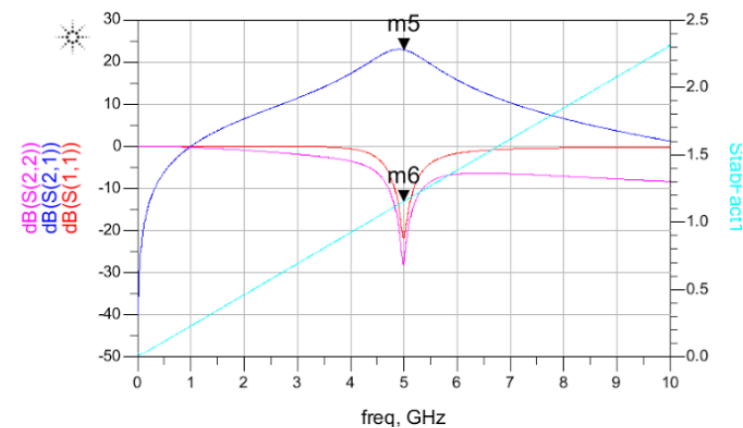

S-PARAMETERS

S: Param
SP1
Start=0.01 GHz
Stop=10 GHz
Step=0.01 GHz

NETLIST: INCLUDE:


NetlistInclude
NetlistInclude1
IncludePath=/users/haichungkuo
IncludeFiles[1]=32nm_bulk.pm nmos



Max Gain
Max Gain1
Max Gain1=max_gain(S)



StabFact
StabFact1
StabFact1=stab_fac(S)

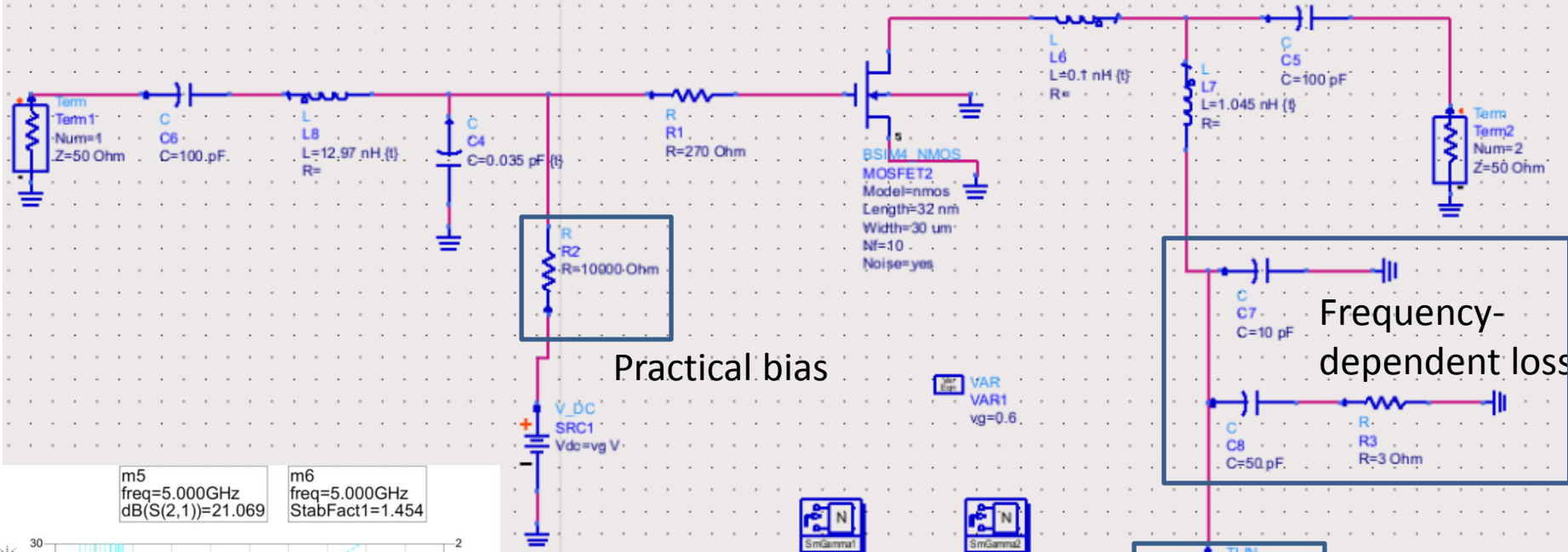


Practical bias

Frequency-dependent loss

m5
freq=5.000GHz
dB(S(2,1))=21.069

m6
freq=5.000GHz
StabFact1=1.454

m7
freq=1.910GHz
StabFact1=1.650

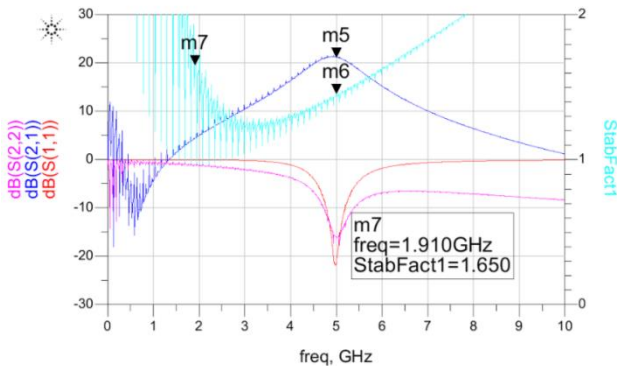


SmGamma1
SmGamma1
SmGamma1=sm_gamma1(S)



SmGamma2
SmGamma2
SmGamma2=sm_gamma2(S)


Outside environment
(not controllable)

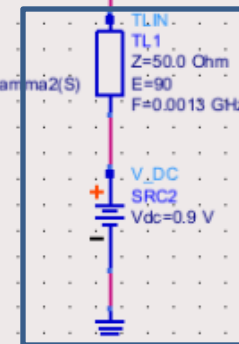

Two-Port Noise Figure

A **noise figure** must associate with a **reference impedance**


Reference impedance = 50 Ω in most cases

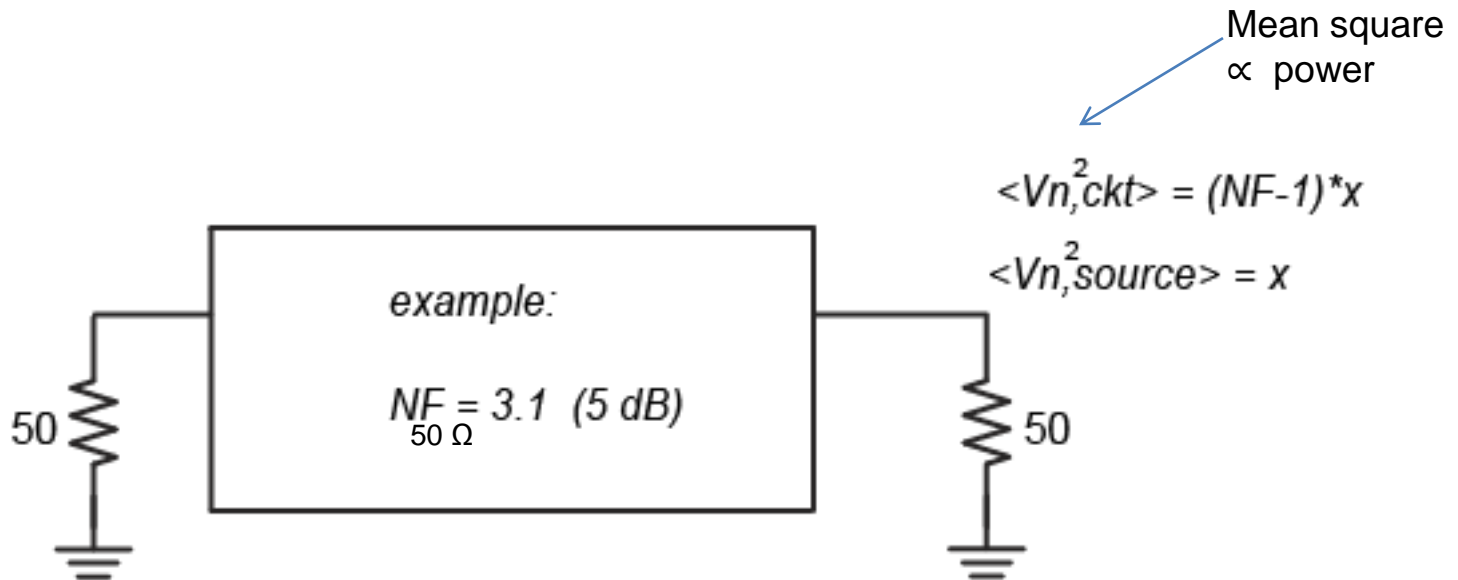

NF can change if the reference impedance change!
(maybe only for midterm purpose?)

Cascade Circuit Noise Figure

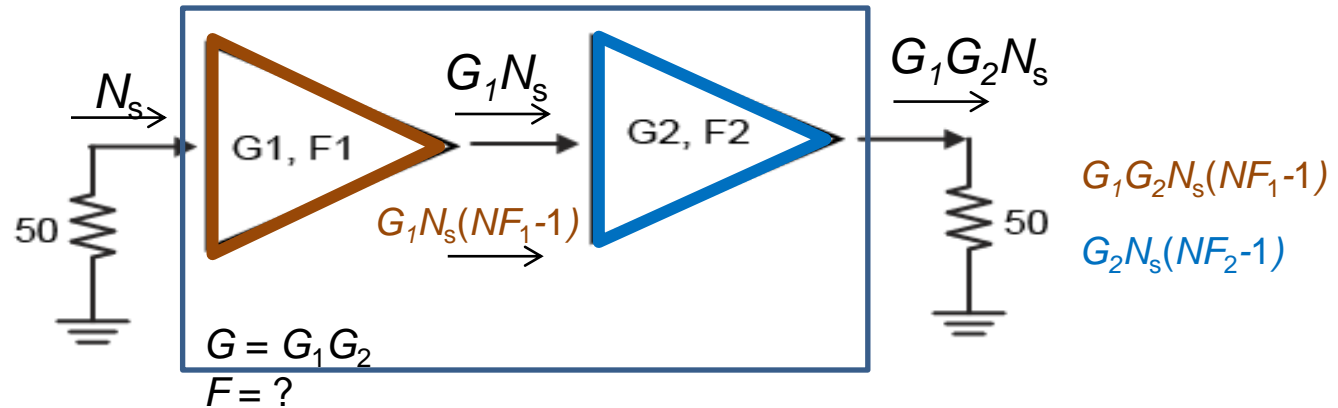Assume the blocks are impedance matched properly




Refer to Output (usually a better method)

$$\begin{aligned}
 F &= P_{o, \text{ noise}} / P_{o, \text{ noise from source}} \\
 &= [G_1 G_2 N_s + G_1 G_2 N_s (F_1 - 1) + G_2 N_s (F_2 - 1)] / [G_1 G_2 N_s] \\
 &= 1 + F_1 - 1 + (F_2 - 1) / G_1
 \end{aligned}$$

Refer to Input

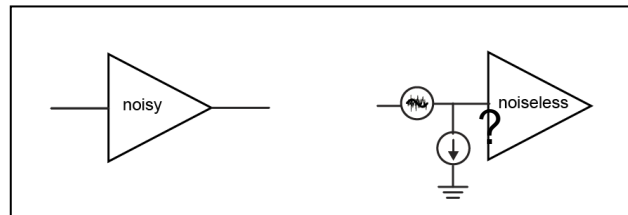
(more difficult in most cases,
misleading if you over-interpret it)



Cascade Circuit Noise Figure

Two unilateral amplifiers

Amp1 Amp2

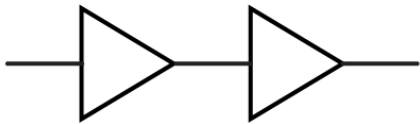

Amp1: $Z_{in,1} = 10 \Omega$, $Z_{out,1} = 70 \Omega$, $A_{v1} = 10$, $NF_{1,50\Omega} = 5 \text{ dB}$ (3.2)

Amp2: $Z_{in,2} = 40 \Omega$, $Z_{out,2} = 100 \Omega$, $A_{v1} = 20$, $NF_{2,50\Omega} = 10 \text{ dB}$ (10)


What is the noise figure of the cascade amplifier?

Amplifier 1: Power Gain (S_{21}) = 1.93 = 2.9 dB

Amplifier 2: Power Gain (S_{21}) = 35.1 = 15.4 dB

Is the total noise figure $F = 3.2 + (10-1)/1.93 = 7.86 = \mathbf{9 \text{ dB}}$???

Cascade Circuit Noise Figure

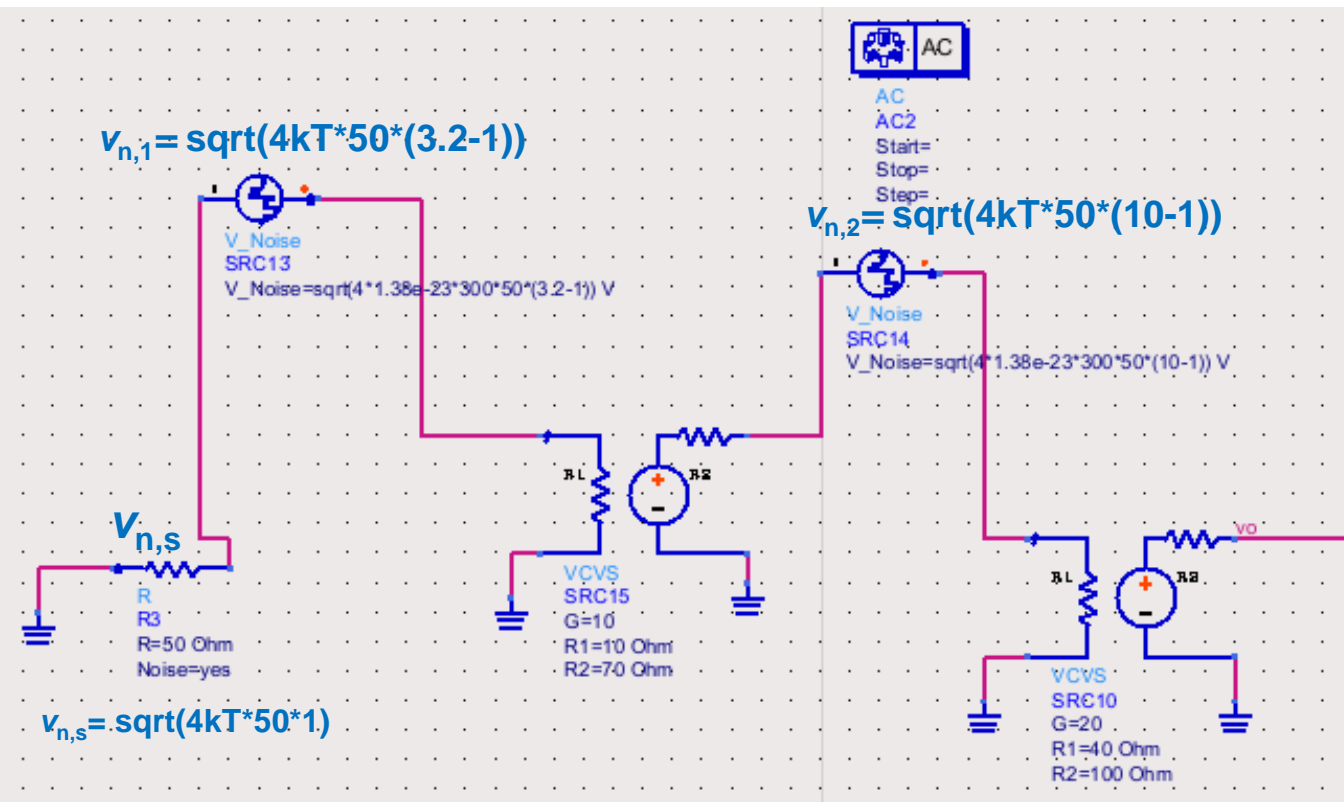

$NF = 8.1 dB$

Calculation

$V_{o,noise} =$

$$\begin{aligned}
 & V_{n,s} \cdot (10/60) \cdot 10 \cdot (40/110) \cdot 20 \cdot (50/150) \\
 & + V_{n,1} \cdot (10/60) \cdot 10 \cdot (40/110) \cdot 20 \cdot (50/150) \\
 & + V_{n,2} \cdot (40/110) \cdot 20 \cdot (50/150) \\
 & = V_{n,s} \cdot 4.04 + V_{n,1} \cdot 4.04 + V_{n,2} \cdot 2.42
 \end{aligned}$$

$P_{output\ noise} / P_{output\ noise\ from\ source}$

$$\begin{aligned}
 & = [4.04^2 \langle V_{n,s}^2 \rangle + 4.04^2 \langle V_{n,1}^2 \rangle + 2.42^2 \langle V_{n,2}^2 \rangle] / [4.04^2 \langle V_{n,s}^2 \rangle] \\
 & = [4.04^2 \cdot 8.28e-19 + 4.04^2 \cdot 1.83e-18 + 2.42^2 \cdot 7.45e-18] / [4.04^2 \cdot 8.28e-19] \\
 & = 6.4 = 8.1 dB
 \end{aligned}$$


Cascade Circuit Noise Figure

- The above noise modeling is only one of many possibilities, and We can find different noise modeling such that


1. Amp1: $Z_{in1} = 10 \text{ ohm}$, $Z_{out1} = 70 \text{ ohm}$, $A_{v1} = 10$, $NF = 5 \text{ dB}$ (3.2)

2. Amp2: $Z_{in2} = 40 \text{ ohm}$, $Z_{out2} = 100 \text{ ohm}$, $A_{v2} = 20$, $NF = 10 \text{ dB}$ (10)

But the total noise figure is not 8.1 dB

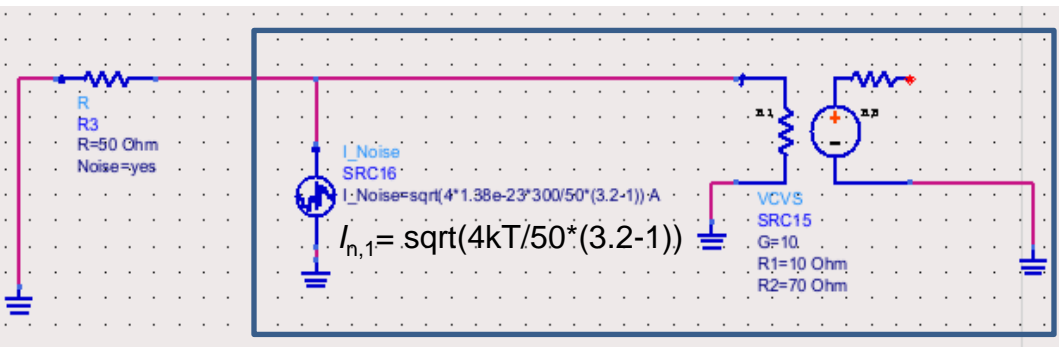

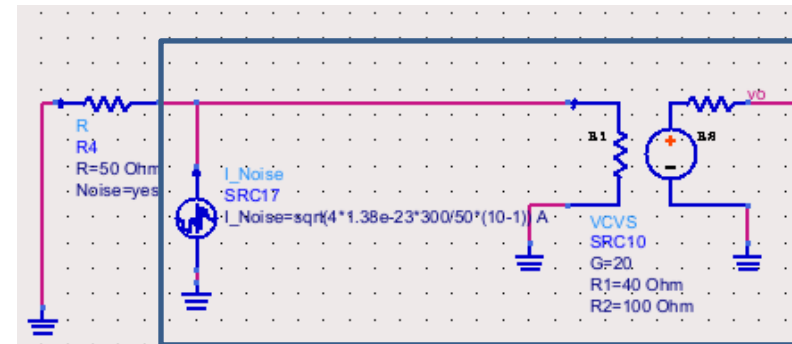
$$NF = 1 + N_{i,amp}/N_s = 3.2 = 5 \text{ dB}$$



$$NF = 1 + N_{i,amp}/N_s = 10 = 10 \text{ dB}$$

Second noise modeling

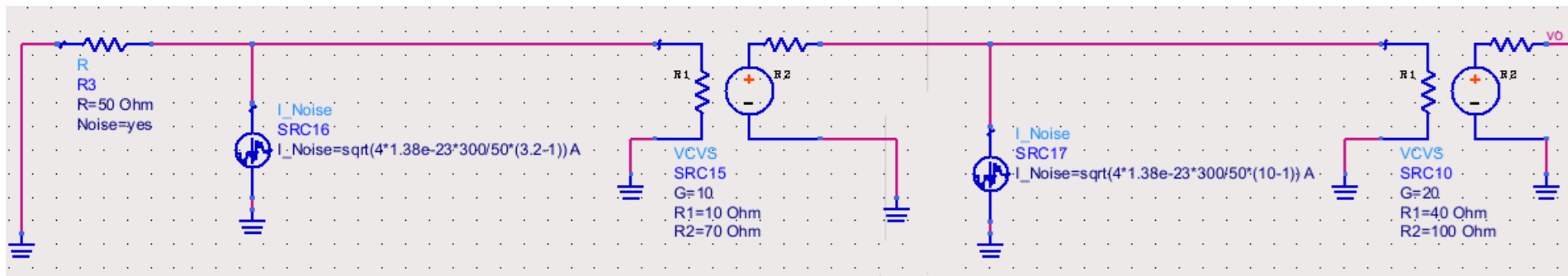

$$NF = 9.8 \text{ dB}$$

Calculation

$$V_{o,noise} =$$

$$v_{n,s} * (10/60) * 10 * (40/110) * 20 * (50/150) \\ + i_{n,1} * (10/50) * 10 * (40/110) * 20 * (50/150) \\ + i_{n,2} * (40/70) * 20 * (50/150)$$

$$= v_{n,s} * 4.04 + i_{n,1} * 202 + i_{n,2} * 170$$

$$P_{o,noise} / P_{o, noise \text{ from source}}$$


$$= [4.04^2 \langle v_{n,s}^2 \rangle + 208^2 \langle i_{n,1}^2 \rangle + 196^2 \langle i_{n,2}^2 \rangle] / [4.04^2 \langle v_{n,s}^2 \rangle]$$

$$= [4.04^2 * 8.28e-19 + 208^2 * 7.32e-22 + 196^2 * 2.98e-21] / [4.04^2 * 8.28e-19]$$

$$= 9.6 = 9.8 \text{ dB}$$


Noise - AC Simulation

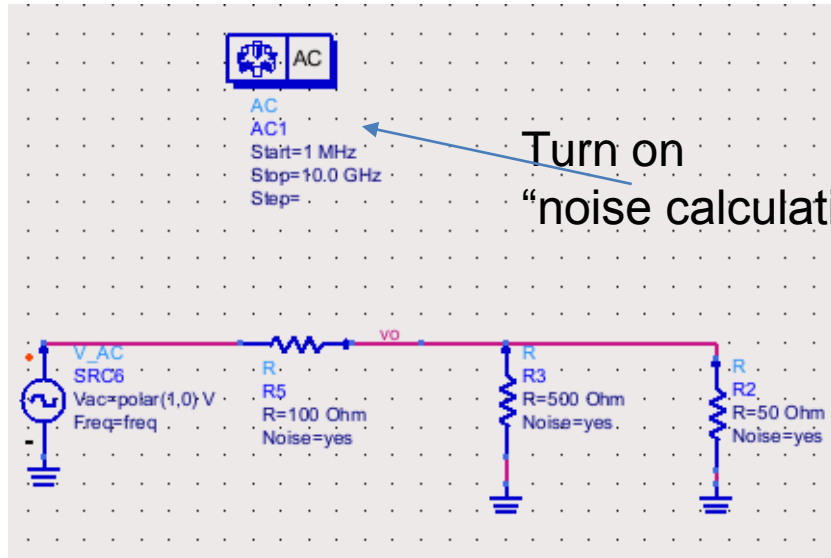Small-signal calculation with noise sources




index	name	vnc
freq=1.000 MHz		
0	_total	717.3 pV
1	R2	567.1 pV
2	R5	401.0 pV
3	R3	179.3 pV
freq=1.259 MHz		
0	_total	717.3 pV
1	R2	567.1 pV
2	R5	401.0 pV
3	R3	179.3 pV
freq=1.585 MHz		
0	_total	717.3 pV
1	R2	567.1 pV
2	R5	401.0 pV
3	R3	179.3 pV
freq=1.995 MHz		
0	_total	717.3 pV
1	R2	567.1 pV
2	R5	401.0 pV
3	R3	179.3 pV

$$717^2 = 567^2 + 410^2 + 179^2$$

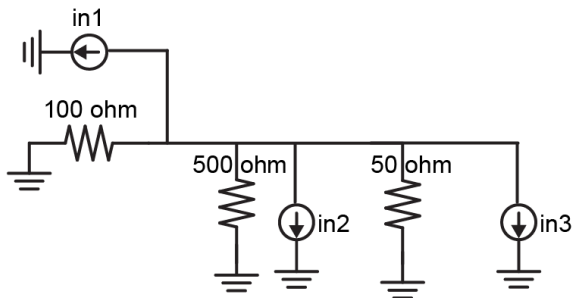

$$v_{o,\text{noise}} = 31.2(i_{n,1} + i_{n,2} + i_{n,3})$$
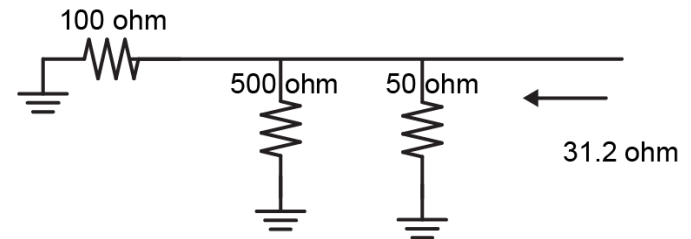
$$\sqrt{\langle v_{o,\text{noise}}^2 \rangle} = 31.2 \cdot \sqrt{\langle i_{n,1}^2 \rangle + \langle i_{n,2}^2 \rangle + \langle i_{n,3}^2 \rangle} = 718 \text{ pV}$$



$$\sqrt{\langle v_{o,\text{noise}}^2 \rangle} = \sqrt{4kT \cdot 31.2} = 718 \text{ pV}$$