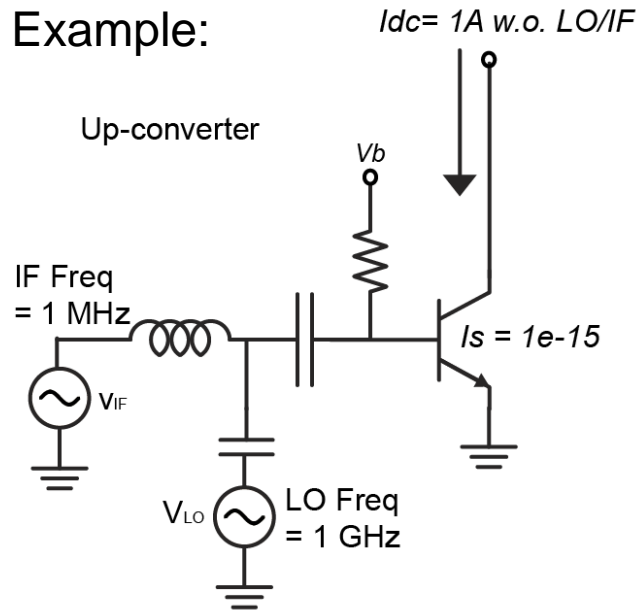


Mixer Analysis and Simulation Examples

Nov. 15 2017

Simple Example (1/3)

Example:



Small-signal distortion power series not applicable

$$i_{out} = I_{c0}/V_T * v_{in} + I_{c0}/(2V_T^2) * v_{in}^2 + I_{c0}/(6V_T^3) * v_{in}^3$$



Restart from the large-signal equation

$$I_c = I_s \exp\{ [V_b + V_{LO} \cos(f_{LO}t) + v_{IF} \cos(f_{IF}t)] / V_T \}$$

$$= I_{c0} \times \exp[V_{LO} \cos(f_{LO}t) / V_T] \times \exp[v_{IF} \cos(f_{IF}t) / V_T]$$

1A

Cannot use power series

Use power series

if $V_{LO} = 10V_T$



$$\exp[V_{LO}/V_T \times \cos(f_{LO}t)] \approx dc \times [1 + 1.9\cos(f_{LO}t) + 1.6\cos(2f_{LO}t) + \dots]$$

$$\exp[v_{IF} \cos(f_{IF}t) / V_T] \approx 1 + v_{IF} \cos(f_{IF}t) / V_T + v_{IF}^2 \cos^2(f_{IF}t) / 2V_T^2 + v_{IF}^3 \cos^3(f_{IF}t) / 6V_T^3$$

1. Voltage-to-current conversion gain: $[I_{c0} \times v_{IF} / V_T \times dc \times 1.9 / 2] / v_{IF} = [I_{c0} / V_T \times dc \times 1.9 / 2]$
2. Mixer IIP3 = $\sqrt{(4a_1)/(3a_3)} = \sqrt{(4 \times 1/V_T)/(3 \times 1/6V_T^3)} = 2.8V_T$
3. Mixer IP1dB = $\sqrt{|4a_1|/|3a_3| \times 0.11} = 0.33 \times 2.8V_T$
4. LO to RF leakage: $(I_{c0} \times dc \times 1.9) / (10V_T)$


Simple Example (2/3)
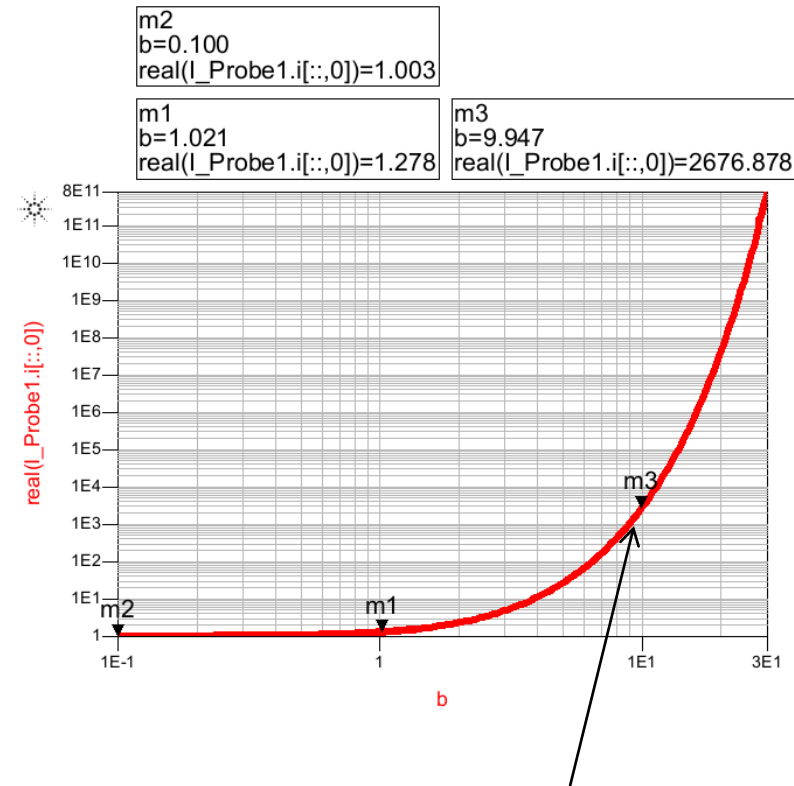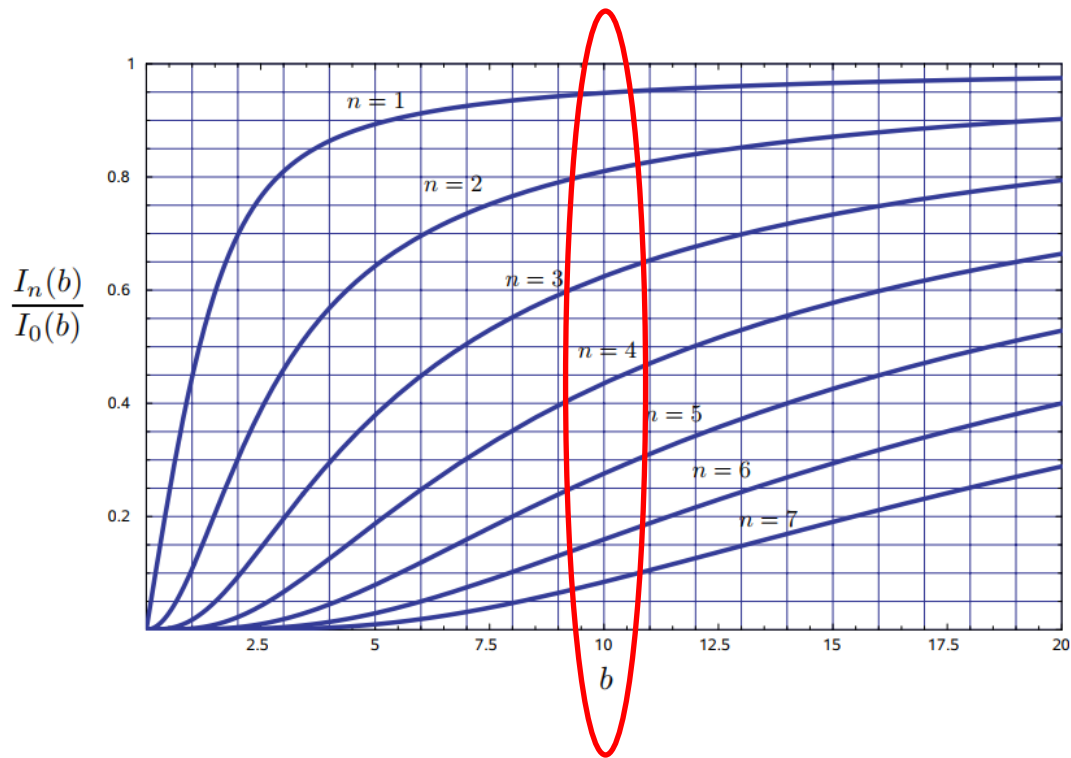
$$e^{b \cos \omega t} = I_0(b) + 2I_1(b) \cos \omega t + 2I_2(b) \cos 2\omega t + \dots$$




The dc current explodes when $V_{LO} = 10V_T$



Simple Example (3/3)

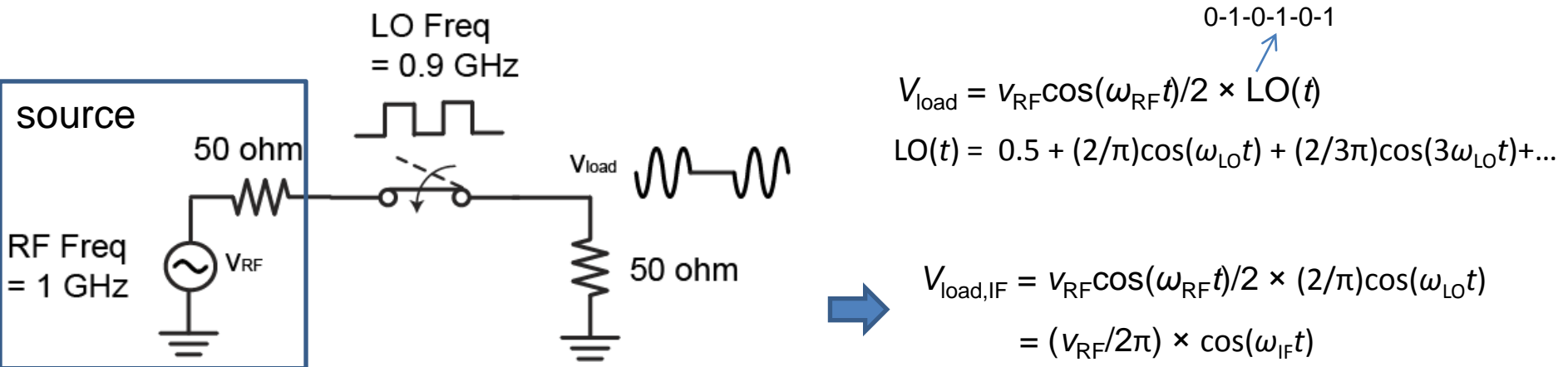


Easy Example

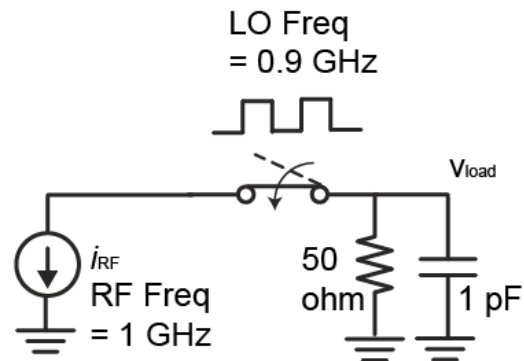

Difficult Example

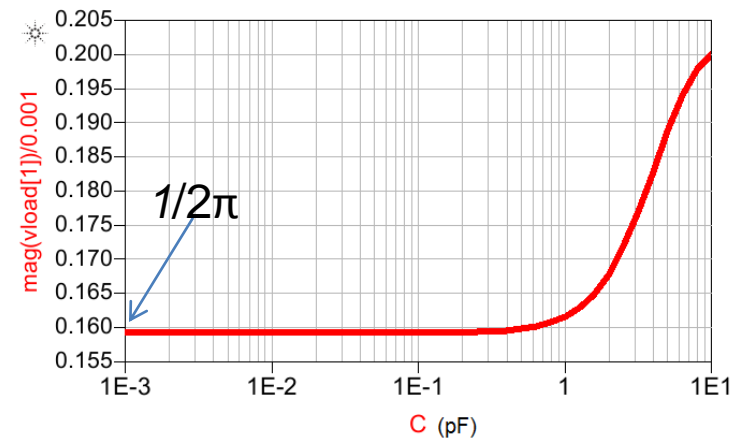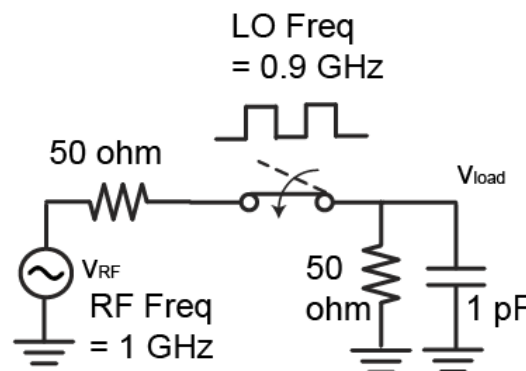

Advanced Example: Analysis

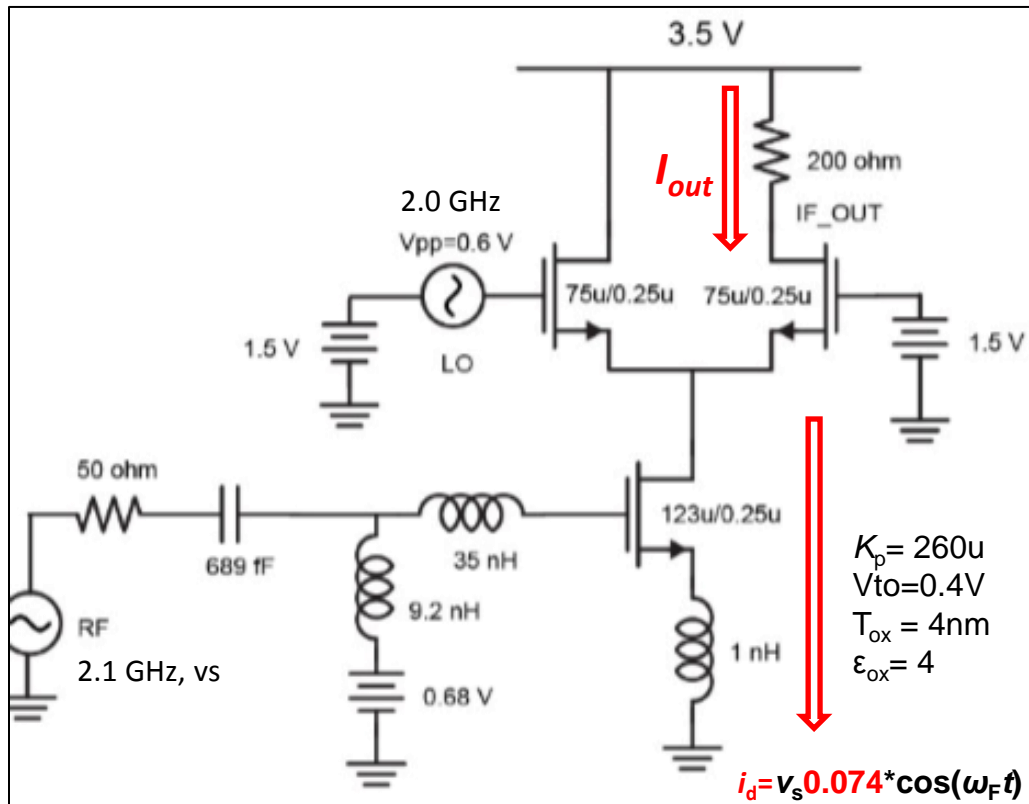

$$I_d = 0.5 \cdot K_p \cdot W/L \cdot (V_{gs} - V_T)^2 = 5 \text{ mA}$$

$$g_m = 2I_d/V_{ov} = 36 \text{ mS}$$

$$G_m = 0.074$$

$$K = 0.5 \cdot 260\mu \cdot 75/0.25 = 0.039$$

$$i_D = K (v_{GS} - V_t)^2$$

$$i_{D1,2} = \frac{I}{2} \pm \sqrt{2KI} \left(\frac{v_{id}}{2} \right) \sqrt{1 - \frac{(v_{id}/2)^2}{I/2K}}$$

$$I = 5 \text{ mA} + v_s \cdot 0.074 \cdot \cos(\omega_{RF} t)$$

$$v_{id} = 0.3 \cos(\omega_{LO} t)$$

$$I_{out} \sim I/2 + \sqrt{2KI} \cdot v_{id}/2$$

$$\sim I/2 + \sqrt{2KI_{dc}} \cdot (1 + I_{ac}/2I_{dc}) \cdot v_{id}/2$$

$$i_{IF} \sim \sqrt{2KI_{dc}} \cdot v_s \cdot 0.074/2I_{dc} \cdot 0.3/2/2 = 0.011 v_s$$

$$v_{IF} \sim i_{IF} \cdot 200 = 2.2 v_s$$



$$(\text{conversion voltage gain} = 2.2)$$

$$\text{RF-to-IF leakage: } v_{out,RF} = v_s \cdot 0.074/2 \cdot 200 = 7.4 v_s$$


$$\text{LO-to-IF leakage: } v_{out,LO} = \sqrt{2KI_{dc}} \cdot (1) \cdot 0.3/2 \cdot 200 = 0.6V$$

Advanced Example: Sim (1/4)



CS current
Load Current

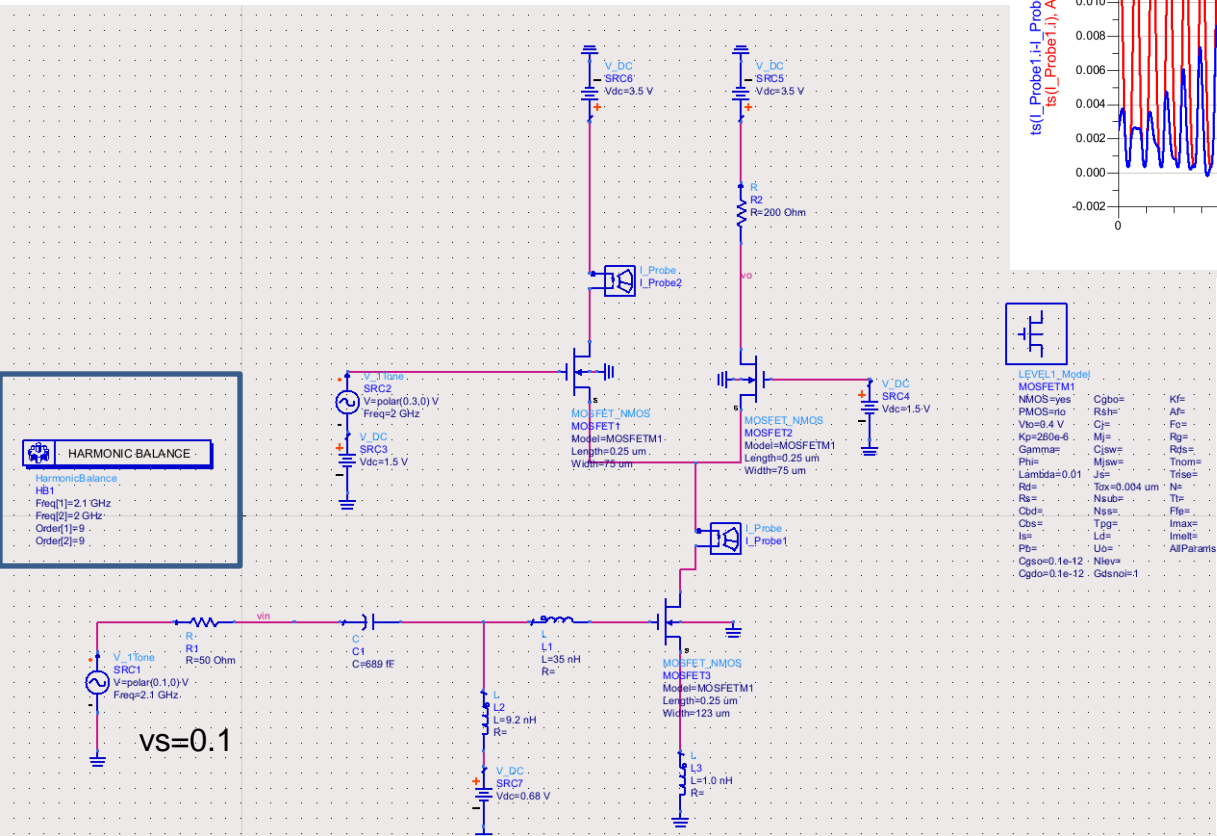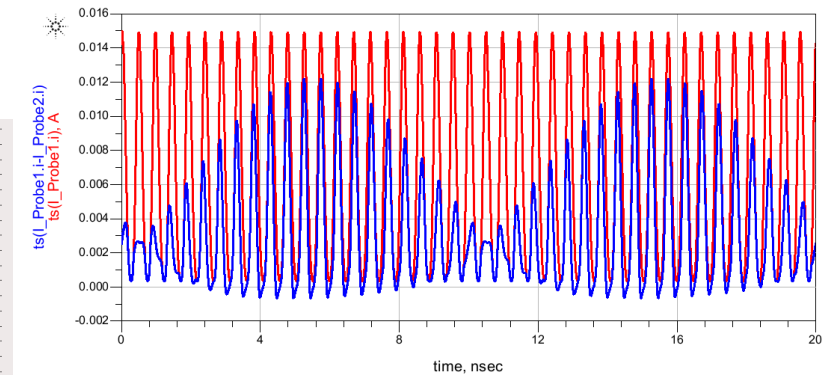

m2	m3	m4
freq=100.0MHz	freq=2.000GHz	freq=2.100GHz
mag(vo)=0.240	mag(vo)=0.511	mag(vo)=0.725

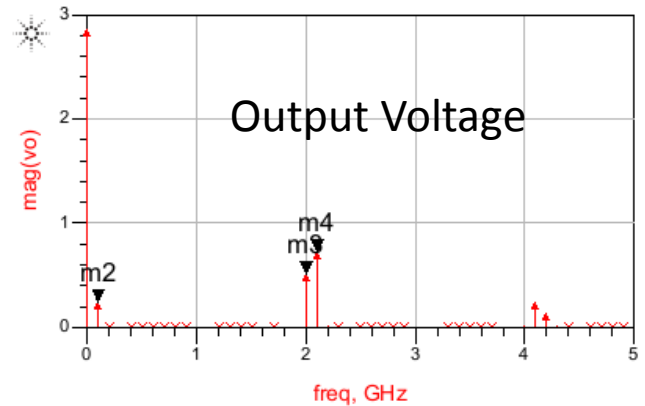

Advanced Example: Sim (2/4)

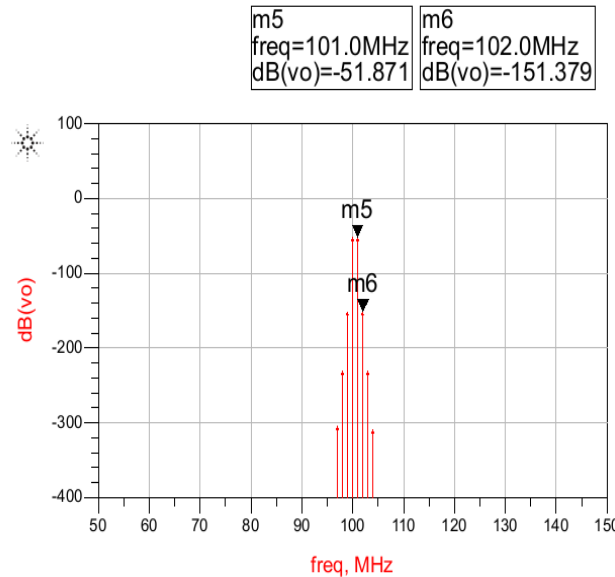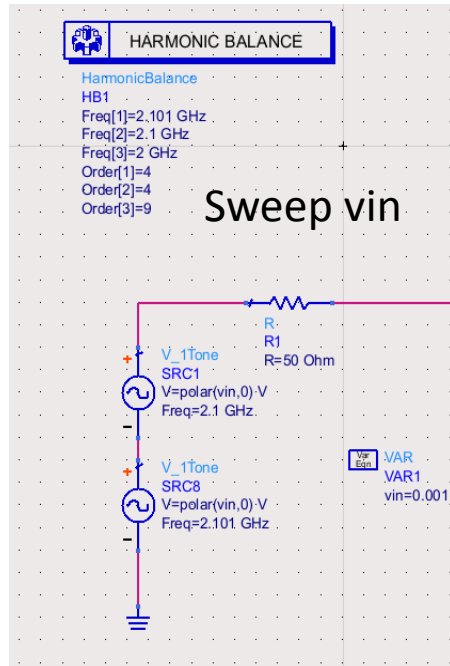


freq	dB(vo)
0.0000 Hz	9.529
1000. kHz	-91.540
2.000 MHz	-218.831
3.000 MHz	-312.639
4.000 MHz	-331.582
97.00 MHz	-304.315
98.00 MHz	-231.098
IM3 99.00 MHz	-151.375
Fund. 100.0 MHz	-51.868
101.0 MHz	-51.871
IM3 102.0 MHz	-151.379
103.0 MHz	-231.102
104.0 MHz	-308.812
198.0 MHz	-307.268
199.0 MHz	-233.305
200.0 MHz	-155.287

m7
indep(m7)=-60.000
plot_vs(dB(vo[8]), db(vin))=-51.868

m8
indep(m8)=-50.153
plot_vs(dB(vo[8]), db(vin))=-42.018

m9
indep(m9)=-60.000
plot_vs(dB(vo[7]), db(vin))=-151.375


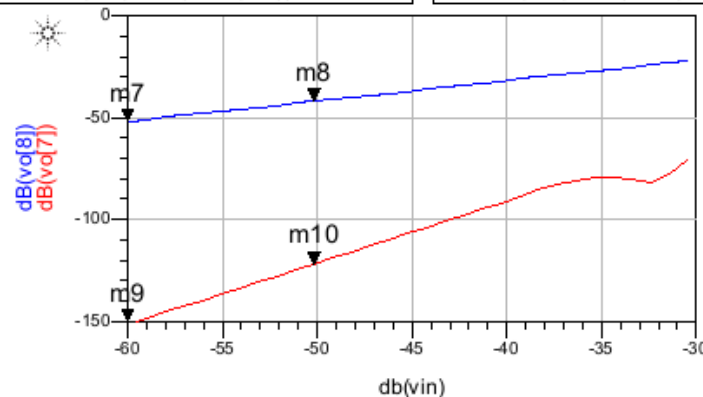
m10
indep(m10)=-50.153
plot_vs(dB(vo[7]), db(vin))=-121.794



IIP3 = -2 dBV

The third-order nonlinearity is created by the FET source degeneration !

Advanced Example: Sim (3/4)

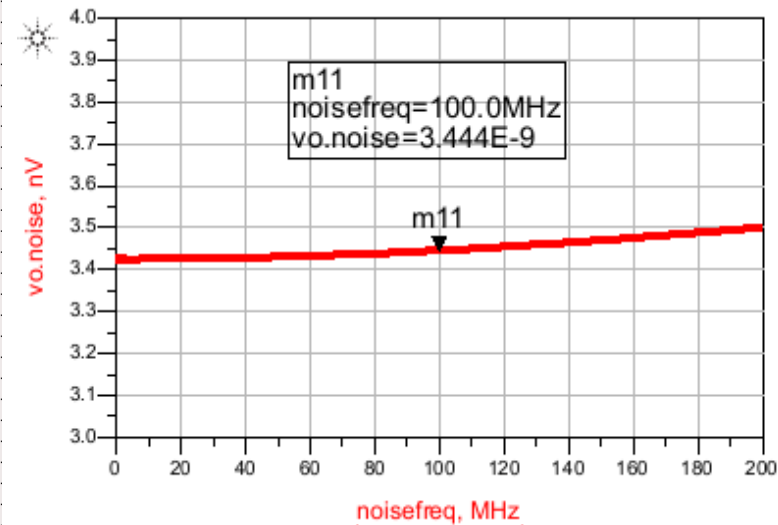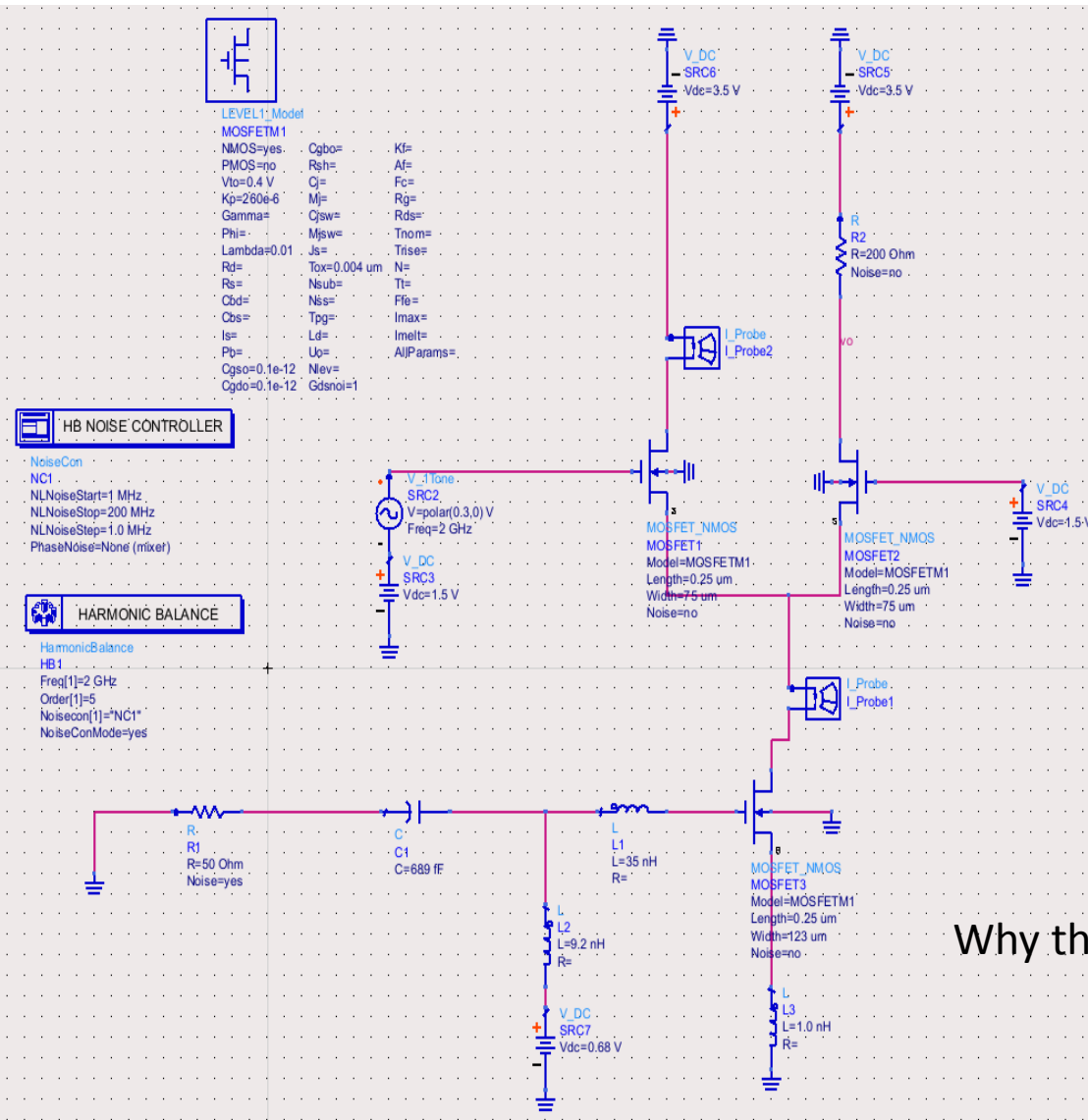


Noise contributed by Rs at 2.1 GHz:

$$v_{n,out} = \sqrt{(4kT \cdot 50)} \cdot 2.2 = 2.1 \text{ nV}$$

Why the output noise is higher than 2.1 nV ?

Advanced Example: Sim (4/4)

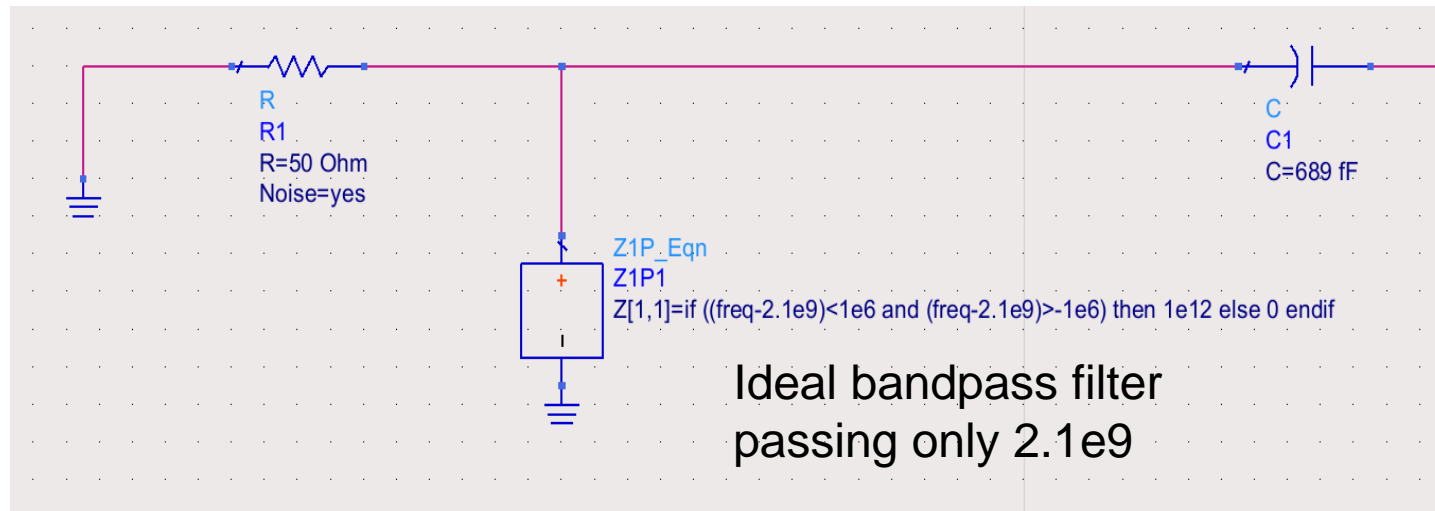

- LO Freq = 2 GHz
- Output noise @ 100 MHz contributed by source noises at many frequencies
- High-frequency noise filtered by input matching network

Freq.	Noise Contribution (nV)	Accumulated Noise
1.9 GHz	2.55e-9	2.55e-9
2.1 GHz	2.31e-9	3.44e-9
3.9 GHz	2.6e-13	~3.44e-9
4.1 GHz	3.4e-13	~3.44e-9
5.9 GHz	8.9e-12	~3.44e-9
6.1 GHz	8.2e-12	~3.44e-9