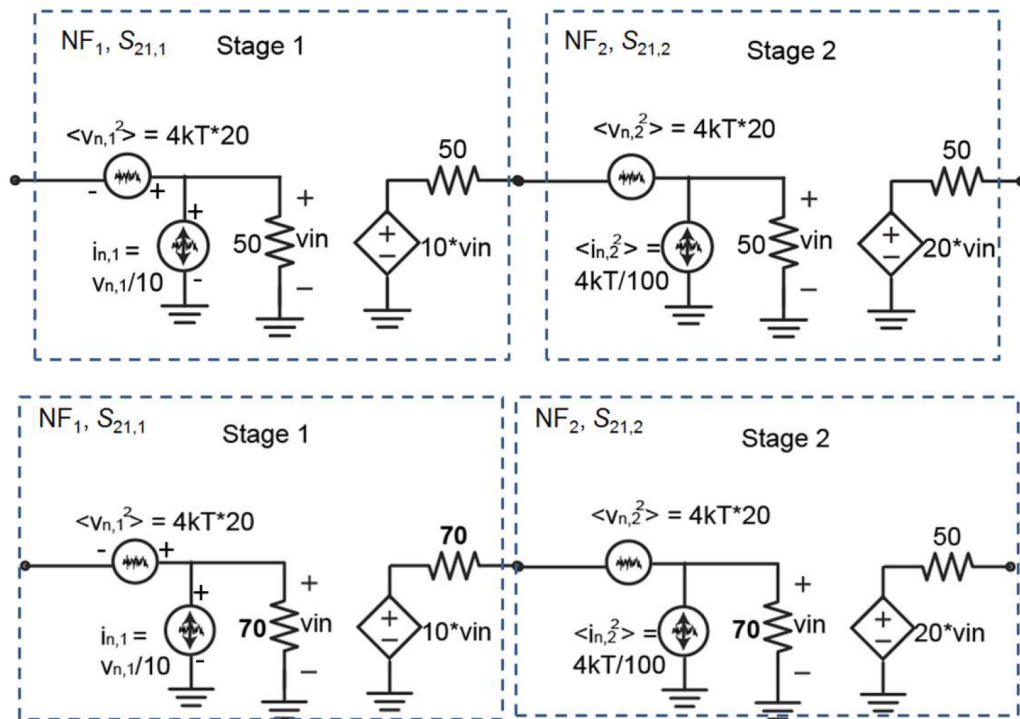


# EE142 Problem Set 7

Vighnesh Iyer

October 21, 2017

## 1 Noise Figure of Cascade Blocks and Lossy Transmission Line



- (a) For the above two cascade circuits, calculate the power gains and noise figures for each stage (i.e.  $S_{21,1}$ ,  $S_{21,2}$ ,  $NF_1$ ,  $NF_2$ ) and the two stage circuits ( $S_{21,total}$ ,  $NF_{total}$ ). The resistors are assumed to be noiseless.

### 1.a Cascade 1

For the first cascade's stage 1, we begin by input referring the noise sources and collapsing the voltage and current noise into  $\overline{v_{eq}^2}$ . From lecture:

$$\overline{v_{eq}^2} = \overline{v_n^2} + \overline{i_n^2} R_s^2$$

$$F = 1 + \frac{N_{amp,i}}{N_s} = 1 + \frac{\overline{v_{eq}^2}}{\overline{v_s^2}}$$

Assume we are calculating noise figure in a  $50\Omega$  environment,  $R_s = 50\Omega$  and  $\overline{v_s^2} = 4kTR_s$ . We assume that all noise sources represented are defined as *spot noise*.

$$F_1 = 1 + \frac{\overline{v_{eq,1}^2}}{\overline{v_s^2}} = \frac{4kT \cdot 20 + 4kT \cdot 2 \cdot 50^2}{4kT \cdot R_s}$$