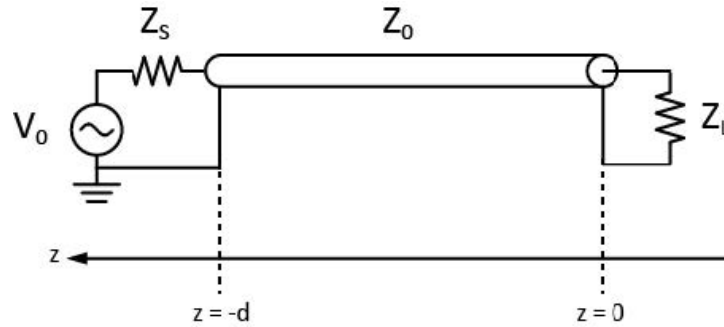


EE 142 Problem Set 3

Vighnesh Iyer

1 T-Lines at Steady State



Voltage source generates 10 GHz sine with 10V amplitude.

Tline terminated with $Z_L = 80 - 40j\Omega$, and $Z_0 = 100\Omega$. $\epsilon_{eff} = 4$ and $d = 22.5$ mm.

1. Find the reflection coefficient at the load ($z = 0$) and at the source ($z = -d$)

At the load:

$$\rho_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\rho_L = -0.0588 - 0.23539j$$

$$|\rho_L| = 0.242$$

At any point on the line, we can derive an effective generalized $\rho(z)$ which represents the ratio of the backwards and forward traveling waves at a given point on the tline.

$$V(z) = V_0^+(e^{-j\beta z} + \rho_L e^{-j\beta z})$$

$$\rho(z) = \frac{V_0^+ \rho_L e^{j\beta z}}{V_0^+ e^{-j\beta z}}$$

$$\rho(z) = \rho_L e^{2j\beta z}$$

Notice that since $\beta = 2\pi/\lambda$, $\rho(z)$ repeats every $\lambda/2$ traversed along the line back to the generator. We can find c_p and λ for this line and frequency.

$$c_p = \frac{c_0}{\sqrt{\epsilon_{eff}}} \approx 1.5e8 \text{ m/s}$$

$$\lambda = \frac{c_p}{f} = 0.015 \text{ m}$$

$$d/\lambda = 1.5 = 3 \cdot \frac{1}{2} \lambda$$

So, $\rho(z)$ at $z = -d$ is $\rho_L = 0.242$.

- Find the input impedance at the source ($z = -d$) and at $z = 18.75\text{mm}$.

The general form is:

$$Z_{in}(-l) = Z_0 \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)}$$

$$\beta = \frac{2\pi}{\lambda} = 418.879$$

$$Z_{in}(0) = Z_L = 100\Omega$$

$$Z_{in}(-18.75 \text{ mm}) = Z_{in}(\lambda + \lambda/4) = \frac{Z_0^2}{Z_L} = 100 + 50j$$

- Plot the magnitude of the voltage along the line. Find voltage maximum, minimum, and SWR.

We assume that $Z_S = Z_0$:

$$SWR = \frac{V_{max}}{V_{min}} = \frac{1 + |\rho_L|}{1 - |\rho_L|}$$


$$SWR = 1.64$$

$$V^+ = \frac{Z_0}{Z_0 + Z_S} = 5 \text{ V}$$

$$V_{max} = |V^+|(1 + |\rho_L|) = 6.2 \text{ V}$$

$$V_{min} = |V^+|(1 - |\rho_L|) = 3.8 \text{ V}$$


Plot of voltage magnitude along line:

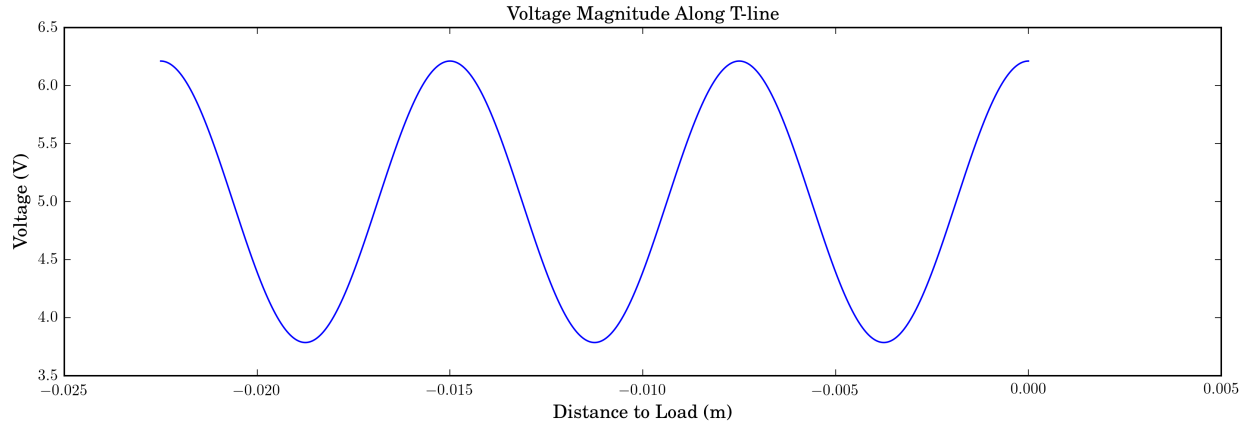

2 T-Line Modeling

We will derive an equivalent two-port circuit model for a short section of transmission line ($l \ll \lambda$) including loss.

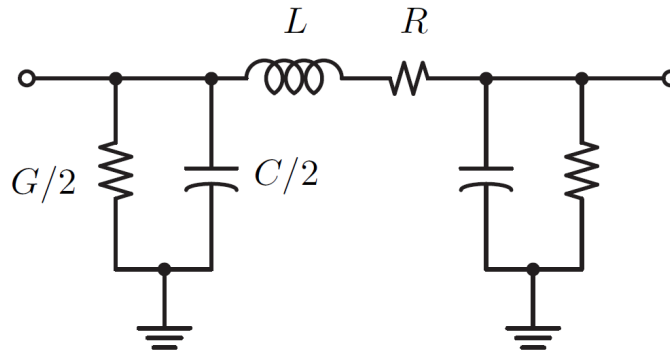1. For a "pi" equivalent circuit shown below, find the two-port Z matrix.



Let's call the current flowing *into* node 1 i_1 and the current flowing *into* node 2 i_2 . The voltage applied across node is v_1 and v_2 for node 2. We will call each section of the pi network Z_1, Z_2, Z_3 going left to right and $Z_1 = Z_3$.

$$Z_{11} = \left. \frac{v_1}{i_1} \right|_{i_2=0} = (Z_1 || (Z_2 + Z_3)) = \frac{Z_1(Z_2 + Z_3)}{Z_1 + Z_2 + Z_3}$$

$$Z_{22} = Z_{11} \text{ due to symmetry}$$

$$Z_{12} = \left. \frac{v_1}{i_2} \right|_{i_1=0} = \frac{Z_1 Z_3}{Z_1 + Z_2 + Z_3}$$

$$Z_{21} = Z_{12} \text{ due to reciprocity}$$

$$Z_1 = Z_3 = \frac{2}{2j\omega C + G}$$

$$Z_2 = R + j\omega L$$

2. Consider a section of transmission line with loss. Find the two port Z matrix. Use the transmission line impedance equation (general expression with loss).

We begin with the general form using ρ_L :

$$Z_{in}(-l) = \frac{V(-l)}{I(-l)} = Z_0 \frac{1 + \rho_L e^{-2\gamma l}}{1 - \rho_L e^{-2\gamma l}}$$

$$\rho_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$Z_{in}(-l) = Z_0 \frac{Z_L(1 + e^{-2\gamma l}) + Z_0(1 - e^{-2\gamma l})}{Z_0(1 + e^{-2\gamma l}) + Z_L(1 - e^{-2\gamma l})}$$

$$Z_{in}(-l) = Z_0 \frac{Z_L + Z_0 \tanh(\gamma l)}{Z_0 + Z_L \tanh(\gamma l)}$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} = \alpha + j\beta$$

Now we open and short the transmission line to measure its Z parameters.

$$Z_{11} = \left. \frac{v_1}{i_1} \right|_{i_2=0, Z_L=\infty} = Z_0 \frac{1}{\tanh(\gamma l)}$$

$$Z_{22} = Z_{11} \text{ due to symmetry}$$

$$Z_{12} = \left. \frac{v_1}{i_2} \right|_{i_1=0, Z_L=0} = Z_0 \frac{1}{\sinh(\gamma l)}$$

$$Z_{21} = Z_{12} \text{ due to reciprocity}$$

Keeping in mind that for a shorted tline, the voltage and current at a given point along the line are:

$$v(z) = V^+(e^{-\gamma z} + e^{\gamma z})$$

$$i(z) = \frac{V^+}{Z_0}(e^{-\gamma z} - e^{\gamma z})$$

3. Take the limit of a very short line and simplify the answer (Hint: use a Taylor series expansion and keep only the first few terms).

Use the expansions:

$$\tanh(x) = x - \frac{x^3}{3} + \frac{2x^5}{15} - \dots \text{ for } |x| < \frac{\pi}{2}$$

$$\sinh(x) = x + \frac{x^3}{3!} + \frac{x^5}{5!} + \dots \text{ for all } x$$

We plug the first two terms into the t-line's Z matrix for tanh and sinh. There isn't any other obvious simplification or limit taking to be done.

- Using the previous results, now derive the values for L, R, C, and G for the equivalent circuit.

I began this problem by equating the Z_{11} and Z_{12} parameters for the pi network and the transmission line. I also wrote down the equation relating γ and Z_0 with R,G,L,C.

```
%%
syms C w G R L
syms Z0 gamma l

Z1 = ((2/G)*(1/1i*w*C) / ((2/G) + (1/1i*w*C)));
%Z1 = 2 / (2*1i*w*C + G);
Z3 = Z1;
Z2 = R + 1i*w*L;

%%
Z_11 = (Z1*(Z2 + Z3)) / (Z1 + Z2 + Z3);
Z_12 = (Z1 * Z3) / (Z1 + Z2 + Z3);

Z_11_tline = Z0 / ((gamma*l - (gamma*l)^3 / 3 + 2*(gamma*l)^5 / 15));
Z_12_tline = Z0 / ((gamma*l + (gamma*l)^3 / 3*2 + (gamma*l)^5 / 5*4*3*2));


gamma_RLGC_relation = gamma == sqrt((R + 1i*w*L) * (G + 1i*w*C));
Z0_LC_relation = Z0 == sqrt((R + 1i*w*L)/(G + 1i*w*C));

sol = solve([Z_11 == Z_11_tline, Z_12 == Z_12_tline], [R, G, L, C]);
```

I tried to give different permutations of these equations to the solver, but wasn't able to find any sensible solution for R, G, L, C in terms of Z_0 , γ , and ω although I'm sure one exists.

3 Impedance Matching for Maximum Power Delivery

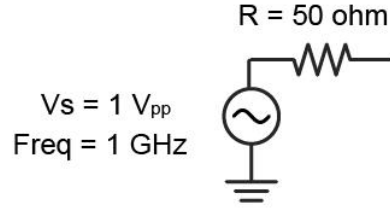- What is the maximum power that can be extracted from the source shown below? What is the optimal load impedance for the maximum power delivery to happen?



$$|I_s| = \frac{|V_s|}{|R_s + R_L|}$$

$$I_{s,rms} = \frac{1}{2}|I_s|$$

$$V_L = I_{s,rms}R_L$$


$$P_L = I_{s,rms}V_L = I_{s,rms}^2 R_L = 1/2 \left(\frac{V_s}{R_s + R_L} \right)^2 R_L$$

$$\frac{\partial P_L}{\partial R_L} = \left(\frac{-R_s}{R_L} \right)^2 + 1$$

Setting the denominator of derivative to 0 and solving gives $R_L = \pm R_s \rightarrow R_L = R_s$. Indeed, this minimizes the denominator, and thus maximizes the power delivered to the load.

$$P_{max} = \frac{V_s^2}{8R_L} = 2.5 \text{ mW}$$

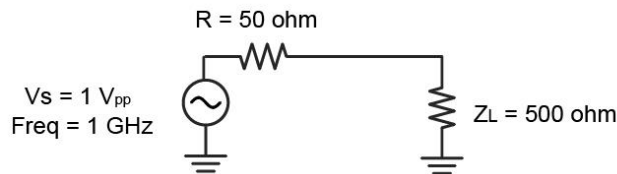2. Use this source to drive a 500Ω load and we directly connect the load to the source, as illustrated by the figure below. What is the power delivered to the 500Ω load and the load voltage?




$$P_L = 0.8 \text{ mW}$$

$$V_L = I_{s,rms}R_L = 0.45 \text{ V}$$

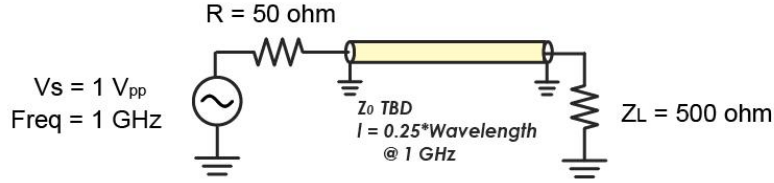3. Let's try to achieve impedance matching by putting a quarter-wavelength transmission line between the load and source, as indicated by the below figure. Find the characteristic impedance

Z_0 that maximizes the power delivered to the load. What are the corresponding power and voltage at the load?



The general form of input impedance for a lossless tline is:

$$Z_{in}(-l) = Z_0 \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)}$$

$$Z_{in}(-\lambda/4) = \frac{Z_0^2}{Z_L} = 50 \rightarrow Z_0 = 158\Omega$$

$$P_L = P_{max} = 2.5mW \text{ since the tline is lossless}$$

$$V_L = \sqrt{P_L R_L} = 1.118 \text{ V}$$

4. Following part c) assume the source frequency can change, what is the frequency interval where the power delivered to the 500Ω load is less than 3 dB from the maximum value? Use ADS to verify.

Assume that $\epsilon_{eff} = 4$. -3 dB power reduction is equivalent to the power halving. We fix the transmission line's length and Z_0 and sweep β to find where the effective resistance looking into the transmission line becomes sufficiently high to halve power.


$$P'_L = 1/2 \left(\frac{1}{50 + R_L} \right)^2 R_L = 2.5/2 \text{ mW}$$

Solving: $R_L = 292\Omega$

$$\beta = 76.1 \text{ to get an effective } R_L \text{ of } 292\Omega$$

$$\rightarrow f' = 1.8 \text{ Ghz}$$

In ADS:

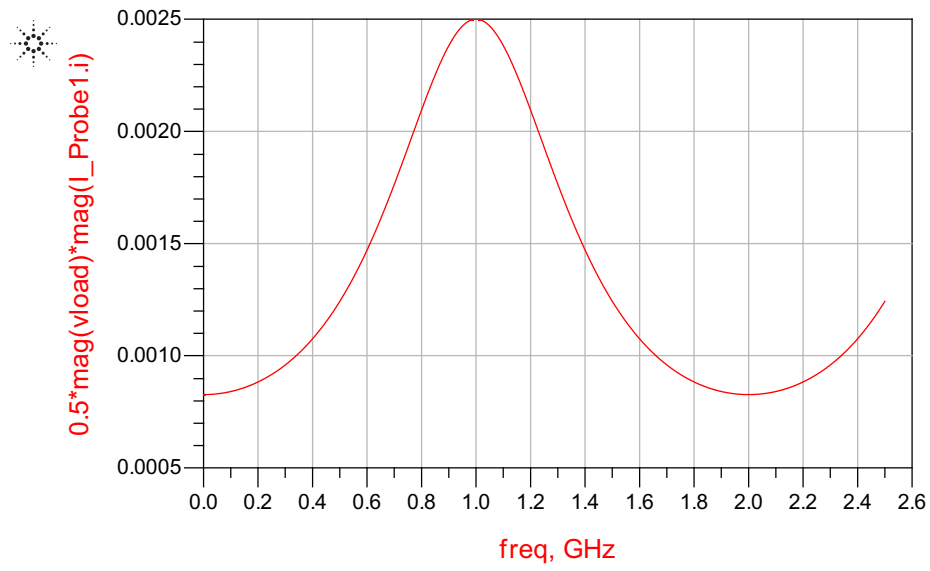

The simulation indicates a power halving at around 1.5 GHz. I suspect my assumption about ϵ_{eff} was problematic in the hand calculation.