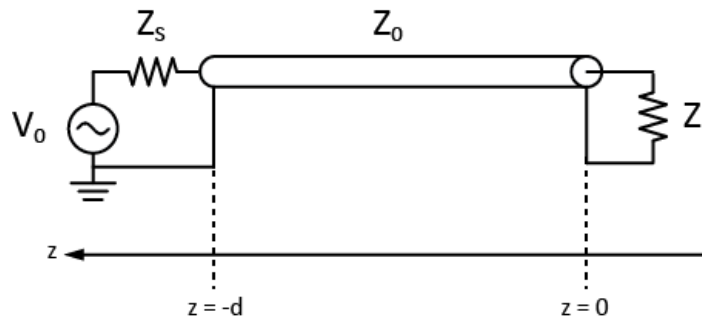



Problem Set 3

Submit through bcourses

1. Consider the transmission line circuit shown below. A voltage source generating 10V amplitude of sinewave at 10 GHz is driving a transmission line terminated with load $Z_L = 80 - j40$ ohm. The transmission line has a characteristic impedance of Z_0 (= 100 ohm), effective dielectric constant of 4, and length $d = 22.5$ mm.



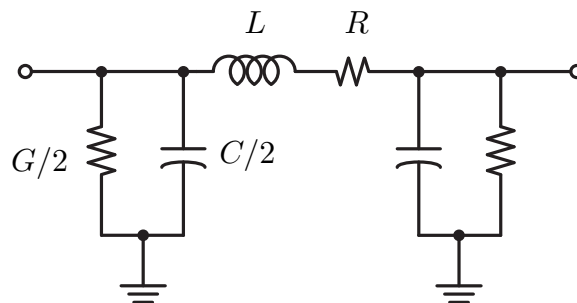- (a) Find the reflection coefficient at the load ($z = 0$) and at the source ($z = -d$).
 - (b) Find the input impedance at the source ($z = -d$) and at $z = 18.75$ mm.
 - (c) Plot the magnitude of the voltage along the line. Find voltage maximum, voltage minimum, and standing wave ratio.
2. In this problem you will derive an equivalent two-port circuit model for a short section of transmission line ($l \ll \lambda$), include loss.
 - (a) For a “pi” equivalent circuit shown below, find the two-port Z matrix.




- (b) Now consider a section of transmission line with loss. Find the two-port Z matrix. You can either derive from first principles or use the transmission line impedance equation derived in the notes (make sure you use the general expression with loss).


- (c) Take the limit of a very short line and simplify the answer (*Hint: Use a Taylor series expansion and keep only the first few terms.*)
- (d) Using the previous results, now derive the values for L , R , C , and G for the equivalent circuit.

3. Impedance Matching for Maximum Power Delivery

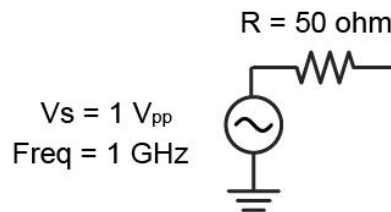
- (a) What is the maximum power that can be extracted from the source shown below? What is the optimal load impedance for the maximum power delivery to happen?



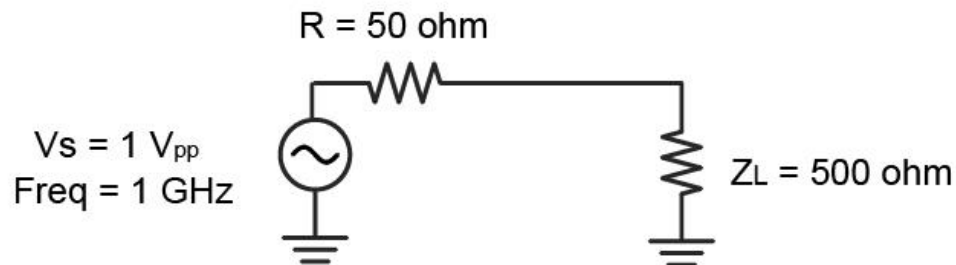- (b) Use this source to drive a 500Ω load and we directly connect the load to the source, as illustrated by the figure below. What is the power delivered to the 500Ω load and the load voltage?




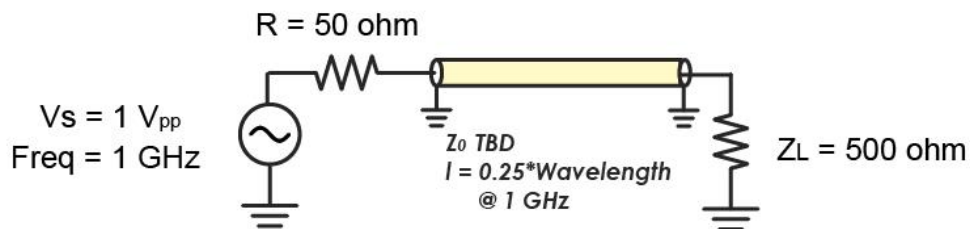- (c) Lets try to achieve impedance matching by putting a quarter-wavelength transmission line between the load and the source, as indicated by the below figure. Find the characteristic impedance Z_0 that maximizes the power delivered to the load. What are the corresponding power and voltage at the load?



- (d) Following part c, assume the source frequency can change, what is the frequency interval where the power delivered to the 500Ω load is less than 3 dB from the maximum value (3-dB bandwidth)? Use ADS simulation to verify your hand calculation. Notice the transmission line is only a quarter wavelength at 1 GHz.

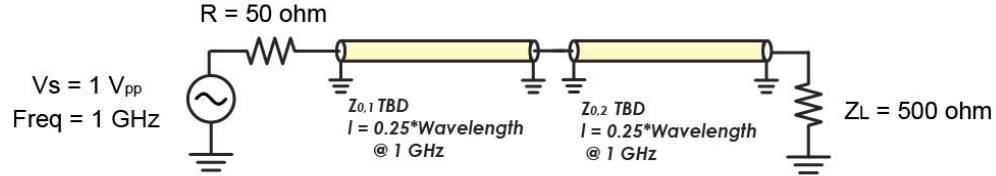- (e) (242A only) In order to achieve a better 3-dB bandwidth, a two-section transmission line is employed, as illustrated in the below figure. Find the two characteristic impedances $Z_{0,1}$ and $Z_{0,2}$ that maximize the power delivered to the 500Ω load at 1 GHz. Are there multiple ($Z_{0,1}$, $Z_{0,2}$) solutions?



- (f) (242A only) Following part (e), what is the ($Z_{0,1}$, $Z_{0,2}$) solution that corresponds to the best 3-dB bandwidth? What is the best 3-dB bandwidth? Use ADS simulation to verify your hand calculation.
4. (242A only) In this problem, compare an LC tank with a quarter wave line in terms of the quality factor (Q). Suppose that we wish to realize a 60 GHz resonator with the highest Q possible. For simplicity, assume that the only source of loss is the resistance of the metal (neglect skin effect), with sheet resistance given by $R_{\square} = 25\text{m}\Omega/\square$. Assume that the integrated circuit process has 8 metal layers with the distance between the top metal and the bottom metal at $10\mu\text{m}$.
- Calculate the dimensions of a microstrip line to resonate at 60 GHz.
 - What is the optimal characteristic impedance of the line to minimize the losses?
 - Calculate the radius of a loop inductor that occupies approximately the same area as the transmission line.
 - Assuming that lumped capacitors of infinite Q are available, compare the quality factor of the loop inductor in resonance with the transmission line resonator.
 - Compare the impedance of the LC tank at second and third harmonic to the transmission line.

You may find the following paper interesting to read: C. Marcu and A. M. Niknejad, "A 60 GHz high- Q tapered transmission line resonator in 90nm CMOS," *Microwave Symposium Digest*, 2008, IEEE MTT-S International, pp. 775- 778