

1. (a).  $\epsilon_r = 4$

$$v = \frac{1}{\sqrt{\epsilon_r}} \cdot c = \frac{1}{\sqrt{4}} \cdot 3 \times 10^8 \text{ m/s} = 1.5 \times 10^8 \text{ m/s}$$

$$\lambda f = v$$

$$\lambda = \frac{v}{f} = \frac{1.5 \times 10^8 \text{ m/s}}{1 \times 10^6 \text{ s}^{-1}} = 150 \text{ mm}$$

$$\frac{d}{\lambda} = 1.5$$

$$d = 1.5\lambda$$

① Use Smith Chart. normalize  $z_L$

$$\bar{z}_L = \frac{Z_L}{Z_0} = \frac{80 - j40}{100} = 0.8 - j0.4$$

So  $r = 0.8$ ,  $x = -0.4$  And find the corresponding point on the chart.

$$\text{So } |P_L| \approx 0.25, \angle P_L \approx 250^\circ$$

② Use calculation.

$$P_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{80 - j40 - 100}{80 - j40 + 100} = 0.2425 e^{j256^\circ}$$

At the source, Since  $d = 1.5\lambda$

$$\therefore P_L \text{ (at the source)} = P_L \text{ (at the load)} = 0.2425 e^{j256^\circ}$$

1(b). ① Use Smith Chart

$$z = 18.75 \text{ mm}$$

$$\frac{z}{\lambda} = 1.25 \text{ quarter wavelength.}$$

draw a circle, and use the opposite point on the circle.

②. read its  $r$  and  $x$  from the chart.  
about  $100 + j50j$ .

③. Use calculation

Since it is quarter wavelength

$$Z_{in} = \frac{Z_0^2}{Z_L} = \frac{100^2}{80 - j40j} = 100 + j50j$$

$\therefore$  input impedance at the source is  $80 - j40j$  (half wave length, so same as  $Z_L$ )  
input impedance at  $z = -18.75 \text{ mm}$  is  $100 + j50j$ .



1. (c).  $Z_S = 100 \Omega$

$$V_m = \frac{Z_m}{Z_m + Z_S} \cdot V_S = V^+ (1 + \rho_{LL})$$

$$\rho_{LL} = \rho_{LL} = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{80 - 40j - 100}{80 - 40j + 100} = 0.2425 e^{j 256^\circ}$$

$$Z_m = Z_L$$

$$Z_m = 80 - 40j$$

$$\frac{80 - 40j}{80 - 40j + 100} \cdot 10 = V^+ \left( 1 + \frac{80 - 40j - 100}{80 - 40j + 100} \right)$$

$$= V^+ \left( \frac{80 - 40j + 100 + 80 - 40j - 100}{80 - 40j + 100} \right)$$

$$= V^+ \left( \frac{160 - 80j}{80 - 40j + 100} \right)$$

$$\therefore V^+ = 5V$$

$$|V^+| = 5V$$

① For SWR, just find from the Smith Chart.

$$SWR \approx 1.65$$

②. For SWR, calculation.

$$SWR = \frac{1 + |\rho_L|}{1 - |\rho_L|} = \frac{1 + 0.2425}{1 - 0.2425} = 1.64$$

$$SWR = \frac{|V_{max}|}{|V_{min}|} = 1.64$$


$$|V_{max}| = (1 + |\rho_L|) \cdot |V^+| = 1.2425 \cdot 5 = 6.2125V$$

$$|V_{min}| = (1 - |\rho_L|) \cdot |V^+| = 3.7875V$$


$$|V_L| = |V_m| = |V^+ (1 + \rho_L)| = 5 \cdot \left( 1 + \frac{80 - 40j - 100}{80 - 40j + 100} \right) = 5 \cdot 0.97 e^{-14^\circ j}$$

$$= |5 \cdot 0.97|$$

$$= 4.85V$$

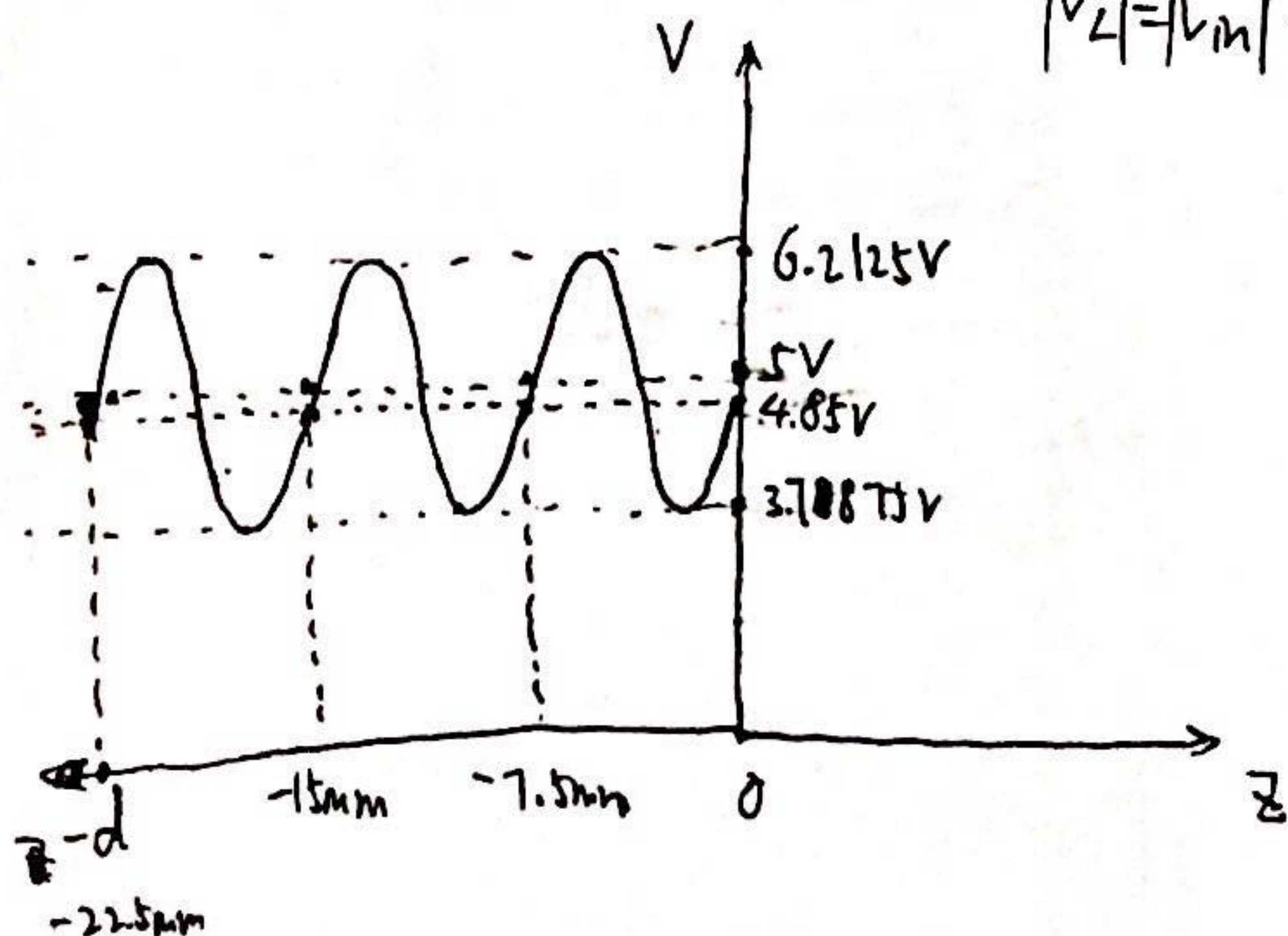




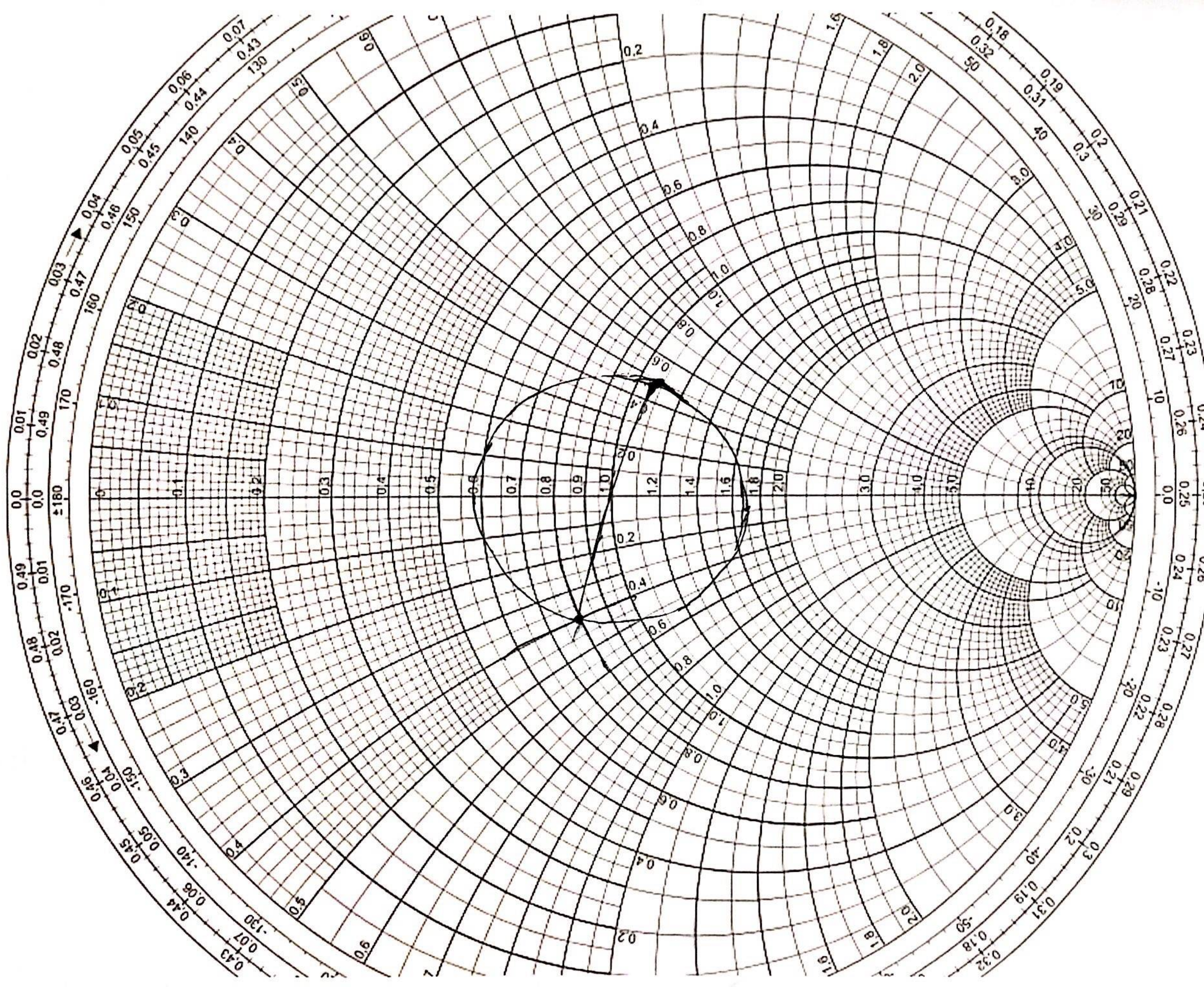



2. (c).

$$Z_{11} = \frac{V_1}{i_1} \Big|_{i_2=0}$$

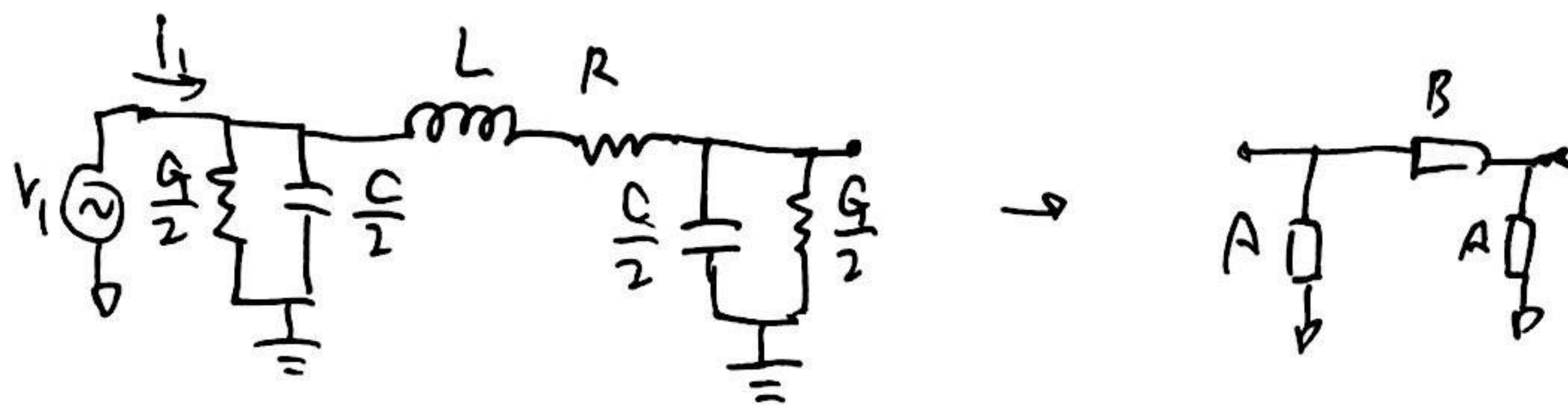


$$Z_{11} = \frac{1}{\frac{G}{2} \parallel \left( \frac{C}{2} \parallel \left[ L + R + \left( \frac{C}{2} \parallel \frac{G}{2} \right) \right] \right)} \quad (\text{"+" means in series})$$

$$= \frac{1}{\left( \frac{2}{G} \parallel \frac{2}{j\omega C} \right) \parallel \left[ j\omega L + R + \left( \frac{2}{j\omega C} \parallel \frac{2}{G} \right) \right]} = A \parallel (A+B)$$

$$Z_{12} = Z_{21}$$

$$Z_{12} = Z_{21} = \frac{V_1}{i_2} \Big|_{i_1=0}$$

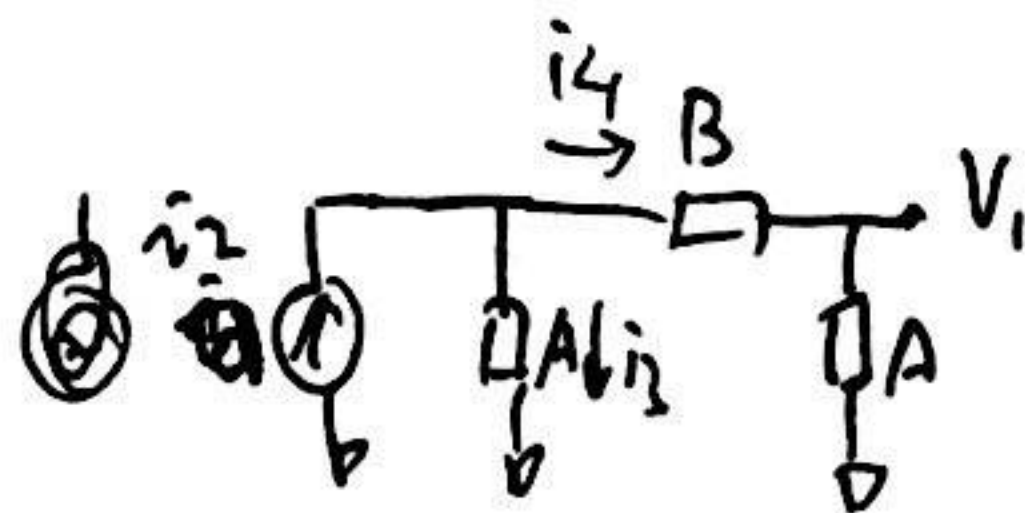

$$\begin{cases} V_1 = i_4 \cdot A \\ i_2 = i_3 + i_4 \\ i_3 A = i_4 (A+B) \end{cases}$$

$$\therefore V_1 = i_4 \cdot A = \frac{A}{2A+B} \cdot i_2 \cdot A$$

$$Z_{12} = Z_{21} = \frac{A^2}{2A+B}$$

$$A = \frac{G}{2} \parallel \frac{2}{j\omega C} = \frac{2}{j\omega C + G}$$

$$B = j\omega L + R$$

$$= \frac{\left( \frac{2}{G} \parallel \frac{2}{j\omega C} \right)^2}{2 \cdot \left( \frac{2}{G} \parallel \frac{2}{j\omega C} \right) + j\omega L + R}$$

$$\therefore Z_{\text{matrix}} = \begin{bmatrix} \left( \frac{2}{G} \parallel \frac{2}{j\omega C} \right) \parallel [j\omega L + R + \left( \frac{2}{j\omega C} \parallel \frac{2}{G} \right)] & \frac{\left( \frac{2}{G} \parallel \frac{2}{j\omega C} \right)^2}{2 \cdot \left( \frac{2}{G} \parallel \frac{2}{j\omega C} \right) + j\omega L + R} \\ \frac{\left( \frac{2}{G} \parallel \frac{2}{j\omega C} \right)^2}{2 \cdot \left( \frac{2}{G} \parallel \frac{2}{j\omega C} \right) + j\omega L + R} & \left( \frac{2}{G} \parallel \frac{2}{j\omega C} \right) \parallel [j\omega L + R + \left( \frac{2}{j\omega C} \parallel \frac{2}{G} \right)] \end{bmatrix}$$

$$= \begin{bmatrix} A \parallel (A+B) & \frac{A^2}{2A+B} \\ \frac{A^2}{2A+B} & A \parallel (A+B) \end{bmatrix}$$

(More detailed organized form is in (c).)


2. (b).  $\gamma = \alpha + j\beta = \sqrt{(R' + j\omega L')(G' + j\omega C')}$

$$V(z) = V^+ e^{-\gamma z} + V^- e^{\gamma z} = V^+ (e^{-\gamma z} + \rho_L e^{\gamma z})$$

$$i(z) = \frac{V^+}{Z_0} e^{-\gamma z} - \frac{V^-}{Z_0} e^{\gamma z} = \frac{V^+}{Z_0} (e^{-\gamma z} - \rho_L e^{\gamma z})$$

$$Z_m(z) = \frac{V(z)}{i(z)} = Z_0 \frac{e^{-\gamma z} + \rho_L e^{\gamma z}}{e^{-\gamma z} - \rho_L e^{\gamma z}} = Z_0 \frac{1 + \rho_L e^{2\gamma z}}{1 - \rho_L e^{2\gamma z}}, \quad \rho_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$
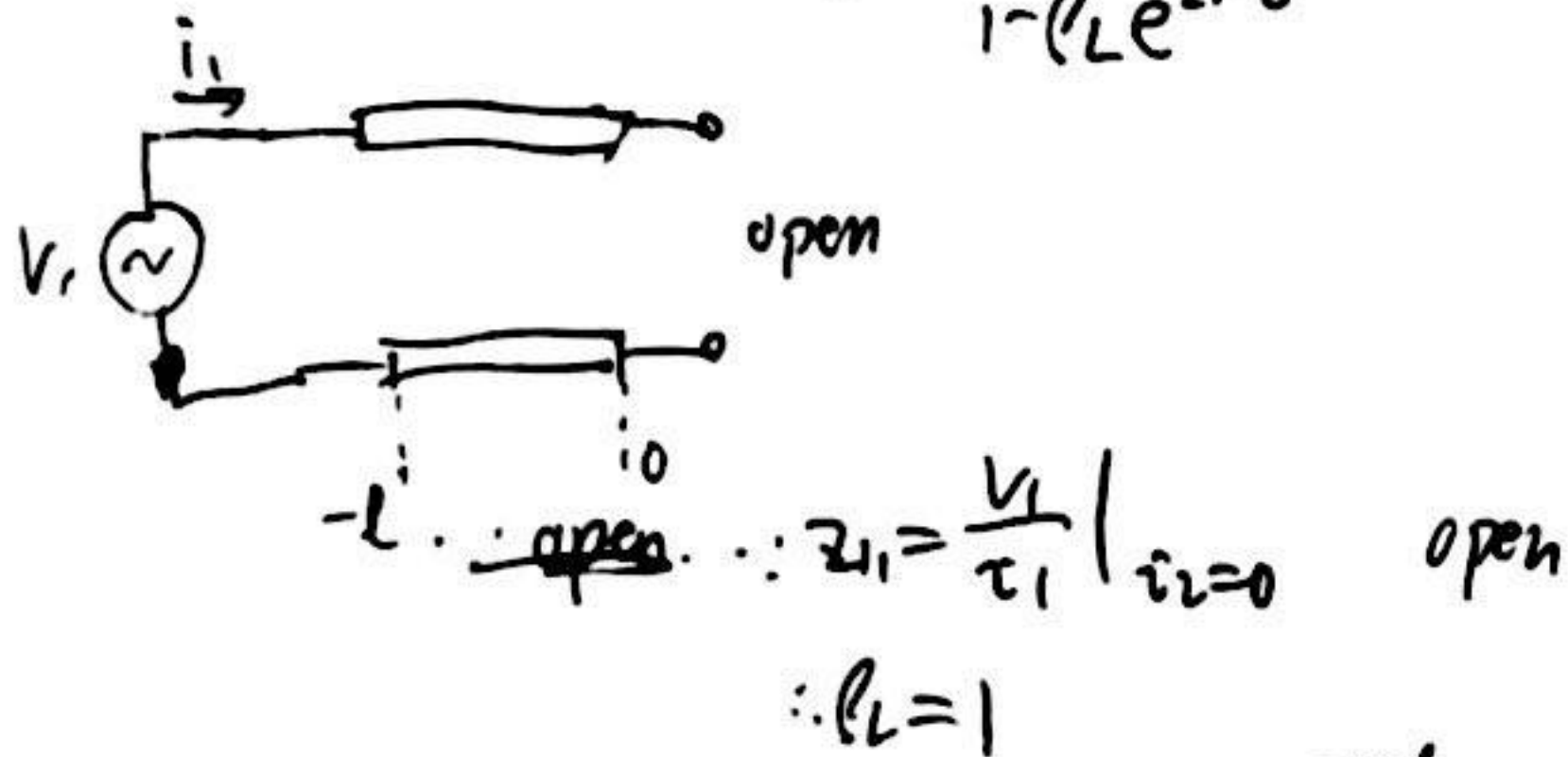
$$Z_{11} = Z_m(-l) = Z_0 \frac{1 + \rho_L e^{2\gamma l}}{1 - \rho_L e^{2\gamma l}}$$




$$\therefore Z_{11} = Z_0 \frac{1 + e^{-2\gamma l}}{1 - e^{-2\gamma l}}$$

$$Z_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$$

$$\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}$$

$$Z_{12} = Z_{21} = \frac{V_2}{i_1} \Big|_{i_2=0}$$

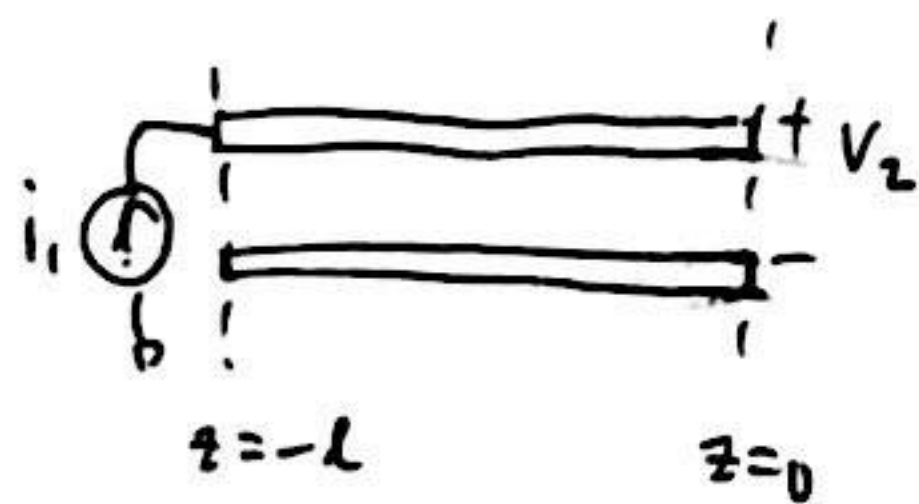

$$i_2 = i(0) = \frac{V^+}{Z_0} (1 - \rho_L) = 0 \Rightarrow \rho_L = 1$$

$$V_{01} = V(-l) = V^+ (e^{\gamma l} + \rho_L e^{-\gamma l}) = V^+ (e^{\gamma l} + e^{-\gamma l})$$

$$i_1 = i(-l) = \frac{V^+}{Z_0} (e^{\gamma l} - \rho_L e^{-\gamma l}) = \frac{V^+}{Z_0} (e^{\gamma l} - e^{-\gamma l})$$

$$V_2 = V(0) = V^+ (1 + \rho_L) = 2V^+$$

$$\therefore Z_{12} = Z_{21} = \frac{V_2}{i_1} \Big|_{i_2=0}$$

$$= \frac{2Z_0}{e^{\gamma l} - e^{-\gamma l}}, \quad Z_0 = \sqrt{\frac{L'}{C'}}, \quad \gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}$$

$$Z_{matrix} = \begin{bmatrix} \frac{1 + e^{-2\gamma l}}{1 - e^{-2\gamma l}} & \frac{2}{e^{\gamma l} - e^{-\gamma l}} \\ \frac{2}{e^{\gamma l} - e^{-\gamma l}} & \frac{1 + e^{-2\gamma l}}{1 - e^{-2\gamma l}} \end{bmatrix} \cdot Z_0 = \begin{bmatrix} \frac{e^{\gamma l} + e^{-\gamma l}}{e^{\gamma l} - e^{-\gamma l}} & \frac{2}{e^{\gamma l} - e^{-\gamma l}} \\ \frac{2}{e^{\gamma l} - e^{-\gamma l}} & \frac{e^{\gamma l} + e^{-\gamma l}}{e^{\gamma l} - e^{-\gamma l}} \end{bmatrix} \cdot Z_0$$



2.(b) continued  $A // (A+B) = \frac{\frac{2}{j\omega C + G} \cdot (j\omega L + R) + \frac{A^2}{j\omega C + G}}{\frac{4}{j\omega C + G} + j\omega L + R}$

$$= \frac{2 \cdot [(j\omega L + R)(j\omega C + G) + 2]}{4(j\omega C + G) + (j\omega L + R)(j\omega C + G)^2}$$

$$\frac{A^2}{2A+B} = \frac{\left(\frac{2}{j\omega C + G}\right)^2}{\frac{4}{j\omega C + G} + j\omega L + R} = \frac{4}{4(j\omega C + G) + (j\omega L + R)(j\omega C + G)^2}$$

$$Z_{matrix} = Z_0 \cdot \begin{bmatrix} \frac{e^{\gamma l} + e^{-\gamma l}}{e^{\gamma l} - e^{-\gamma l}} & \frac{2}{e^{\gamma l} - e^{-\gamma l}} \\ \frac{2}{e^{\gamma l} - e^{-\gamma l}} & \frac{e^{\gamma l} + e^{-\gamma l}}{e^{\gamma l} - e^{-\gamma l}} \end{bmatrix}$$

$$\therefore \int e^{\gamma l} + e^{-\gamma l} = [(j\omega L + R)(j\omega C + G) + 2]$$

$$\frac{1}{Z_0} (e^{\gamma l} - e^{-\gamma l}) = \frac{1}{2} [4(j\omega C + G) + (j\omega L + R)(j\omega C + G)^2] = 2(j\omega C + G) + \frac{1}{2}(j\omega L + R)(j\omega C + G)^2$$

(c)  $\cancel{e^{\gamma l} + e^{-\gamma l}}$   
 $e^{\gamma l} \approx 1 + \gamma l + \frac{1}{2}\gamma^2 l^2 + \frac{1}{6}\gamma^3 l^3$   
 $e^{-\gamma l} \approx 1 - \gamma l + \frac{1}{2}\gamma^2 l^2 - \frac{1}{6}\gamma^3 l^3$

$$e^{\gamma l} + e^{-\gamma l} = 2 + \gamma^2 l^2 = \cancel{2 + (\alpha + j\beta)^2 l^2}$$

$$e^{\gamma l} - e^{-\gamma l} = 2\gamma l + \frac{1}{3}\gamma^3 l^3$$

$$\therefore \int \cancel{2 + \gamma^2 l^2} = 2 + (j\omega L + R)(j\omega C + G)$$

$$\frac{1}{2(2\gamma l + \frac{1}{3}\gamma^3 l^3)} \cdot \frac{1}{Z_0} = \frac{1}{Z_0} \gamma l (2 + \frac{1}{3}\gamma^2 l^2) = 2(j\omega C + G) + \frac{1}{2}(j\omega L + R)(j\omega C + G)^2$$

To match each equation.



2 (c) continued.

$$Z_{matrix} = Z_0 \begin{bmatrix} \frac{2+\gamma^2 l^2}{2\gamma l + \frac{1}{3}\gamma^3 l^3} & \frac{2}{2\gamma l + \frac{1}{3}\gamma^3 l^3} \\ \frac{2}{2\gamma l + \frac{1}{3}\gamma^3 l^3} & \frac{2+\gamma^2 l^2}{2\gamma l + \frac{1}{3}\gamma^3 l^3} \end{bmatrix}$$

$$Z_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} \quad \gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}$$

compare to simple model

$$\begin{bmatrix} \frac{2 + (j\omega L + R)(j\omega C + G)}{2(j\omega C + G) + \frac{1}{2}(j\omega L + R)(j\omega C + G)^2} & \frac{2}{2(j\omega C + G) + \frac{1}{2}(j\omega L + R)(j\omega C + G)^2} \\ \frac{2}{2(j\omega C + G) + \frac{1}{2}(j\omega L + R)(j\omega C + G)^2} & \frac{2 + (j\omega L + R)(j\omega C + G)}{2(j\omega C + G) + \frac{1}{2}(j\omega L + R)(j\omega C + G)^2} \end{bmatrix}$$

(d). From observation


$$\begin{cases} 2 + \gamma^2 l^2 = 2 + (j\omega L + R)(j\omega C + G) \\ \frac{1}{Z_0} \cdot \gamma l (2 + \frac{1}{3}\gamma^2 l^2) = (j\omega C + G) \cdot [2 + \frac{1}{2}(j\omega L + R)(j\omega C + G)] \end{cases}$$

$$\therefore \begin{cases} \gamma l = \sqrt{(R + j\omega L)(G + j\omega C)} = \sqrt{(R' + j\omega L')(G' + j\omega C')} \cdot l \\ \frac{\gamma l}{Z_0} = j\omega C + G = (j\omega C' + G') \cdot l \end{cases}$$

$$\therefore \begin{cases} R = R' \cdot l \\ G = G' \cdot l \\ C = C' \cdot l \\ L = L' \cdot l \end{cases}$$

(The 3rd order has coefficient mismatch, but 0, 1, & 2 order match, so the approximation is very close)

So the model is equivalent

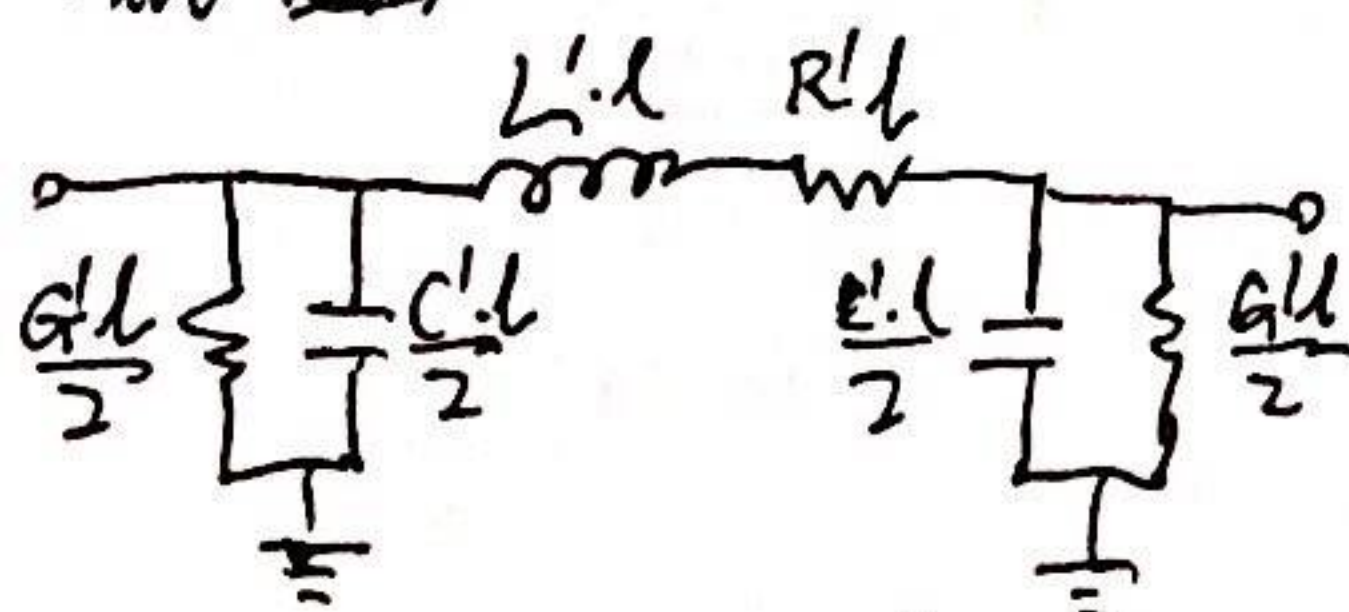

So the spi model is a good approximation.



3. (a) Load impedance should be  $50 \Omega$ .

$$P_{\max} = \frac{1}{2} \left( \frac{V_{PP}}{2R} \right)^2 \cdot R = \frac{V_{PP}^2}{32} \cdot \frac{1}{50 \Omega} = \frac{1}{32} \cdot \frac{1}{50} = 0.625 \text{ mW}$$

(b).

$$P_L = \frac{1}{8} \cdot \left( \frac{V_{PP}}{R+Z_L} \right)^2 \cdot Z_L = \frac{1}{8} \left( \frac{1}{50+500} \right)^2 \cdot 500 = 0.2066 \text{ mW}$$

$$V_L = \frac{Z_L}{Z_L+R} \cdot V_S = 0.909 V_{PP}$$

(c).

$$Z_0 = \sqrt{R \cdot Z_L} = \sqrt{50 \cdot 500} \approx 158.1 \Omega$$

$$V_L = \frac{Z_L}{Z_L+R} \cdot V_S = 0.909 V_{PP}$$

$$P_L = \frac{1}{8} \cdot \left( \frac{V_{PP}}{2R} \right)^2 \cdot R = 0.625 \text{ mW}$$

$$P_L = \frac{1}{8} \cdot \left( \frac{V_{PP}}{2R} \right)^2 \cdot R = 0.625 \text{ mW}$$

(d).

$$P_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{500 - 158.1}{500 + 158.1} = 0.52$$

Let  $\alpha$  be the division.

$$P_{\text{refl}} = \frac{1}{8} \frac{V_{PP}^2}{|Z_m + R|^2} \cdot \text{Re}\{Z_m\} = \frac{1}{2} P_{\text{in}} = \frac{1}{2} \cdot 0.625 \text{ mW}$$

$$Z_m = Z_0 \cdot \frac{1 + \rho_L e^{-2\gamma L (\frac{A}{4} + x)}}{1 - \rho_L e^{-2\gamma L (\frac{A}{4} + x)}} = 50 \cdot \frac{1 + 0.52 e^{-2\gamma L x}}{1 - 0.52 e^{-2\gamma L x}}$$

Solve the equation.

$$\frac{1}{|Z_m + R|^2} \text{Re}\{Z_m\} = 0.3125 \text{ mW}$$

we get  $x \approx \pm 11.13 \text{ mm}$

$$\Delta f \approx \pm 495 \text{ MHz}$$

$\therefore$  frequency range from  $505 \text{ MHz} \sim 1.495 \text{ GHz}$ .

The simulation yields same results.



$$\text{Eqn } P = 0.5 * \text{dB}(VL * VL / 500 / 2)$$

m3  
freq=1.001GHz  
P=-32.041

m2  
freq=1.495GHz  
P=-35.048

m1  
freq=504.5MHz  
P=-35.048

