

# EE142 Problem Set 4

Vighnesh Iyer

September 27, 2017

## Problem 1

Calculate the scattering parameters of the following circuits:

- (a) Find the input  $S_{11}$  for a general two-port terminated at port 2 with a load reflection coefficient of  $\Gamma_L$ .

We will call the wave going into port 1  $V_1^+$ , the wave coming out of port 1  $V_1^-$ , the wave *into* port 2  $V_2^+$  and the wave out of port 2  $V_2^-$ .

We can then write the voltage waves in terms of the *two-port* S parameters.

$$\begin{aligned}V_1^- &= S_{11}V_1^+ + S_{12}V_2^+ \\V_2^- &= S_{21}V_1^+ + S_{22}V_2^+\end{aligned}$$

Now, if port two is terminated by a load which results in reflection coefficient  $\Gamma_L$ , then the network effectively becomes a 1 port network. We can write the one-port  $S_{11}$  in terms of the two-port S parameters.

Throughout this problem we will assume that the two-port S parameters, the one port  $S_{11}$ , and  $\Gamma_L$  are with respect to a reference of  $Z_0$ .

$$\begin{aligned}V_2^+ &= V_2^- \Gamma_L \\V_1^- &= S_{11}V_1^+ + S_{12}V_2^- \Gamma_L\end{aligned}\tag{1}$$

$$V_2^- = S_{21}V_1^+ + S_{22}V_2^- \Gamma_L\tag{2}$$

$$\text{Rewriting equ 2: } V_2^- = \frac{S_{21}V_1^+}{1 - S_{22}\Gamma_L}$$

$$\text{Plug into equ 1: } V_1^- = S_{11}V_1^+ + S_{12}\Gamma_L \frac{S_{21}V_1^+}{1 - S_{22}\Gamma_L}$$

$$\text{Finally: } \boxed{\frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L}}$$

$$\text{Notice: } \frac{V_1^-}{V_1^+} = S_{11,one-port}$$

- (b) In the previous problem, what is the power that reaches the load in terms of the two-port scattering parameters and  $\Gamma_L$ ? Suppose the input is driven with a matched source.

We derived the available power from the source for a 1-port network to be:

$$P_{avs} = \frac{|V_s|^2}{8Z_0}$$

where  $V_s$  is the amplitude at the generator. Assuming a perfect input match:

$$V_1^+ = V_s/2$$

The power seen by the load can be found as:

$$P_L = \frac{|V_2^-|^2 - |V_2^+|^2}{2Z_0} = \frac{|V_2^-|^2(1 - |\Gamma_L|^2)}{2Z_0}$$

Recall from the previous part that  $V_2^-$  can be written in terms of S parameters:

$$V_2^- = \frac{S_{21}v_1^+}{1 - S_{22}\Gamma_L}$$

Then,  $P_L$  can be written as such:

$$P_L = \frac{|S_{21}|^2|v_1^+|^2}{|1 - S_{22}\Gamma_L|^2} \cdot \frac{1 - |\Gamma_L|^2}{2Z_0}$$

Substituting for  $V_1^+$ :

$$P_L = \frac{|S_{21}|^2|v_s|^2}{4|1 - S_{22}\Gamma_L|^2} \cdot \frac{1 - |\Gamma_L|^2}{2Z_0}$$

- (c) Derive the two-port scattering parameters of a three-port where port 3 is terminated in a load with reflection coefficient  $\Gamma_L$ .