

# EE142 Problem Set 9

Vighnesh Iyer

November 15, 2017

## 1 Review of Important Concepts


Assume a memoryless distortion circuit is modeled by  $I_{out} = a_0 + a_1 V_{in} + a_2 V_{in}^2 + a_3 V_{in}^3$  and the input DC bias voltage is  $V_{in,0}$ .

- (a) Derive IIP3, OIP3,  $IP_{1dB}$ , and  $IP_{3dB}$
- (b) If IIP3 is 10V, what is the input-blocker level that degrades the small-signal gain of the desired signal by 2dB?
- (c) Following part (b), what will be the tolerable blocker levels for a two-tone blocker?
- (d) If IIP3 is 10V, what are the  $IP_{1dB}$  for two-tone and three-tone input signals?
- (e) If the modeled circuit is a BJT with  $I_{out} = I_s \exp(V_{be}/V_T)$ , use a math tool to find the actual output third-harmonic current as a function of the input magnitude. Compare the actual values to the estimated values via the power series.

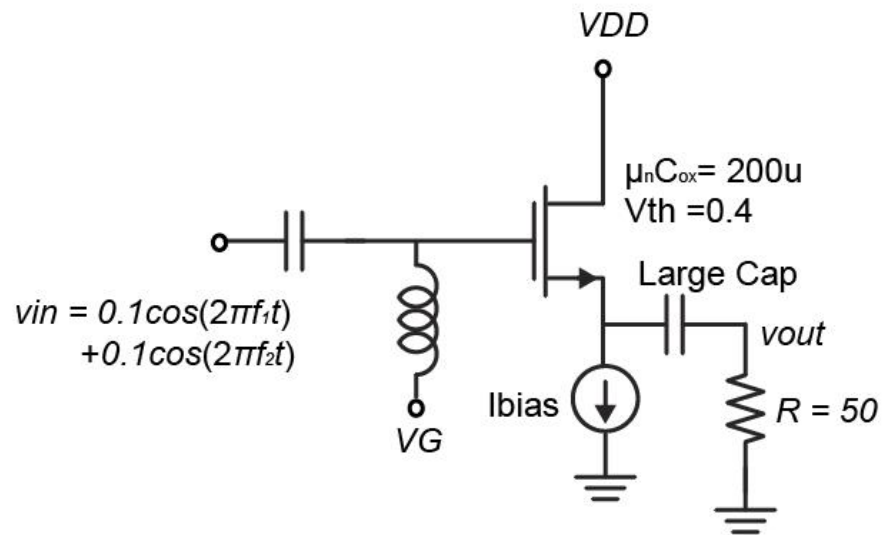
## 2 Distortion of a Source Follower

For the source follower shown below, calculate the required bias current ( $I_{bias}$  and W/L for the long-channel transistor to drive the load with a swing of 100 mV (at both  $f_1$  and  $f_2$ ), with IM3 equal to -50 dBc.

Correction:  $v_{out} = 0.1\cos(2\pi f_1 t) + 0.1\cos(2\pi f_2 t)$   $v_{in}$  magnitude is not specified


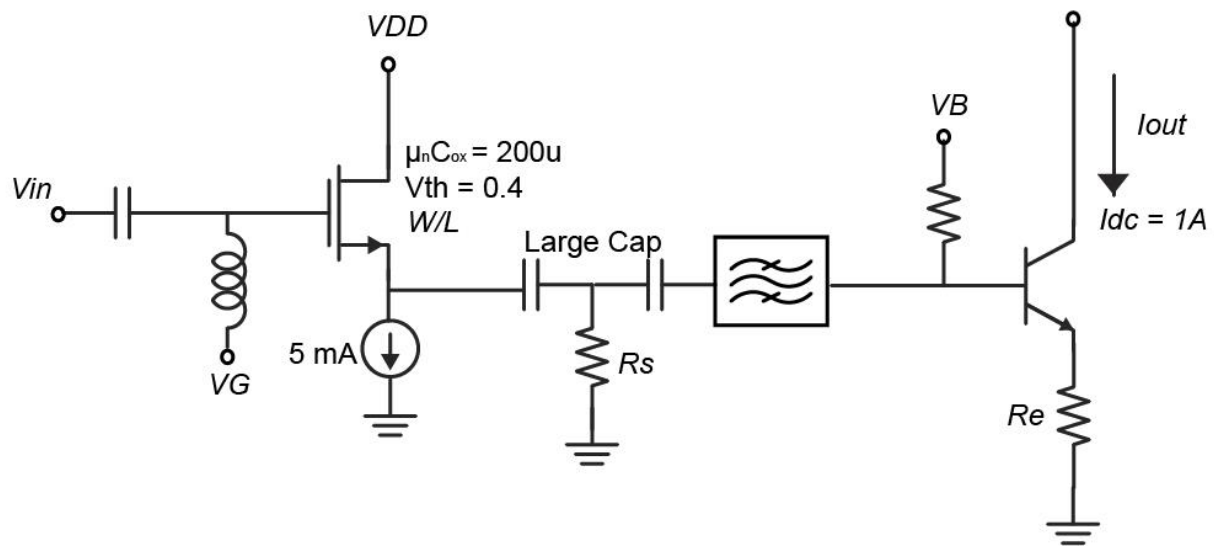
### 3 Pre-distortion and Source-degeneration Linearizer



- For the above schematic, what are the OIP3 of the BJT stage for  $R_e = 0\Omega$  and  $R_e = 0.02\Omega$ ?
- What are the two possible  $R_e$  for the BJT stage to have an OIP3 of 10A?