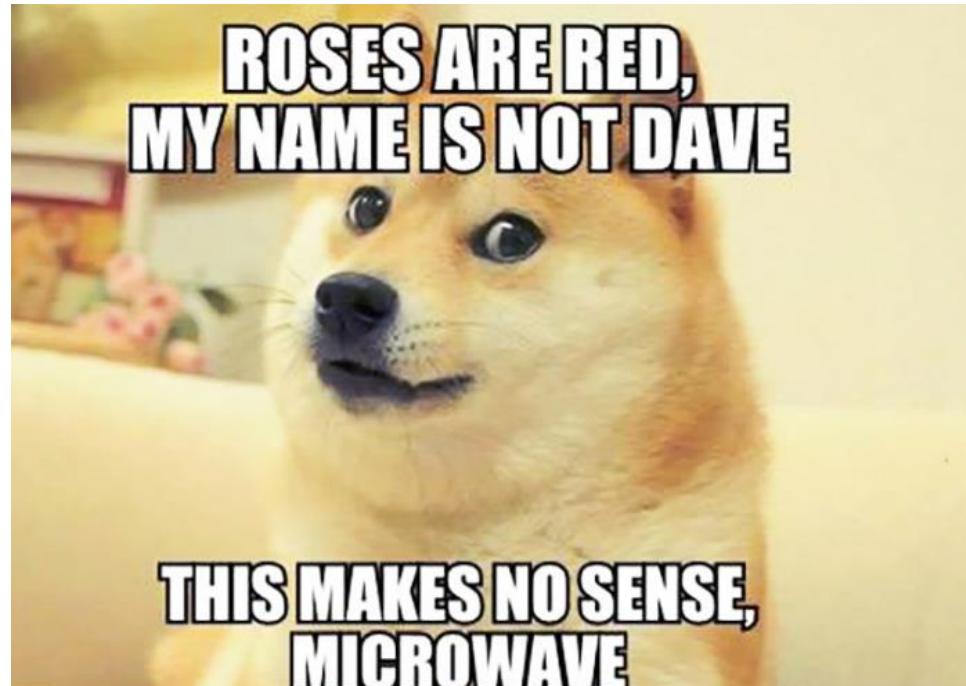


Today's Agenda (09272017)

- HW4#1. More S-parameter Questions
- HW4#2,3. Simple Smith Chart Manipulation
- HW4#4(d)(e) Smith Chart Matching Examples



1. Calculate the scattering parameters of the following circuits:


- (a) Find the input S_{11} for a general two-port terminated at port 2 with a load reflection coefficient of Γ_L .

Assume the two-port is described by a S -parameter with reference Z_0

Assume the required input S_{11} is with reference Z_0

Assume the load reflection Γ_L is with reference Z_0
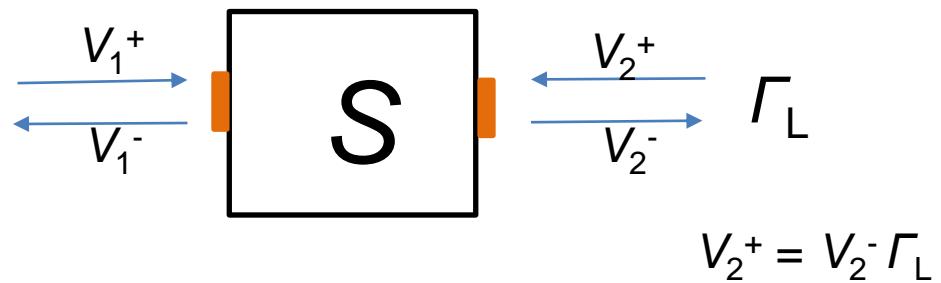
$$\begin{pmatrix} \frac{V_1^-}{\sqrt{Z_1}} \\ \frac{V_2^-}{\sqrt{Z_2}} \\ \frac{V_3^-}{\sqrt{Z_3}} \end{pmatrix} = \begin{pmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{pmatrix} \begin{pmatrix} \frac{V_1^+}{\sqrt{Z_1}} \\ \frac{V_2^+}{\sqrt{Z_2}} \\ \frac{V_3^+}{\sqrt{Z_3}} \end{pmatrix}$$



$$\begin{pmatrix} V_1^- \\ V_2^- \end{pmatrix} = \begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} \begin{pmatrix} V_1^+ \\ V_2^+ \end{pmatrix}$$

$$V_1^+ = V_2^- (1 - S_{22}\Gamma_L)/S_{21}$$


$$V_1^- = V_2^- \{(1 - S_{22}\Gamma_L)S_{11}/S_{21} + S_{12}\Gamma_L\}$$

$$V_1^-/V_1^+ = S_{11} + S_{12}S_{21}\Gamma_L/(1 - S_{22}\Gamma_L)$$

Recall how did we calculate S_{11} of a two port

S-Parameter and Power

In phasor domain (ac analysis)

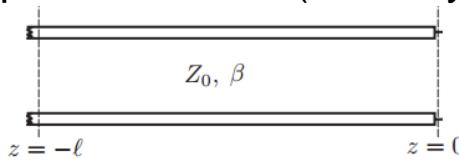

Recall what can exist on a cable

$$v(z) = V^+ e^{-\gamma z} + V^- e^{\gamma z}$$

$$i(z) = \frac{V^+}{Z_0} e^{-\gamma z} - \frac{V^-}{Z_0} e^{\gamma z}$$

$$\gamma = j\beta = j2\pi/\lambda$$

Power sent:

$$P_{in} = 0.5 * \text{Real}\{ v(z) i(z)^* \}$$

$$= 0.5 * \text{Real}\{ |V^+|^2/Z_0 - |V^-|^2/Z_0 + V^*(V^{+*}) e^{2\gamma z}/Z_0 - V^+(V^{*}) e^{-2\gamma z}/Z_0 \}$$

$$= |V^+|^2/2Z_0 - |V^-|^2/2Z_0$$

Power Sent = Forward-wave power - Backward-wave power

$$P_{in} = [|V_1^+|^2 - |V_1^-|^2] / 2Z_0$$

$$P_{load} = [|V_2^+|^2 - |V_2^-|^2] / 2Z_0 = |V_2^-|^2 [1 - |\Gamma_L|^2] / 2Z_0$$

$$\text{Power Gain} = P_{load}/P_{in} = |S_{21}/(1-S_{22}\Gamma_L)|^2 \times [1 - |\Gamma_L|^2] / [1 - |S_{11}|^2 + S_{12}S_{21}\Gamma_L/(1-S_{22}\Gamma_L)]^2$$


Remarks:

1. P_{av} of a source with $Z_s = Z_0$ is $|V_1^+|^2/2Z_0$ (explained later)
2. If $\Gamma_L = 0$, $P_{load}/P_{in} = |S_{21}|^2 / (1 - |S_{11}|^2)$ (power gain)
3. If $\Gamma_L = 0$, $P_{load} = |V_2^-|^2 / 2Z_0$
4. If $Z_s = Z_0$ and $\Gamma_L = 0$, $P_{load} = P_{av}|S_{21}|^2$ (using 1 and 3)
5. If $Z_s = Z_0$ and $\Gamma_L = 0$, $P_{in} = P_{av}(1 - |S_{11}|^2)$ (using 1 and 4)



Why S-Parameters ? (B)

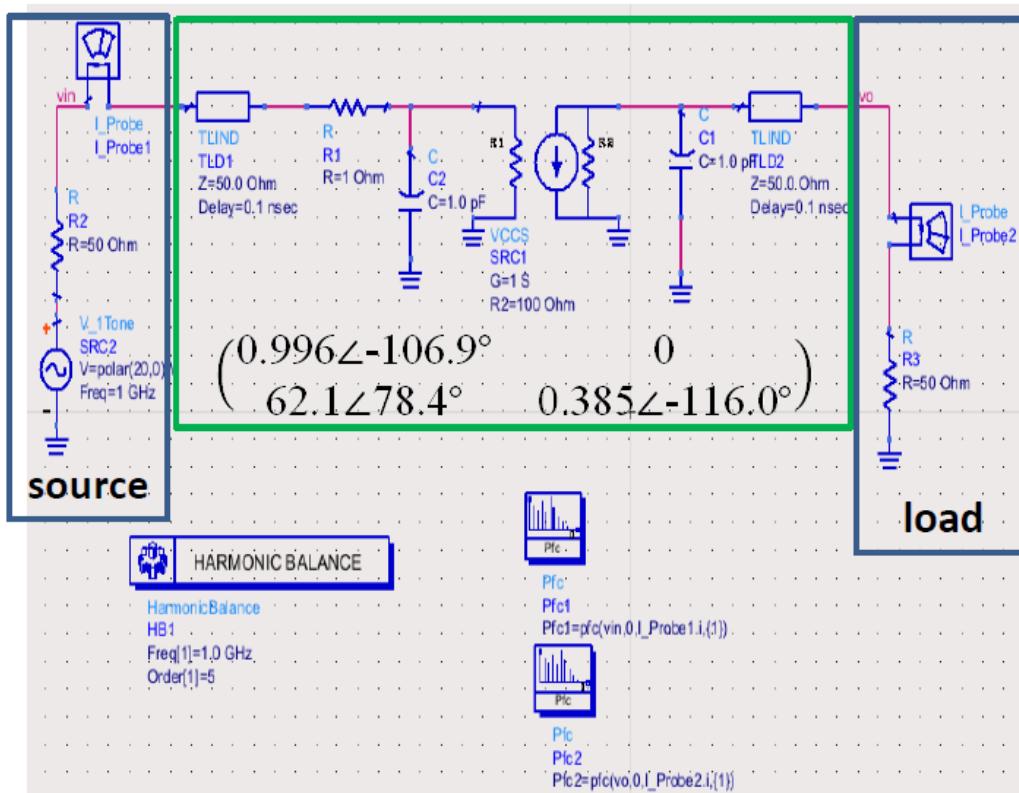S-parameter has a straightforward connection to the power flow in a microwave system



- In microwave systems, load and source impedances are usually 50Ω (**why?**)
- In this case, the source can provide maximum power of **1 W**

$$\text{Power to the load: } P_{\text{load}} \\ \textcolor{red}{1}^*|S_{21}|^2 = 3856$$


- Power into the circuit: P_{load}
 $1^*(1-|S_{11}|^2) = 1 - 0.9964^2 = 0.0072$

($S_{11} = 0.996$ indicates most power from the source is reflected)

- Matching:** Create a $50\text{-}\Omega$ load impedance for the source so all the 1-W power can be delivered into the circuit

S-parameter and Power

- P_{avs} of a source with $Z_s = Z_0$ is $|V_1^+|^2/2Z_0$

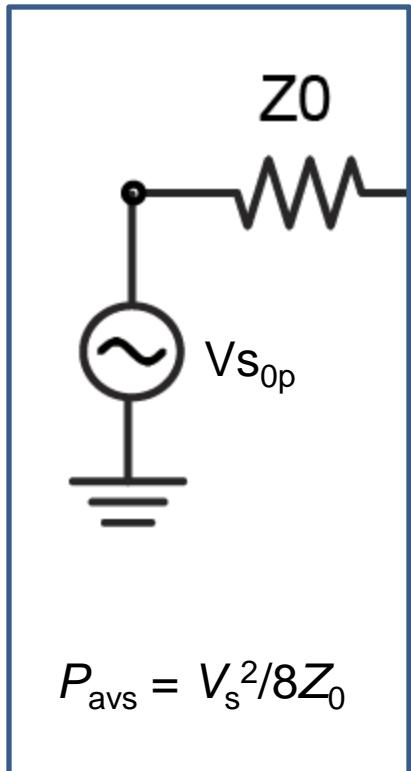

$$V_1^- = V_1^+ \Gamma_L$$

$$V_1^+ + V_1^- = V_s - Z_0(V_1^+/Z_0 - V_1^-/Z_0)$$

$$\Rightarrow V_1^+ = V_s/2$$

$$\Rightarrow P_{\text{avs}} = |V_1^+|^2/2Z_0$$

$$P_{\text{in}} = |V_1^+|^2/2Z_0 - |V_1^-|^2/2Z_0$$


$$= P_{\text{avs}}(1 - |V_1^-/V_1^+|^2)$$

$$= P_{\text{avs}}(1 - |\Gamma_L|^2)$$

1. Calculate the scattering parameters of the following circuits:

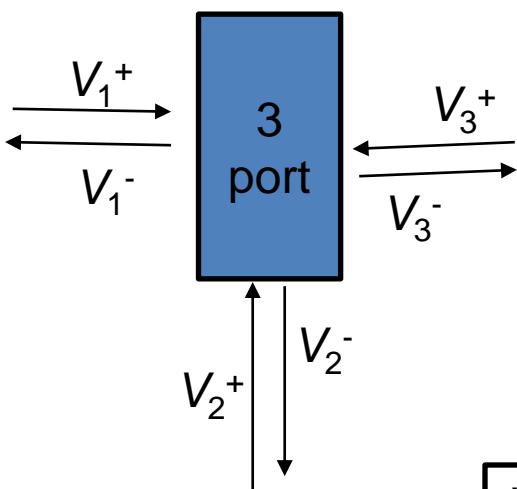- (a) Find the input S_{11} for a general two-port terminated at port 2 with a load reflection coefficient of Γ_L . (see page 2)
- (b) In the previous problem, what is the power that reaches the load in terms of the two-port scattering parameters and Γ_L ? Suppose the input is driven with a matched source. ($P_{avs} = P_{in}$)
- (c) Derive the two-port scattering parameters of a three-port where port 3 is terminated in a load with reflection coefficient Γ_L .

Need to find the reduced two-port S-parameter



$$\begin{aligned}V_1^- &= S_{11}V_1^+ + S_{12}V_2^+ + S_{13}V_3^+ \\V_2^- &= S_{21}V_1^+ + S_{22}V_2^+ + S_{23}V_3^+ \\V_3^- &= S_{31}V_1^+ + S_{32}V_2^+ + S_{33}V_3^+\end{aligned}$$

$$V_3^+ = V_3^- \Gamma_L$$

$$\begin{aligned}V_1^- &= S_{11}V_1^+ + S_{12}V_2^+ + S_{13}V_3^+ \\V_2^- &= S_{21}V_1^+ + S_{22}V_2^+ + S_{23}V_3^+ \\0 &= S_{31}V_1^+ + S_{32}V_2^+ + (S_{33}-1/\Gamma_L)V_3^+\end{aligned}$$


$$\begin{aligned}V_1^- &= S_{11}V_1^+ + S_{12}V_2^+ + S_{13}(S_{31}V_1^+ + S_{32}V_2^+)/(1/\Gamma_L - S_{33}) \\V_2^- &= S_{21}V_1^+ + S_{22}V_2^+ + S_{23}(S_{31}V_1^+ + S_{32}V_2^+)/(1/\Gamma_L - S_{33})\end{aligned}$$

$$S_{11_NEW} = S_{11} + S_{13}S_{31}/(\Gamma_L^{-1} - S_{33})$$

Can $\Gamma_L^{-1} = S_{33}$? ⁶

Signal Flow Approach

A systematic method to calculate

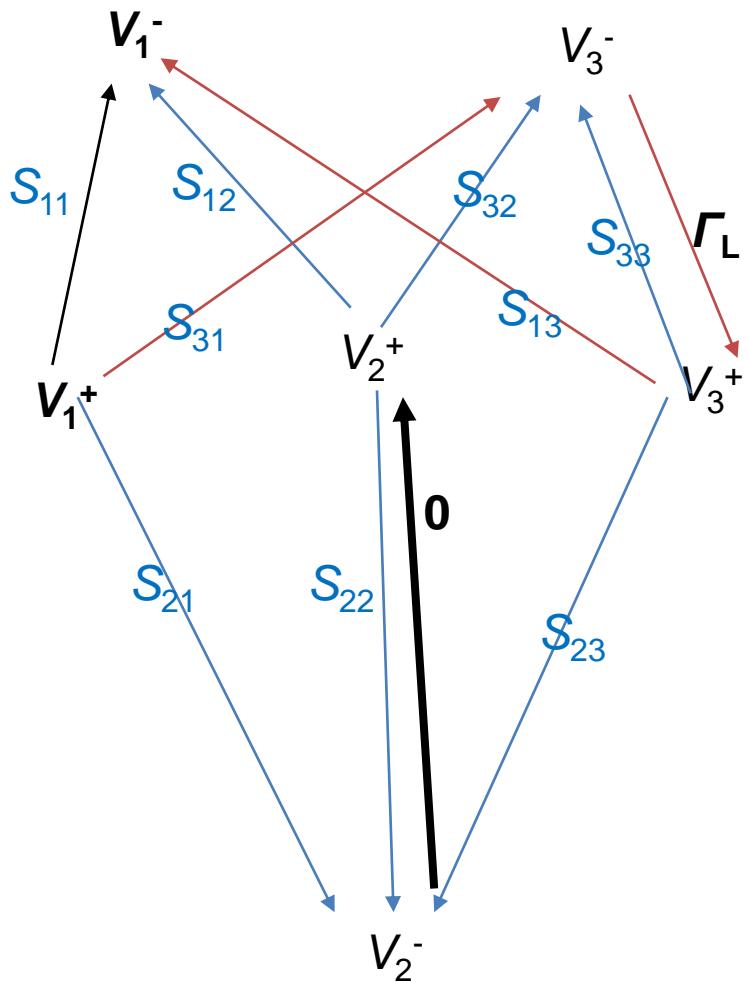

$$\begin{aligned}V_1^- &= S_{11} V_1^+ + S_{12} V_2^+ + S_{13} V_3^+ \\V_2^- &= S_{21} V_1^+ + S_{22} V_2^+ + S_{23} V_3^+ \\V_3^- &= S_{31} V_1^+ + S_{32} V_2^+ + S_{33} V_3^+\end{aligned}$$

$$V_3^- = V_3^+ \Gamma_L$$

- Add the arrow from b3 to a3 with Γ_L
- Since $S_{11_new} = V_1^-/V_1^+$ with $V_2^+ = 0$, add an arrow from V_2^- to V_2^+ with 0
- Find the close loops

$$S_{11_new} = V_1^-/V_1^+ = \text{N/D}$$

$$\text{N} = S_{11}(1 - S_{33}\Gamma_L) + S_{31}\Gamma_L S_{13}(1)$$

$$\text{D} = (1 - S_{33}\Gamma_L)$$

$$\Rightarrow S_{11_new} = S_{11} + S_{31}\Gamma_L S_{13}/(1 - S_{33}\Gamma_L)$$

Signal Flow Approach

Formula [\[edit\]](#)

The gain formula is as follows:

$$G = \frac{y_{\text{out}}}{y_{\text{in}}} = \frac{\sum_{k=1}^N G_k \Delta_k}{\Delta}$$

$$\Delta = 1 - \sum L_i + \sum L_i L_j - \sum L_i L_j L_k + \dots + (-1)^m \sum \dots + \dots$$


where:

- Δ = the determinant of the graph.
- y_{in} = input-node variable
- y_{out} = output-node variable
- G = complete gain between y_{in} and y_{out}
- N = total number of forward paths between y_{in} and y_{out}
- G_k = path gain of the k^{th} forward path between y_{in} and y_{out}
- L_i = loop gain of each closed loop in the system
- $L_i L_j$ = product of the loop gains of any two non-touching loops (no common nodes)
- $L_i L_j L_k$ = product of the loop gains of any three pairwise nontouching loops
- Δ_k = the cofactor value of Δ for the k^{th} forward path, with the loops touching the k^{th} forward path removed. *





2. (a) Assume $Z_0 = 50\Omega$. Using Smith Chart to find ρ_L for a load impedance $Z_L = 25 + 30j\Omega$. **Use Z chart: $Z' = 0.5 + 0.6j$**

- (b) Assume $Z_0 = 50\Omega$. Using Smith Chart to find the load impedance for $\rho_L = 0.5 + 0.1j$.

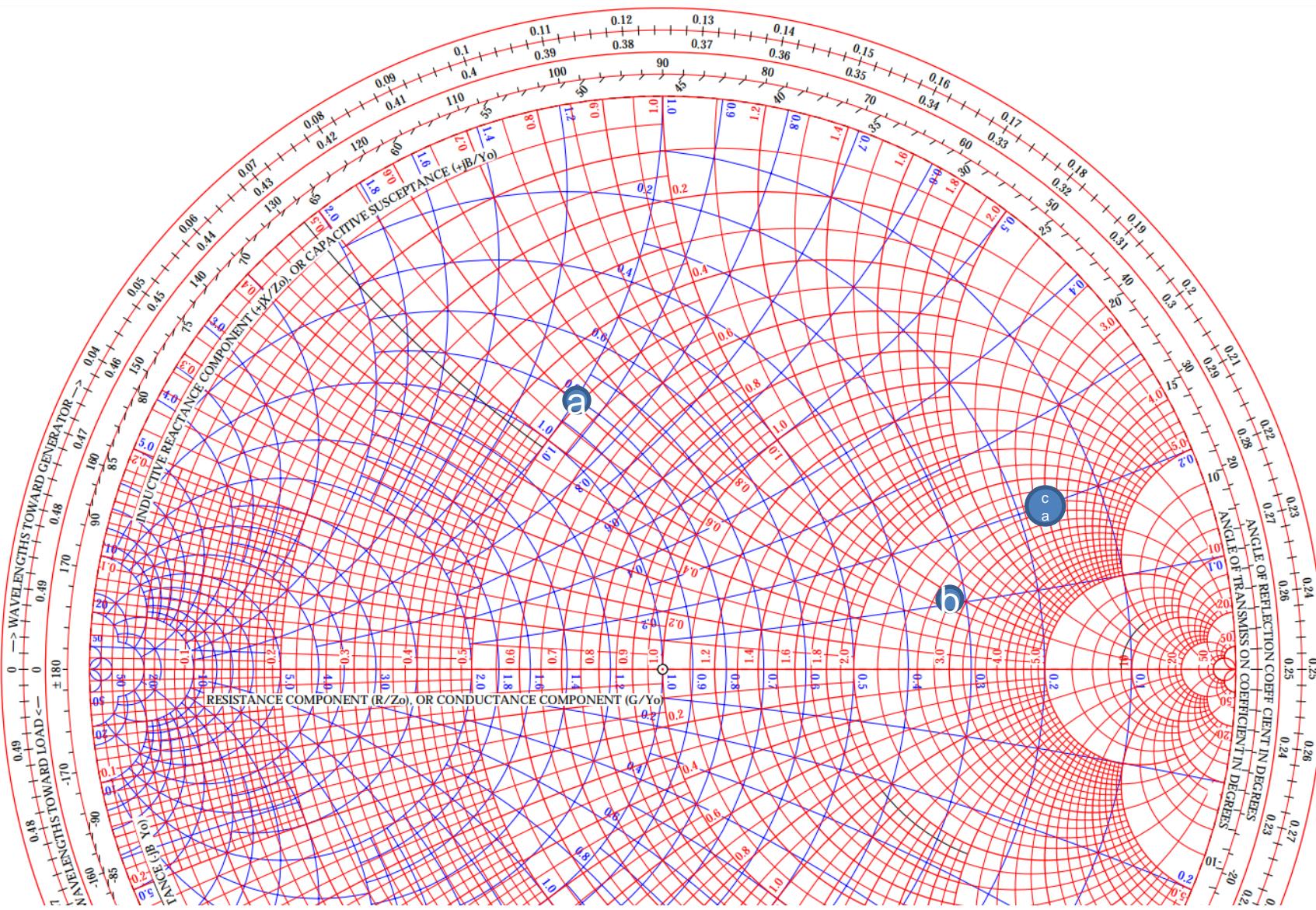- (c) Repeat (a) and (b) with Z_0 changed to 10Ω .



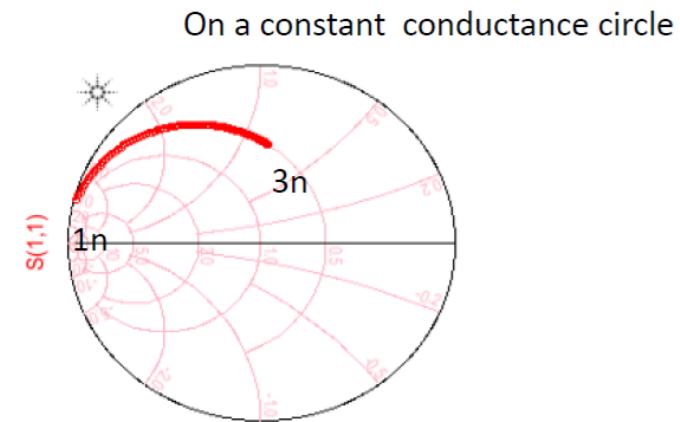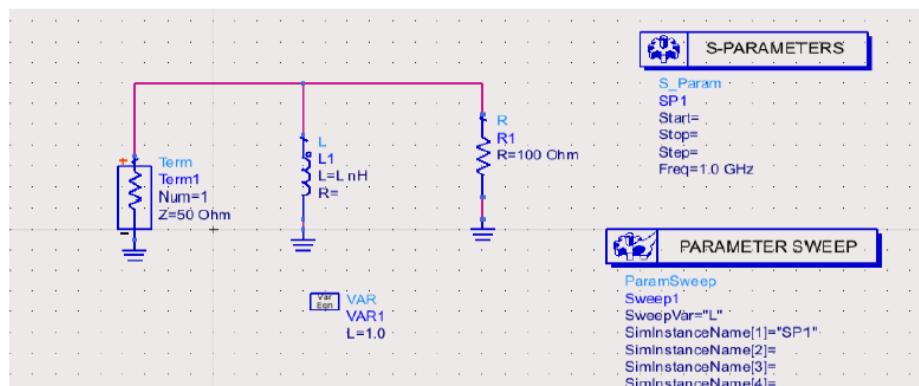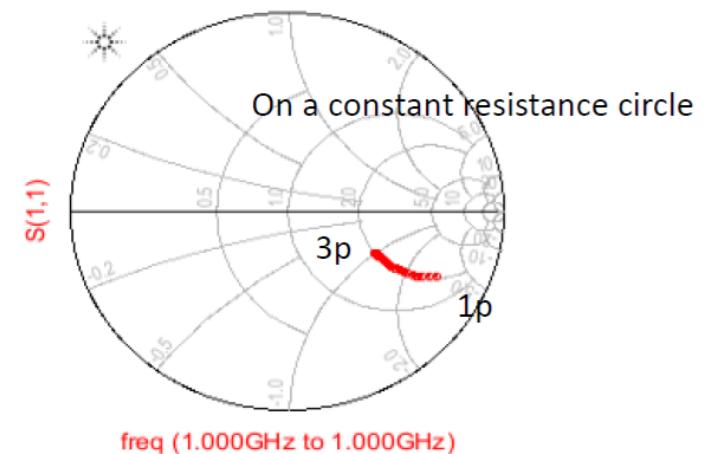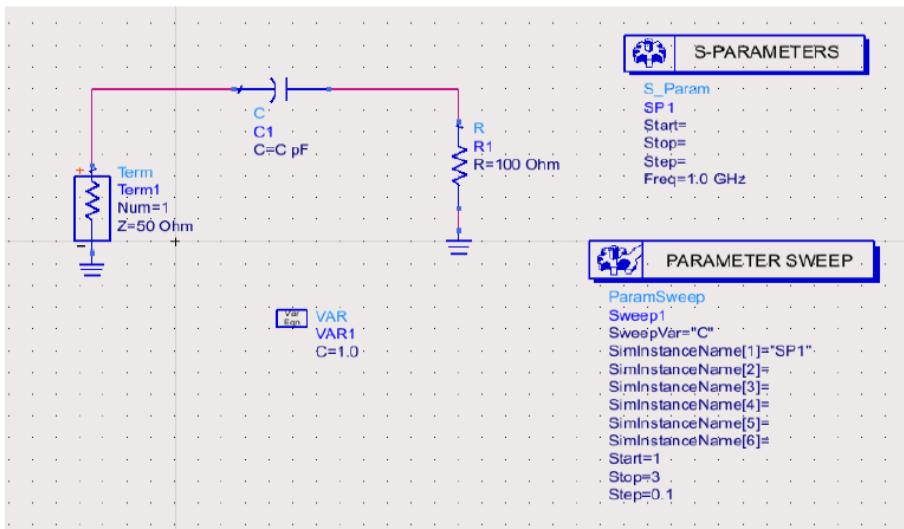(d) For the following two circuits, trace ρ_L on a Smith Chart with $Z_0 = 50\Omega$.





- $R=100$ circle and $G=0.01$ circle have one intersection
- All constant resistance circles pass 1 and all constant conductance circles pass -1



Series and Parallel Transmission line


T-line char. impedance = Z_0
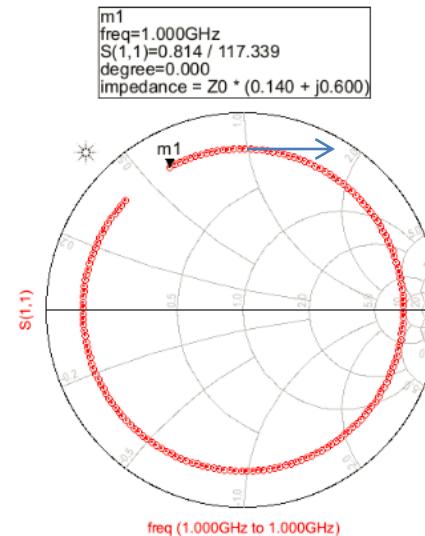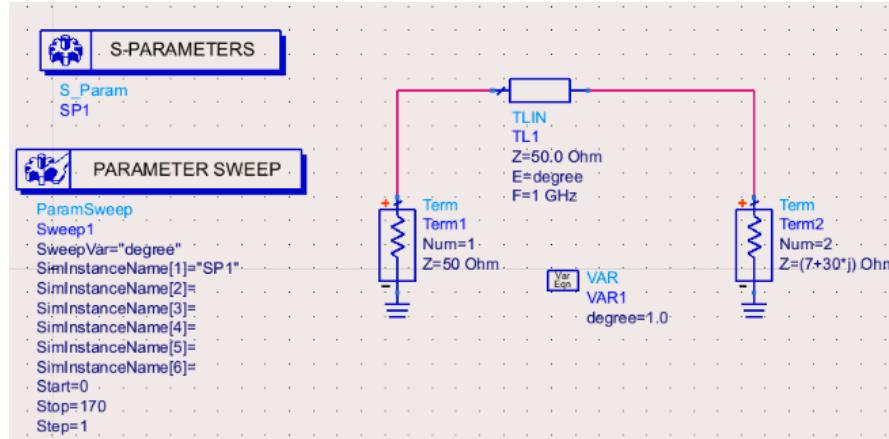
$$Z_{in} = Z_{L,Z_0} \times \exp(-2j\beta l)$$



Same magnitude
clockwise

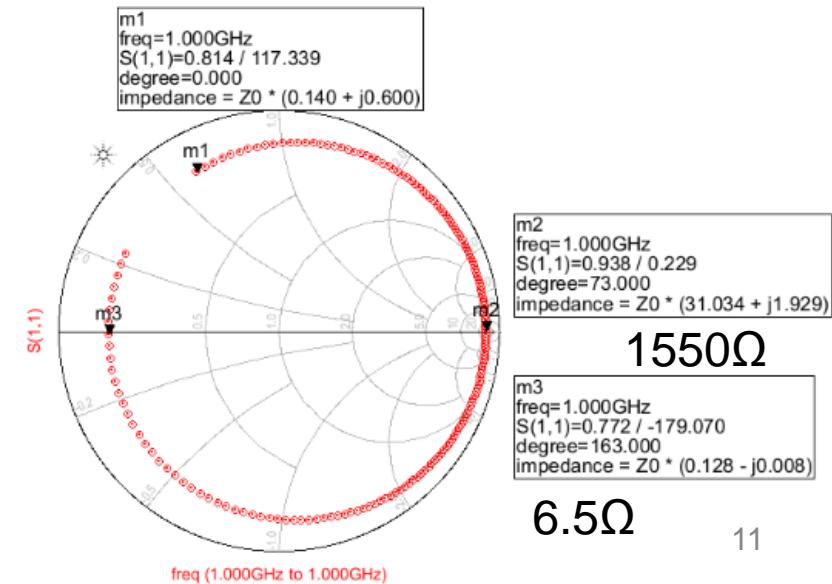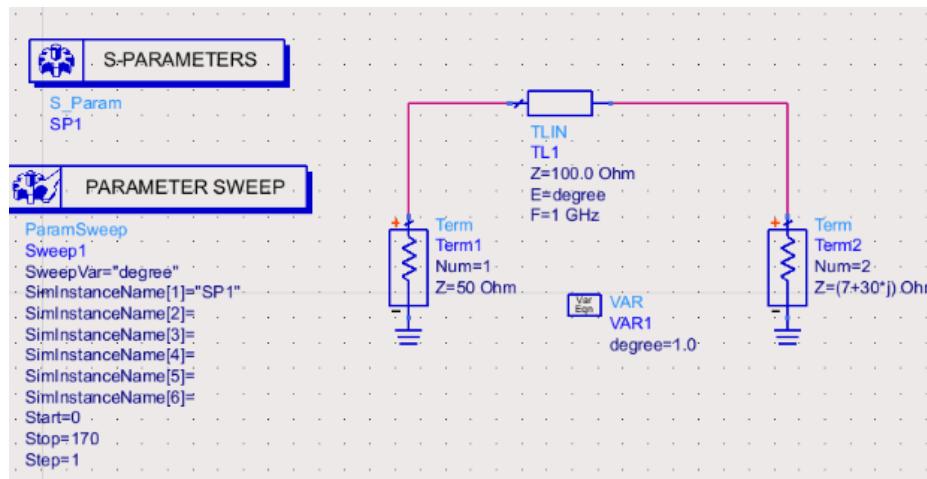


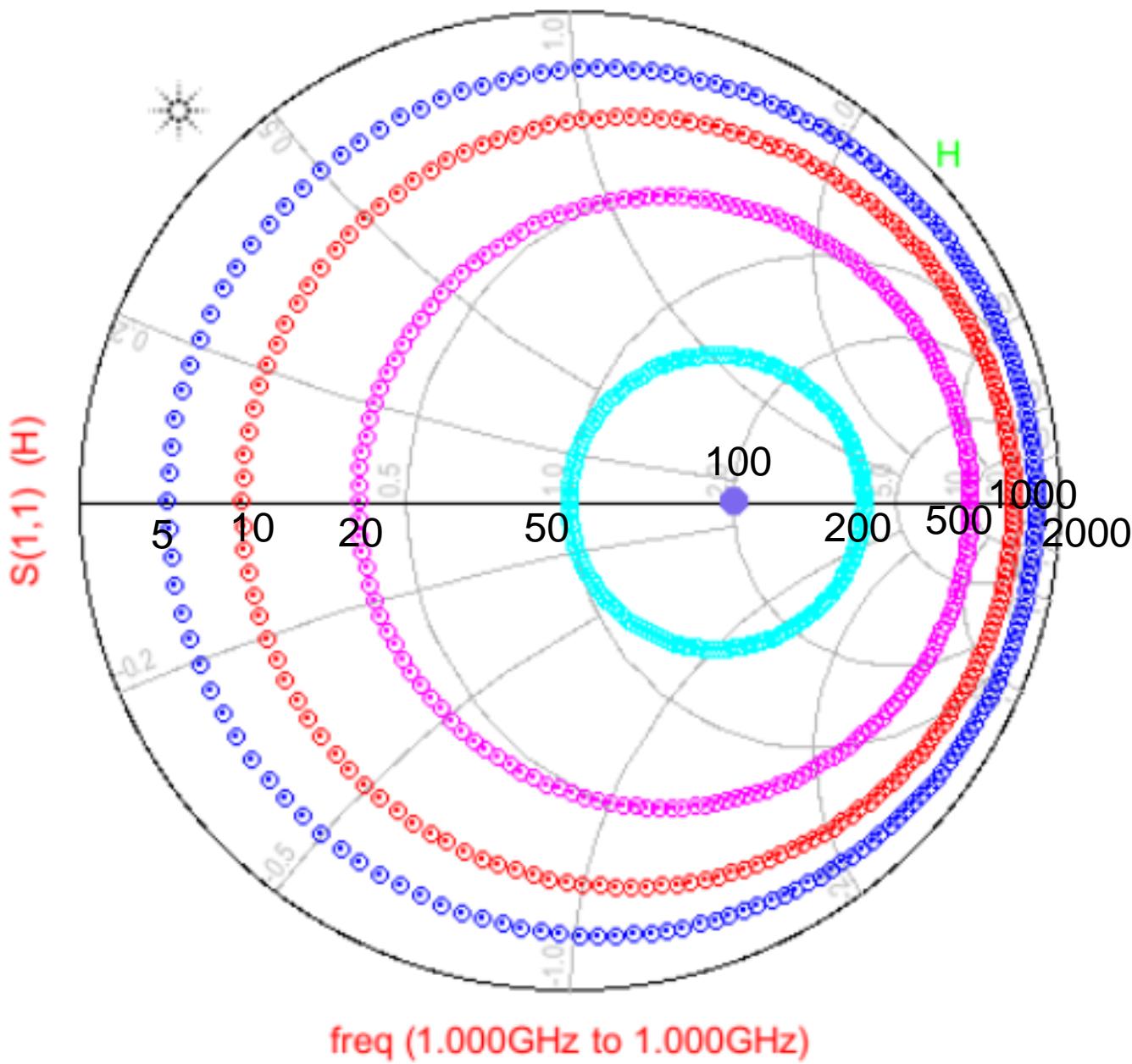



50Ω Smith Chart
100Ω series T-line

- The S_{11} trajectories are also circles
- The accurate position is difficult to find using Smith Chart

HW4.4(d)

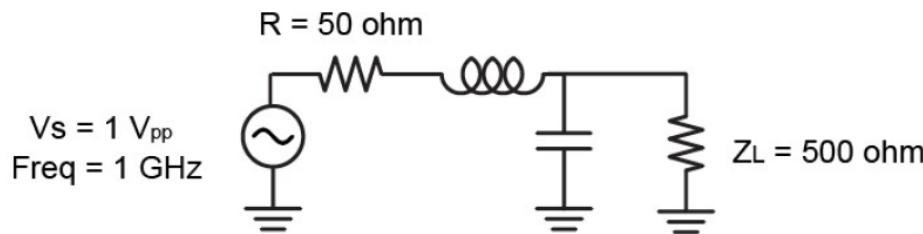


Old
Slides

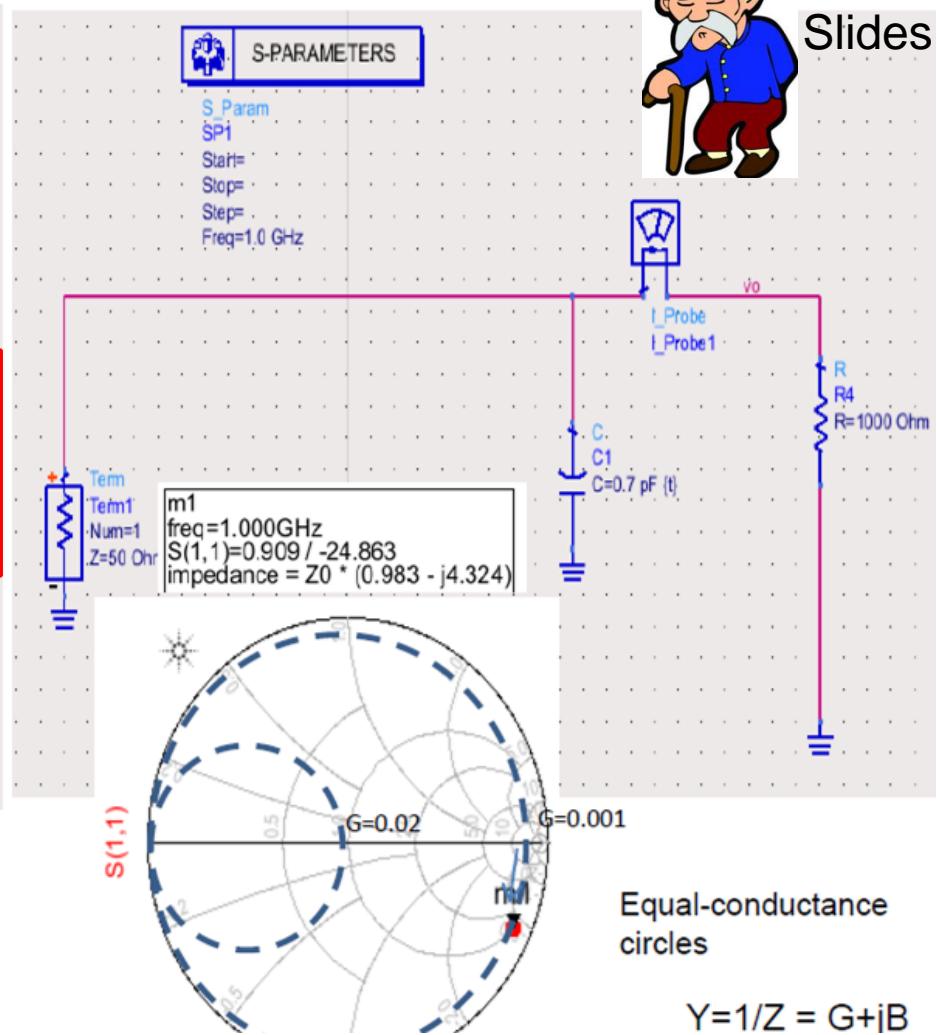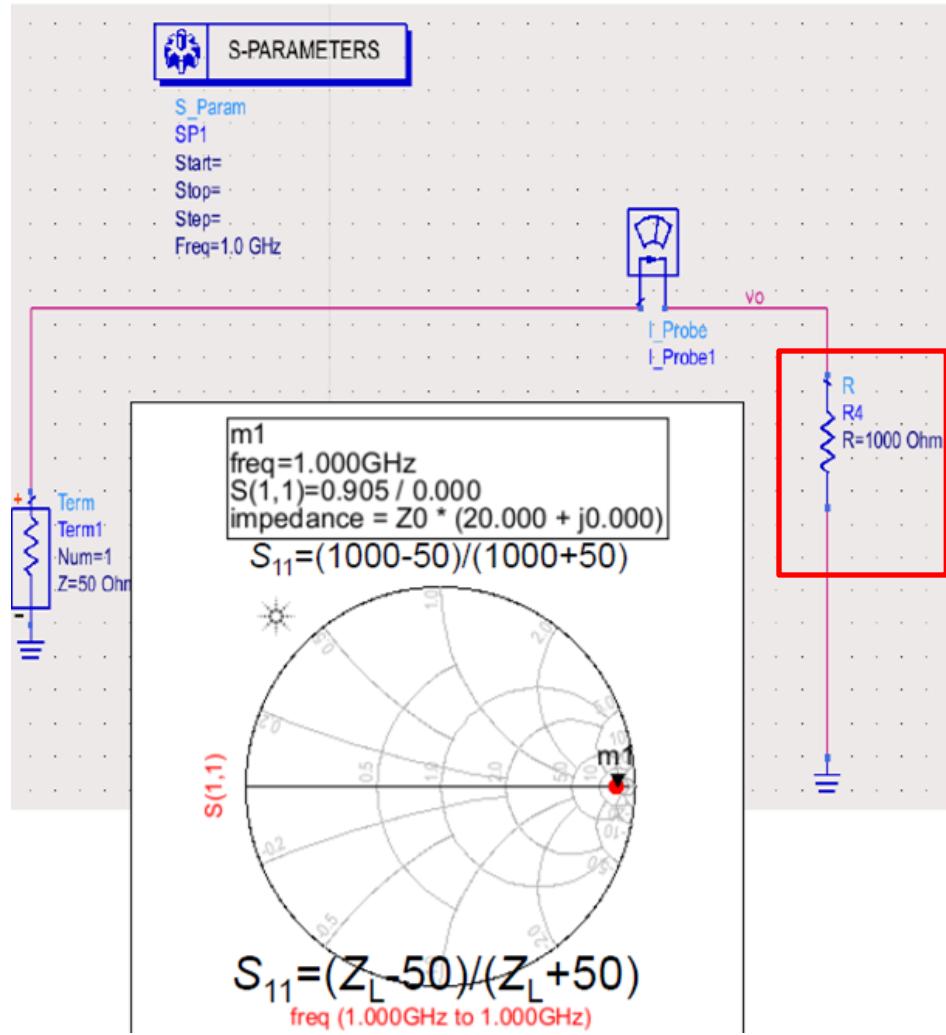




Old Slides

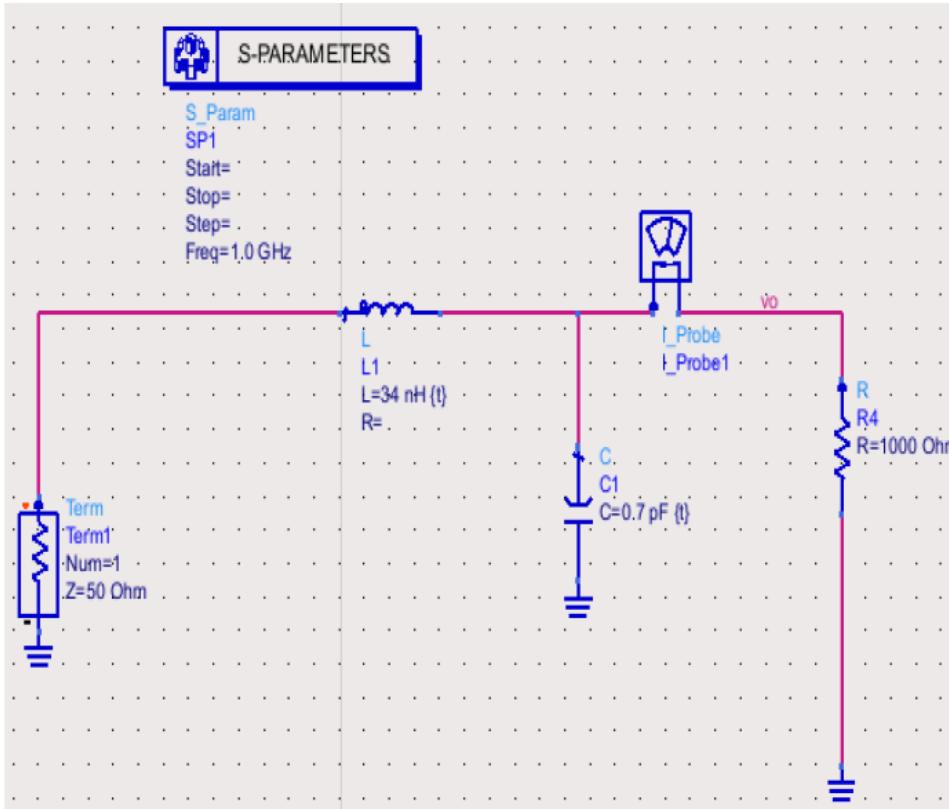

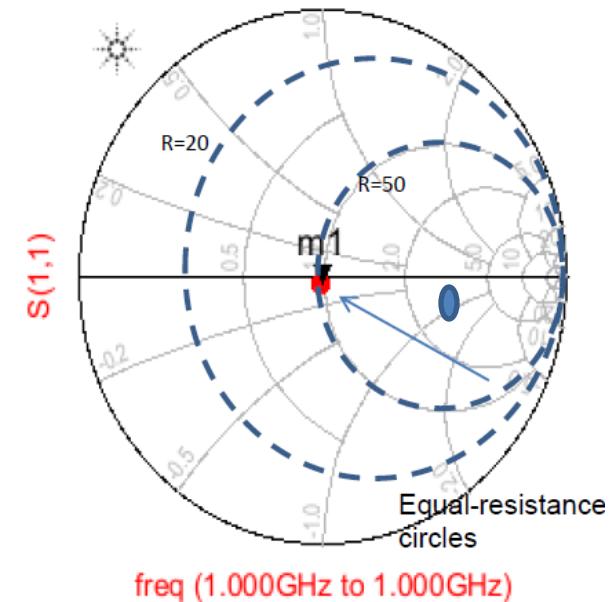
m1
freq=1.000GHz
 $S(1,1)=0.027 / -106.817$
impedance = $Z_0 * (0.983 - j0.051)$




- Shunt-series matching
- First step: Move S_{11} on Smith Chart (along the equal-conductance circle) to a point on the equal-resistance circle with $R = 50$
- Second step: Move S_{11} on Smith Chart (along the equal-resistance circle) to $S_{11} = 0$
- The shunt component can be an inductor, but then the series one must be a capacitor

Can we put a series component first ???

Determine the Component Values

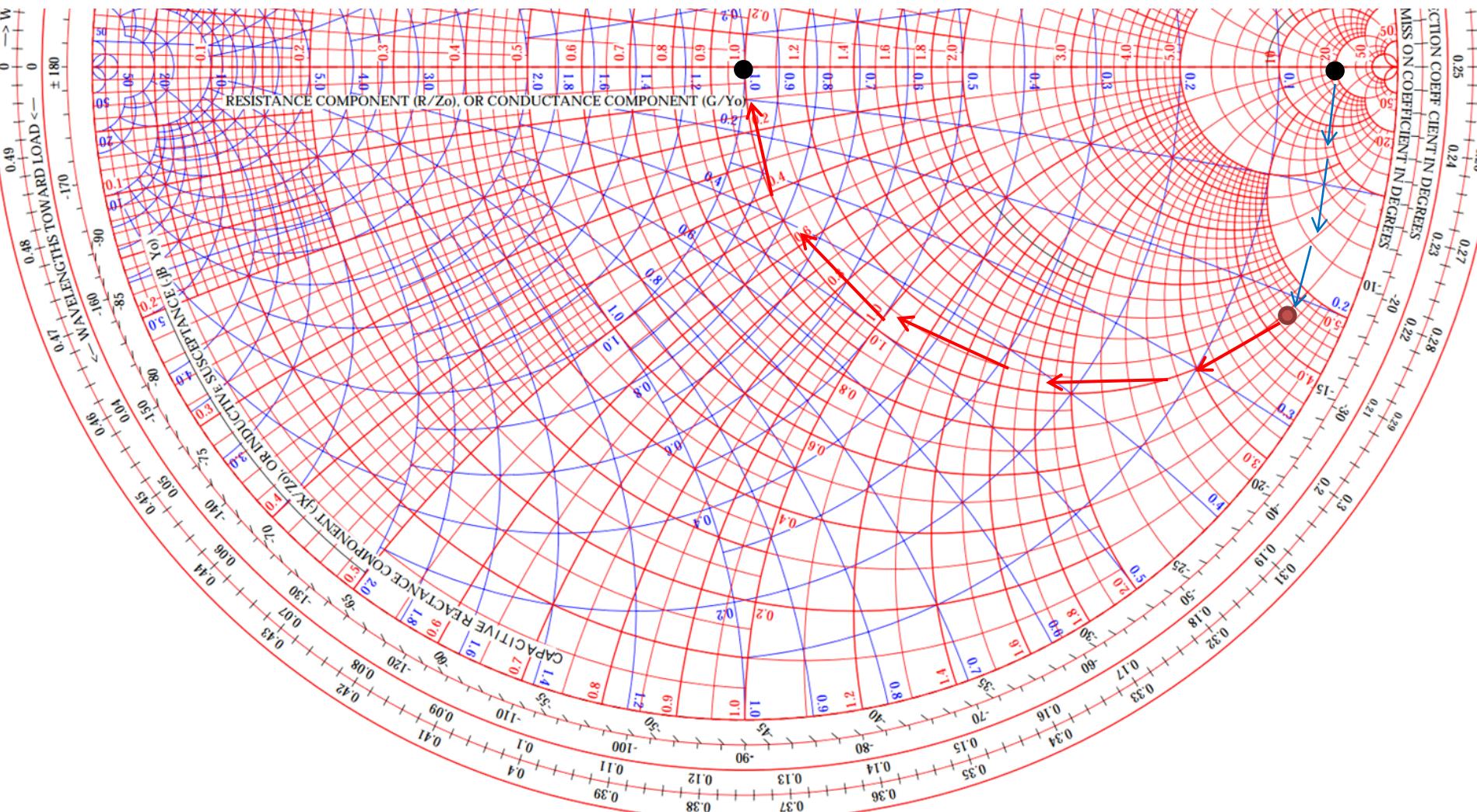

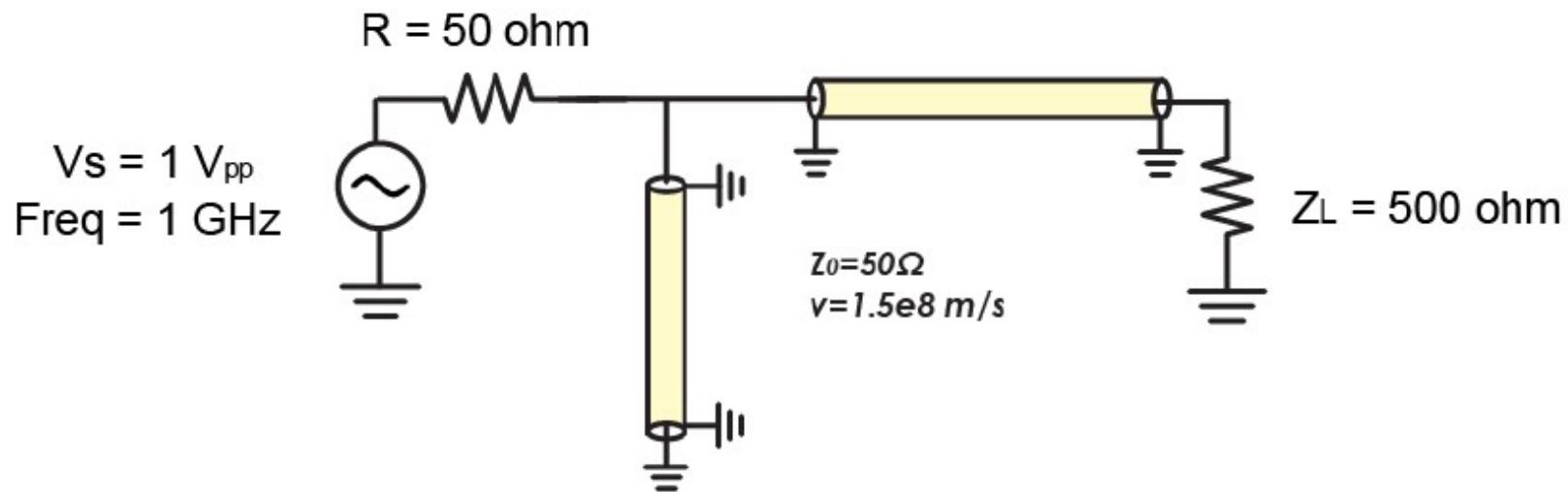First Step: Add $B' \approx 0.22j \Rightarrow B = 0.22^*Y_0 = 0.0044j \text{ S} \Rightarrow 2\pi f C = 0.0044 \Rightarrow C = 0.70 \text{ pF}$ 15
 Second Step: $X \approx -4.5j \Rightarrow X = -4.5^*Z_0 = -225j \Omega \Rightarrow 2\pi f L = 225 \Rightarrow L = 35 \text{ nH}$




(f) (242A only) Alternatively, the impedance matching network can be designed by using transmission lines, as illustrated above. What are the length of the two lines?

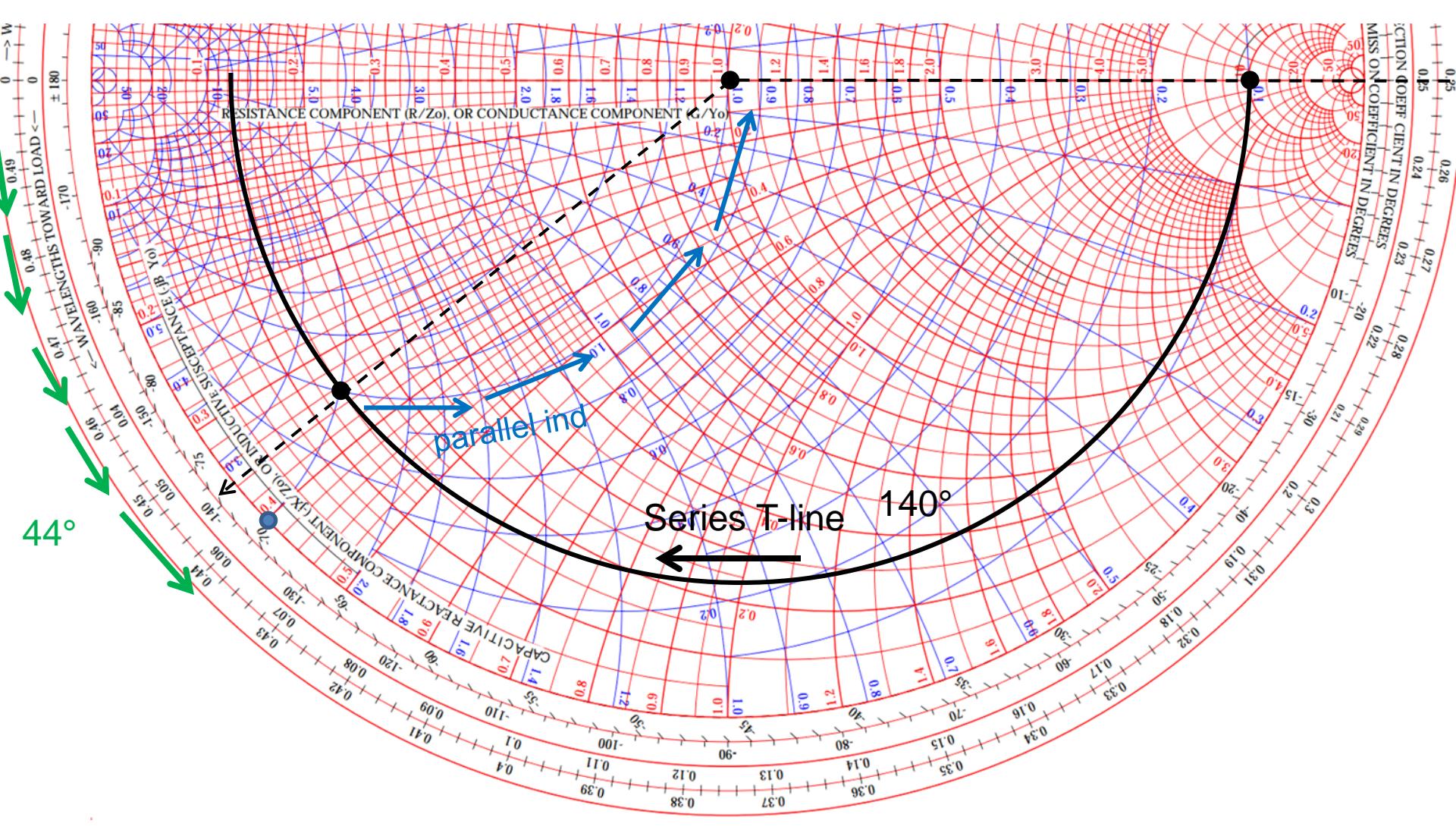(g) (242A only) Repeat (f) with Z_0 of the transmission lines changed to 100Ω .



Suggestion: Use Smith Chart with $Z_0 = 100$ is more convenient ($Z_L' = 5$ to $Z_{in}' = 0.5$)



First Step: Add series T-line; travel 140° on Smith Chart \Rightarrow line length $\approx 140/180 * 0.25$ wavelength

Second Step: $B' \approx 2.5j$ so we have to add a parallel inductor with $B' \approx -2.5j$ or $X' = 0.4j$
 \Rightarrow short-circuited line length $\approx 44/180 * 0.25$ wavelength