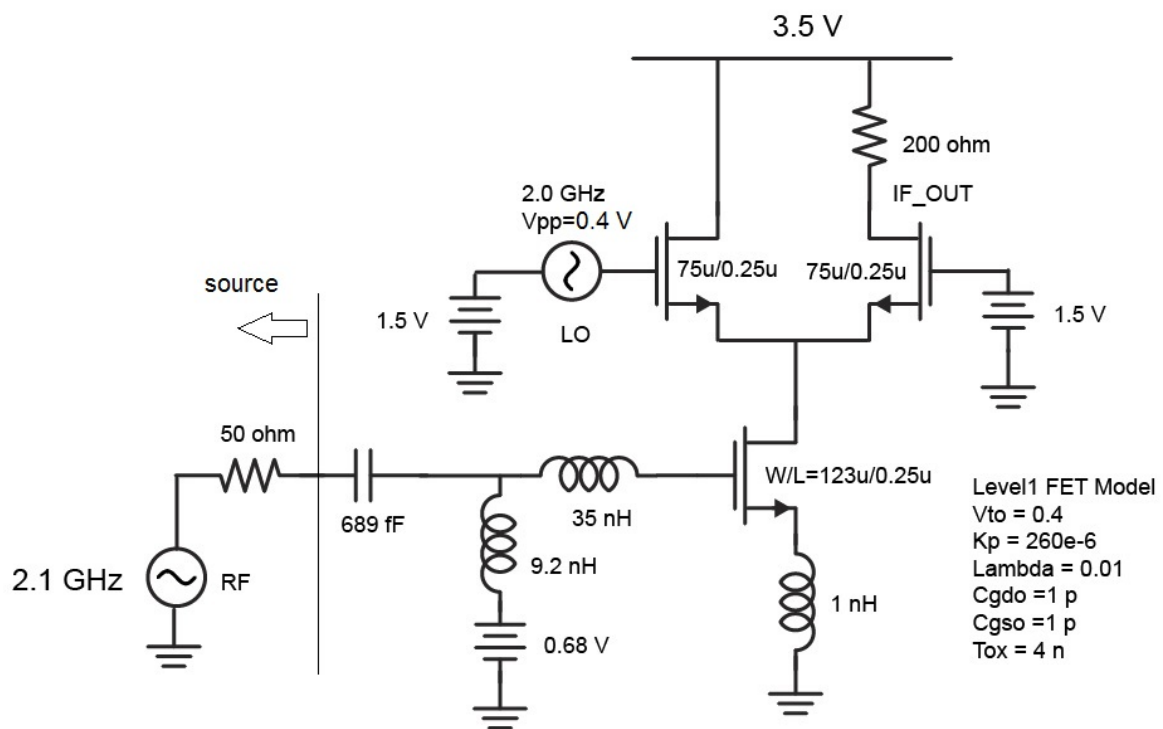


# EE142 Problem Set 10

Vighnesh Iyer

December 1, 2017

## 1 Mixer Analysis




- (a) For the FET mixer shown above with the FET parameters annotated, estimate (calculate) the mixer down-conversion power gain for an input RF signal at 2.1 GHz and LO at 2 GHz. Verify your estimation by ADS simulation.

We do the hand-calculations assuming a long-channel device.


$$\begin{aligned}
 I_d &= \frac{1}{2} K_p \frac{W}{L} (V_{gs} - V_{th})^2 \\
 &= 5 \text{ mA} \\
 g_m &= \frac{2I_d}{V_{ov}} = 0.036 \\
 G_m &= Q \cdot g_m = 2.002 \cdot g_m = 0.072 \\
 I_{tail} &= I_d + v_s \cos(\omega_{RF} t) \cdot G_m \\
 &= 5 \text{ mA} + v_s \cos(\omega_{RF} t) \cdot 0.076 \\
 K &= \frac{1}{2} K_p \frac{W}{L} \\
 i_{d,1,2,diffpair} &\approx \frac{I_{tail}}{2} \pm \sqrt{2KI_{tail}} \frac{v_{id}}{2} \text{ from disc slides} \\
 &= \frac{I_{tail}}{2} + \sqrt{2KI_{dc}} \left(1 + \frac{I_{ac}}{2I_{dc}}\right) \frac{v_{id}}{2} \\
 i_{IF} &= \sqrt{2KI_{dc}} v_s \frac{G_m}{2I_{dc}} \frac{0.2}{4} = 0.007 v_s \\
 v_{IF} &= 200 \cdot i_{IF} = 1.414 v_s
 \end{aligned}$$

The voltage conversion gain is 1.414.

The ADS schematic:

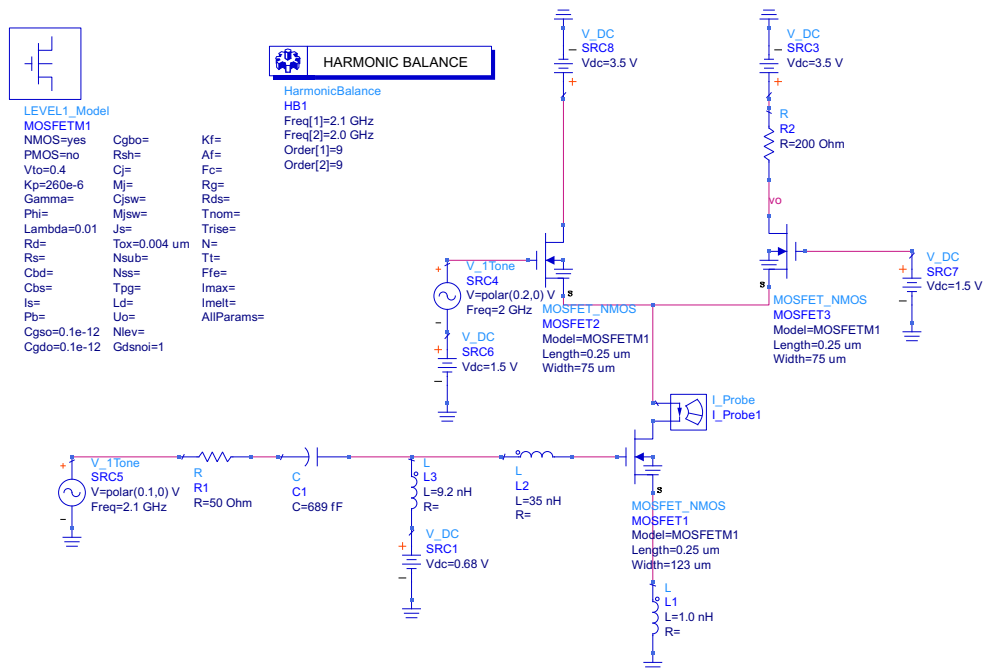

Simulation results:

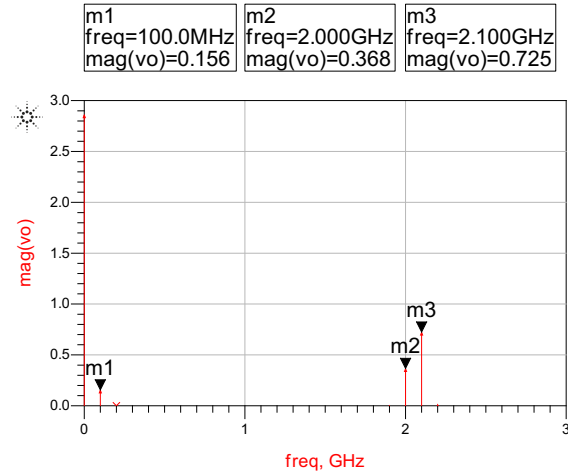

- (b) Calculate the LO and RF leakages at the IF port. Verify your results by ADS simulation.

The RF-to-IF leakage is caused by the Q-booster transconductance of the tail FET which flows through the IF FET.


$$v_{out,RF} = v_s G_m \frac{1}{2} \cdot 200 = 7.17 v_s$$

The LO-to-IF leakage is caused by the differential swing on the IF FET.


$$v_{out,LO} = \sqrt{2KI_{dc}} \frac{v_{id}}{2} \cdot R_L = 0.395 \text{ V}$$

The simulation results closely match the hand calculation.

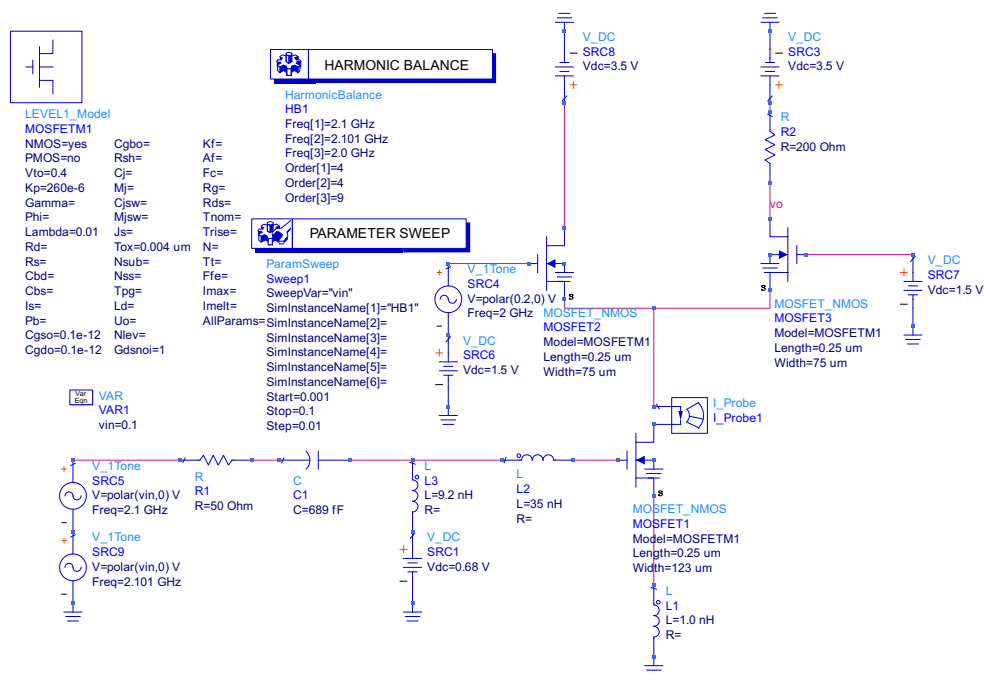- (c) Simulate the mixer IIP3. The ADS schematic:



Simulation results:

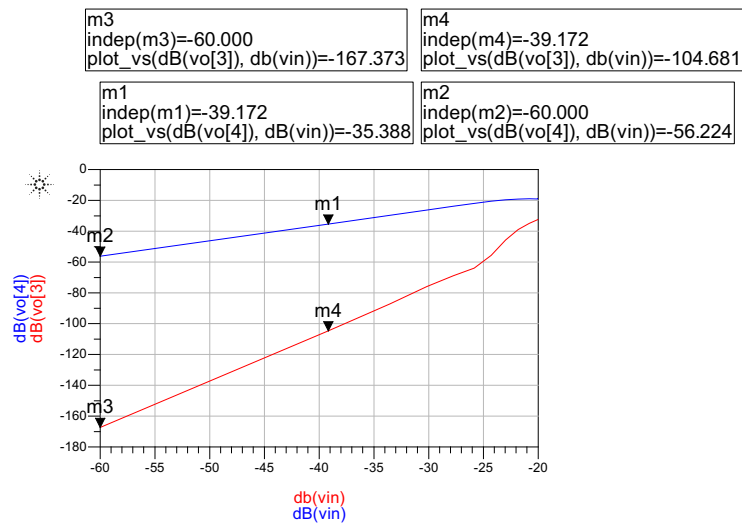

We find that the extrapolated lines intersect at -4.69 dBV.

- Estimate the mixer IIP3 by hand calculation. Unfortunately, I don't have time to look into this part.
- Repeat part (a) to part (c) with the LO drive enhanced to  $0.8V_{pp}$ .

- (f) Roughly estimate the mixer SSB NF. The noise of the FETs and the noise of the load resistance can be excluded. Use an LO drive of  $0.4V_{pp}$ .

## 2 Power Amplifier (PA) Output Waveform and Efficiency

Assume your FET transistor device has the following properties:

- Maximum drain current of  $I_{d,max}$
  - Maximum drain voltage of  $V_{d,max}$
  - Minimum drain voltage of  $V_{d,min}$
  - If  $V_g > 0.5$  then  $I_d = (V_g - 0.5)$  else  $I_d = 0$
  - Input impedance of  $50\Omega$
- (a) Design the transistor drain bias voltage, gate bias voltage, drain bias current, and load impedance (including the load impedance at harmonics of the operation frequency) for Class-A and Class-B power amplifier operations.
- (b) What are the power gains of the two designs?
- (c) Following part(a), draw the time-domain transistor voltage and current waveforms at the peak output for the two designs.
- (d) Following part(a), draw the power delivered to the load, dc power consumption, and the drain efficiency for your Class-A and Class-B designs. The x-axis in your plots should be the input power back-off from the input level corresponding to the maximum output power.
- (e) Following part(a), what are the peak power-added efficiencies (PAE) of your Class-A and Class-B PA designs?