

EE142 Problem Set 6


Vighnesh Iyer

October 14, 2017

1 Design of a 5-GHz Linear Microwave Amplifier

Use the 32nm PTM HP NMOS model with:

V_D	0.9 V
V_G	0.6 V
L	32 nm
W_{tot}	20 μm
$N_{fingers}$	5

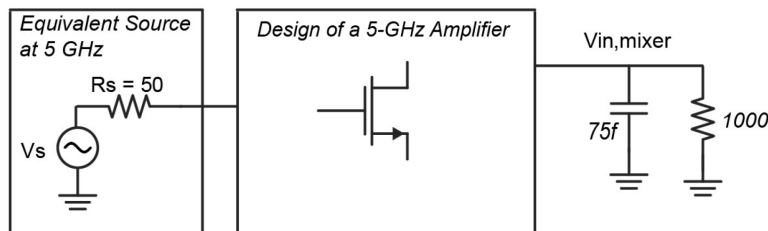

1.1 Mixer Input Impedance

The mixer input is not 50Ω . What will be the problem if this mixer is used as a connector module like the ones sold by MiniCircuits?

The connector modules assume operation in a 50Ω environment. Since the mixer input is 1000Ω , any modules driving it will not be able to achieve the maximum possible power transfer to the mixer. Also, the reflections produced will distort the input waveform to the mixer.

1.2 Stability Factor

Plot the stability factor (k), of this device versus frequency. Is the device unconditionally stable at 1 GHz? If not, find a (passive) device load impedance such that the real part of the device input impedance is negative at 1 GHz.

The stability factor (k) provides a necessary condition for unconditional stability of a 2-port network. It enforces that the input admittance/impedance of the two-port doesn't have a negative real part.

$$Y_{in} = y_{11} - \frac{y_{12}y_{21}}{y_{22} + Y_L}$$

$$Y_{out} = y_{22} - \frac{y_{12}y_{21}}{y_{11} + Y_S}$$

For instability: $\Re(Y_{in}) < 0$ and $\Re(Y_{out}) < 0$

We set up a S-parameter simulation in ADS to calculate the stability factor versus frequency, using the provided transistor sizing and biasing.

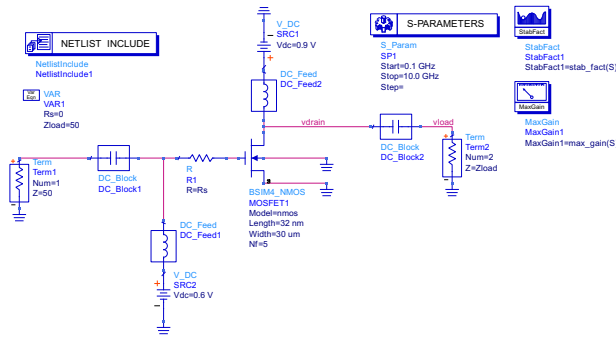


Figure 1: Stability Factor Testbench

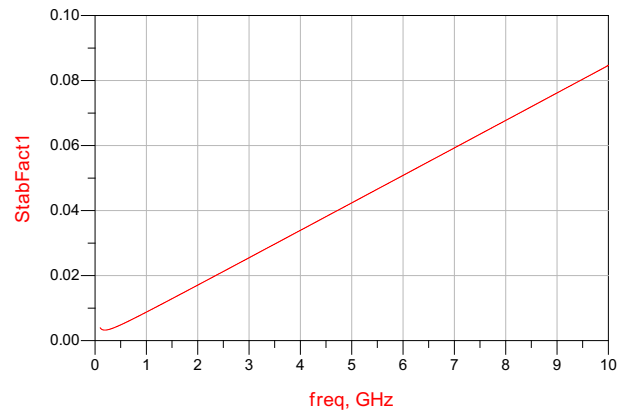


Figure 2: Stability Factor vs. Frequency

The transistor is not unconditionally stable at 1 GHz. To find a passive load impedance that gives a negative real impedance, we can use the stability analysis (circle) feature of ADS.

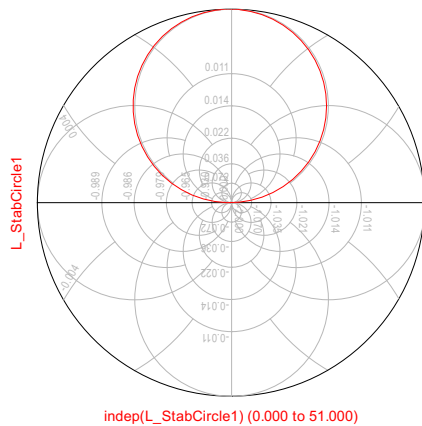


Figure 3: Load Stability Circle (not scaled to unit impedance circle)

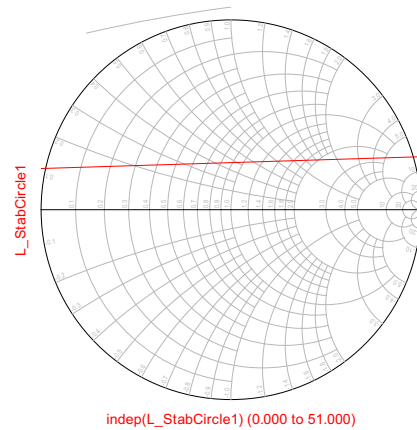


Figure 4: Load Stability Circle (in unit impedance circle)

It can be seen that for sufficiently inductive loads, the transistor isn't stable. For instance a load of $Z_L = 50 + 1.2j$ will lead to a negative input impedance.

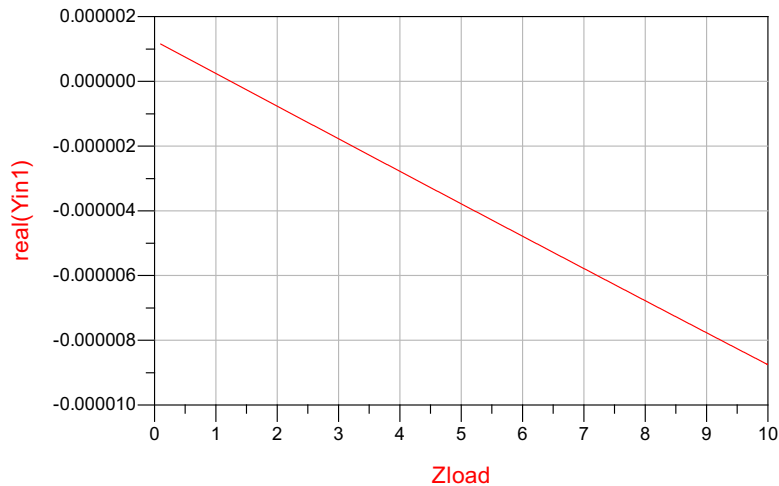


Figure 5: $Z_L = 50 + jZ_{load}$

1.3 Move Pole to Im Axis

Following (b), find the passive source impedance at 1 Ghz that moves the system pole to the imaginary axis.

If the system pole is moved to the imaginary axis, it indicates that the system is marginally stable. This would correspond to when the system poles for this circuit move from possible instability to certain stability by changing the source impedance. We can plot the source stability circle and take a point right on the circle.

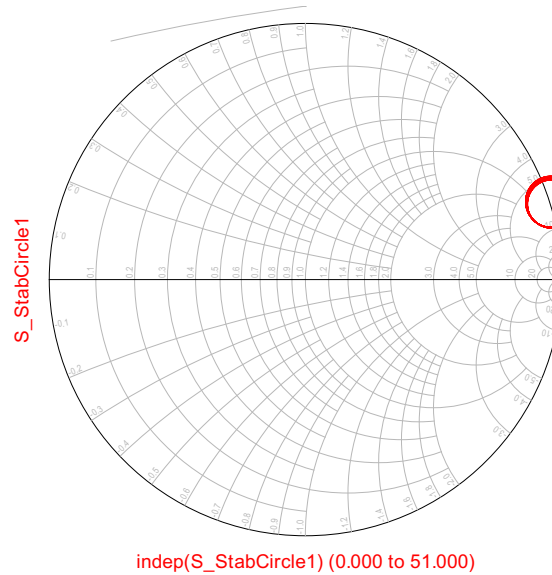


Figure 6: Source Stability Circle

We can immediately read off a value of $Z_s = 1.0 + 5j$ (normalized to 50Ω).

1.4 Stabilize with Series Resistor

Add a series resistor at the transistor gate to make the device unconditionally stable at 5 GHz with $k = 1.2$. What is the resistor value and the maximum transducer gain of this new device (FET+resistor) at 5 GHz? Plot k versus frequency

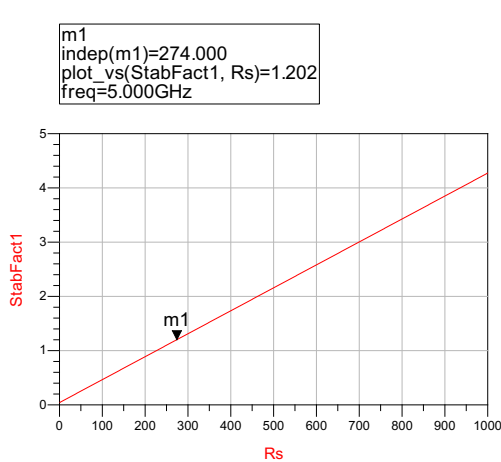


Figure 7: Series resistance sweep vs. K

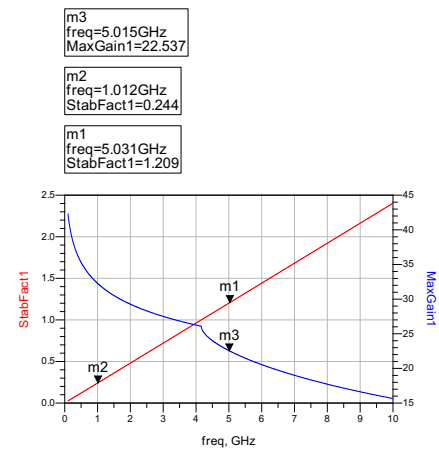


Figure 8: Stability and Gain of Device at 5 GHz

We see an ideal series resistance of 274Ω and a max gain of 22.5 dB.

1.5 Drawbacks of Series Resistance

The new device still has $k < 1$ at 1 GHz, which is undesirable because the load and source impedances of a 5 GHz design are usually not controlled at 1 GHz. Therefore, a pair of undesired source and load impedances at 1 GHz can make the system unstable and the 5 GHz amplifier is no longer useable. Further increasing the series resistor can make $k > 1$ at 1 GHz. What is the main drawback of this approach?

The main drawback is losing maximum transducer gain. As the source resistance increases, it dissipates more power and the overall power gain of the circuit is reduced.

1.6 Max Voltage Gain and Power Gain

We will eventually make $k > 1$ at all frequencies with a better method. Let's focus on the 5 GHz design for now. Assuming the source resistor is 50Ω , what is the voltage gain ($V_{in,mixer}/V_s$) and power gain ($P_{in,mixer}/P_{avs}$) without any matching network?

We use a 50Ω source resistance and the gate resistance from part (d) to stabilize the amplifier at 5 GHz. The load is replaced with the mixer input impedance model.

To use a standard S-parameter termination, we use a parallel to series conversion.

asdf