

# Today's Agenda (Nov. 29)


- PA Waveform and Efficiency: Class A & B
- Maximum Gain and Maximum Power Designs
- PA Load Pull
- PA Design Example

# PA Waveform and Efficiency: Class A


- ❑ Assume the maximum current is 1 A and the supply voltage is 0.5 V
- ❑ Current is  $0.5+0.5\cos(\omega t)$ ; Voltage is  $0.5-0.5\cos(\omega t)$
- ❑ Power from supply:  $0.5 \times 0.5 = 0.25$
- ❑ FET power dissipation:  $\langle \text{Current} \times \text{Voltage} \rangle = \langle 0.25 - 0.25\cos^2(\omega t) \rangle = \langle 0.25 - 0.125 \rangle = 0.125$
- ❑ FET fund. pow. dissipation :  $0.5 \times -0.5/2 = -0.125$  (ac power to load = 0.125)

## Class-A Waveform @ Drain

freq	mag(Pfc1/0.5/I_Probe1.i[0])	Pfc1
1.000 GHz	0.500	-0.125

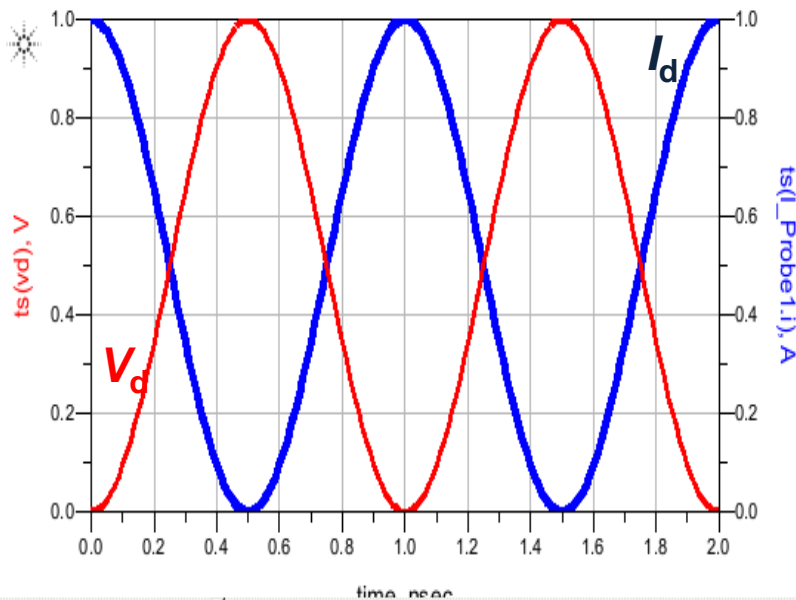


## Class-A Setup

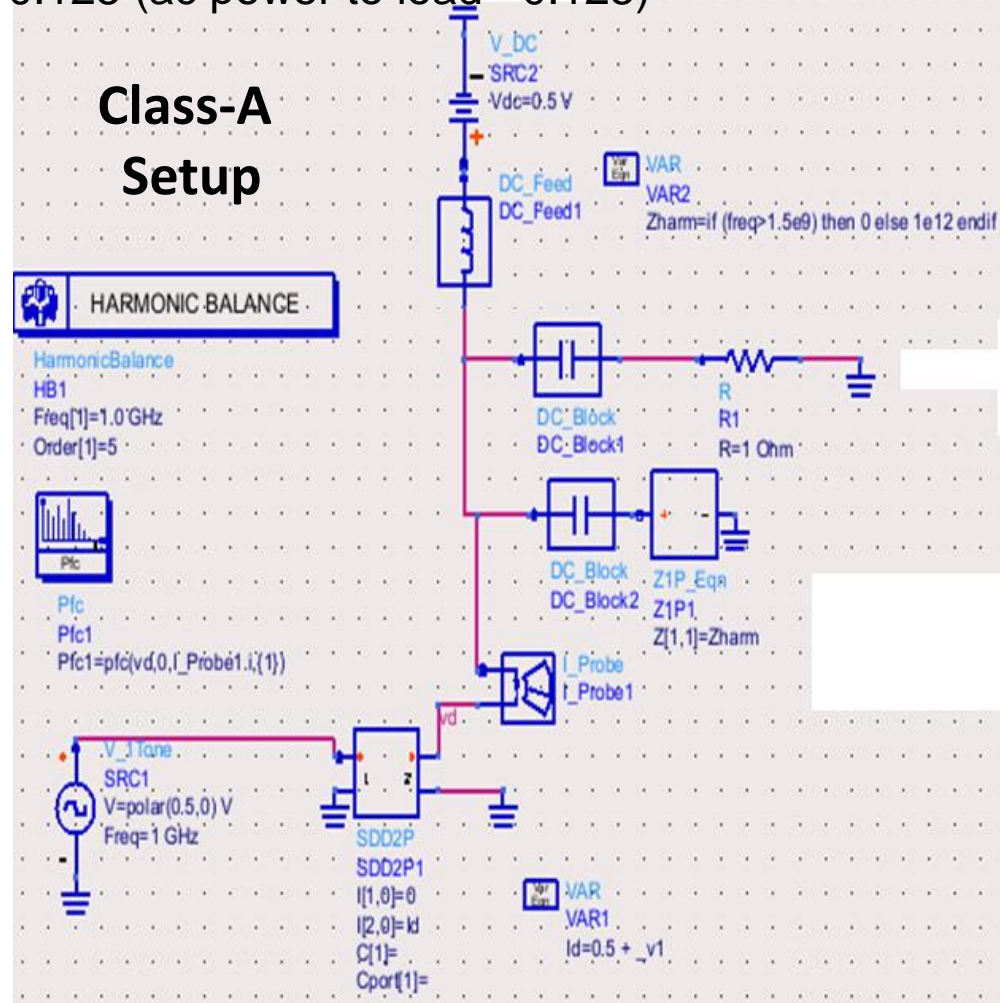

# PA Waveform and Efficiency: Class A

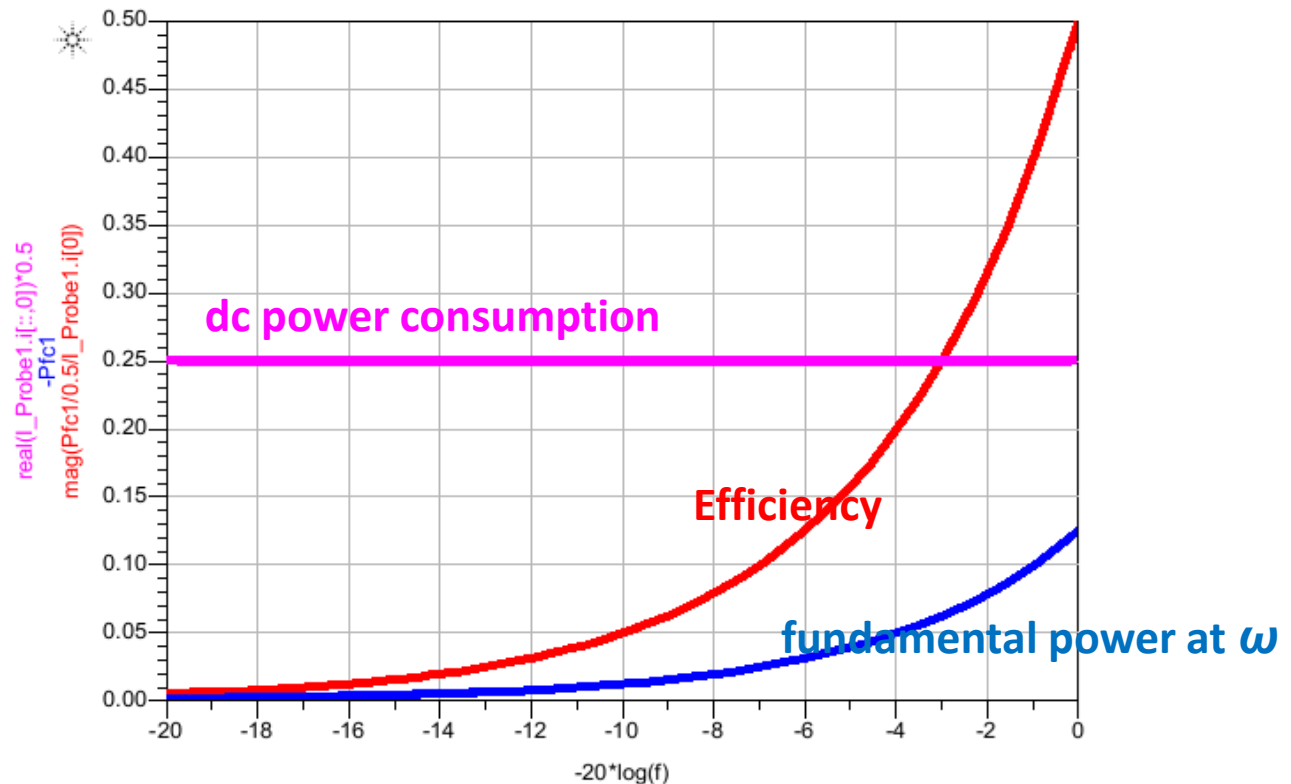
- I. Class-A PA peak power =  $(V_{\max} - V_{\min}) \times I_{\max} / 8$
- II. Class-A PA peak drain efficiency = 50%
- III. @ 6-dB power back-off:
  - a. FET current is  $0.5 + 0.25\cos(\omega t)$ ; FET drain voltage is  $0.5 - 0.25\cos(\omega t)$
  - b. Power from supply =  $0.5 \times 0.5 = 0.25$
  - c. FET power dissipation:  $\langle 0.25 - 0.0625\cos^2(\omega t) \rangle = 0.25 - 0.03125$
  - d. FET fund. pow. dissipation :  $0.25 \times -0.25/2 = -0.03125$  (ac power to load = 0.03125)
  - e. Drain Efficiency (DE) = 12.5%




# PA Waveform and Efficiency: Class B

- ❑ Assume the maximum current is 1 A and the supply voltage is 0.5 V
- ❑ Current is  $(1/\pi) + 0.5\cos(\omega t) + \text{harmonics}$ ; Voltage is  $0.5 - 0.5\cos(\omega t)$
- ❑ Power from supply:  $0.5 \times 1/\pi$
- ❑ FET power dissipation:  $\text{dc}(\text{Current} \times \text{Voltage}) = (0.5 \times 1/\pi - 0.125)$
- ❑ FET fund. pow. dissipation at  $\omega$ :  $0.5 \times -0.5/2 = -0.125$  (ac power to load = 0.125)

## Class-B Waveform @ Drain

 


# Class-B Setup

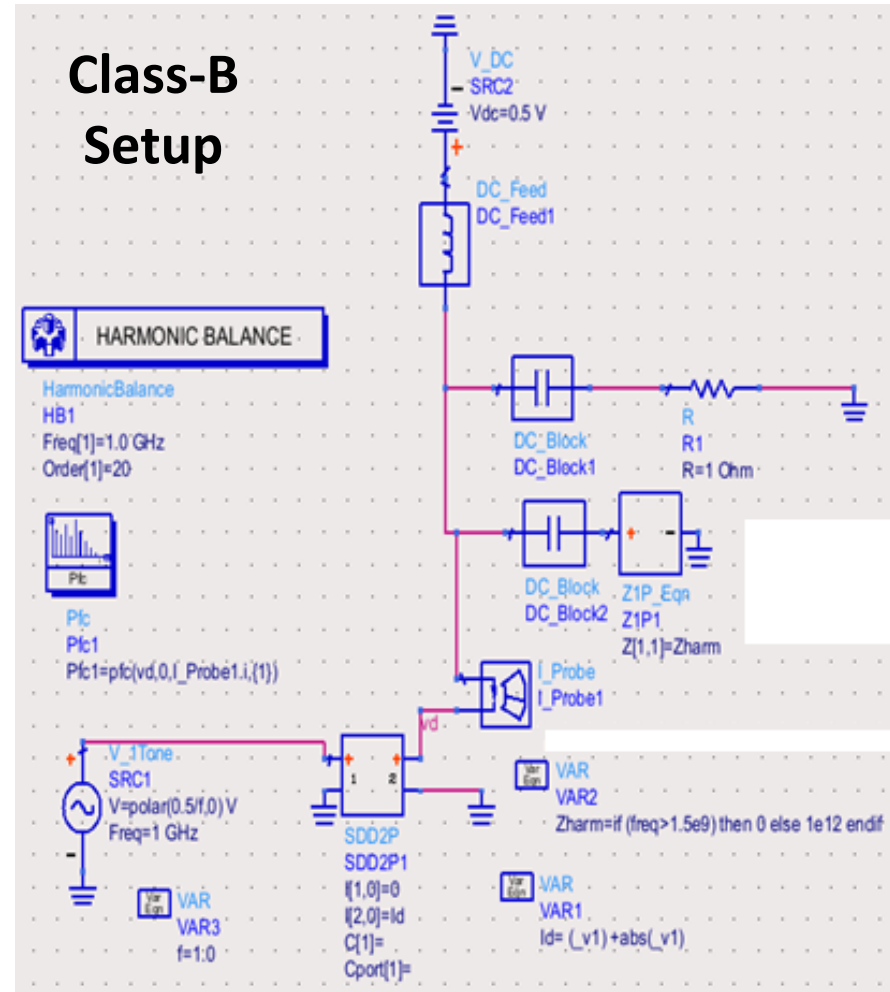

# PA Waveform and Efficiency: Class B

- I. Class-B PA peak power  $= (V_{\max} - V_{\min}) \times I_{\max} / 8$
- II. Class-B PA peak DE = 78.5%
- III. @ 6-dB power back-off:

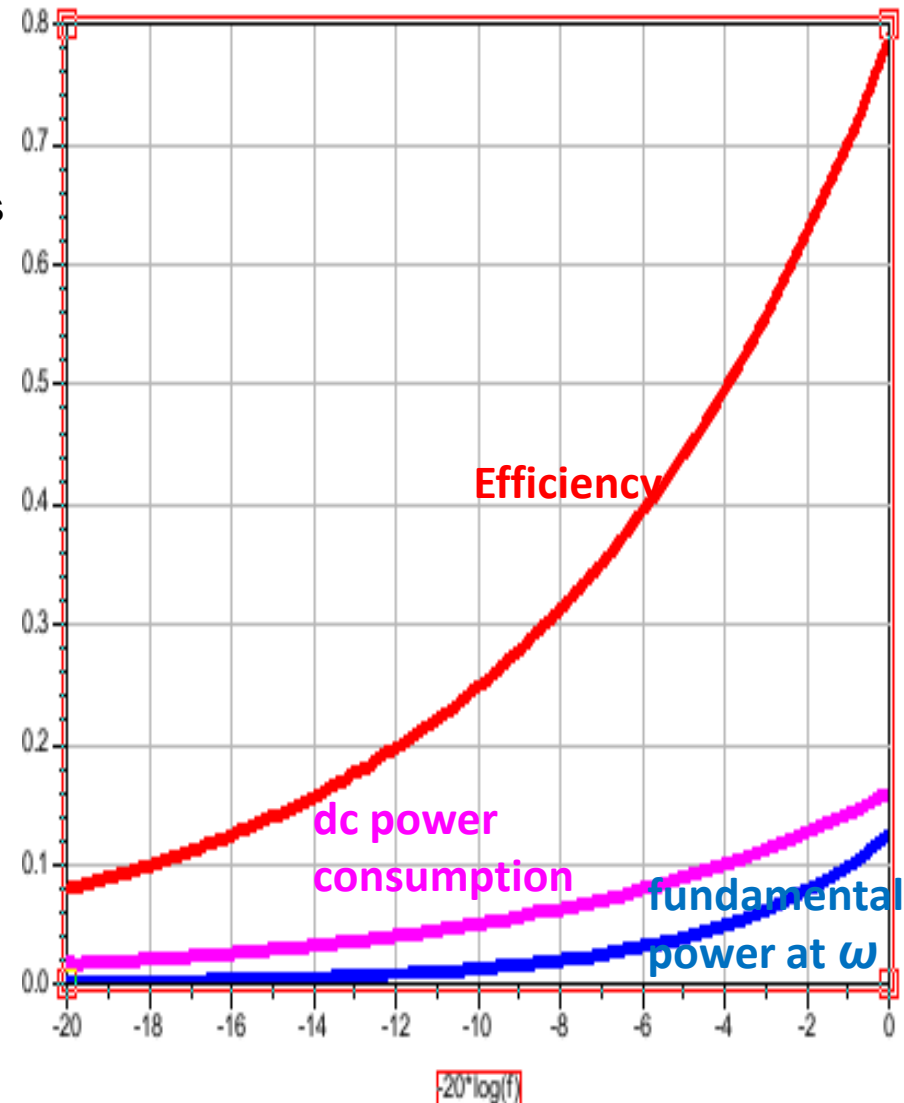
- a. FET Current is  $(0.5/\pi) + 0.25\cos(\omega t) + \text{harmonics}$
- b. FET Drain Voltage is  $0.5 - 0.25\cos(\omega t)$
- c. power from supply =  $0.5 \times 0.5/\pi$
- d. FET power dissipation:  
 $\langle 0.25/\pi - 0.0625\cos^2(\omega t) \rangle = 0.25/\pi - 0.03125$
- e. FET fund. pow. dissipation at  $\omega$ :  
 $0.25 \times -0.25/2 = -0.03125$   
 (ac power to load = 0.03125)
- f. DE = 39.3%



# Design for Max. Gain or Max. Power


- ❑ Load impedance for the max. power does not depend on the small-signal parameters
- ❑ Load impedance for the max. gain depends on the small-signal parameters
- ❑ Consider an illustrative FET device with  $I_d = (V_g - 0.5)(1 + V_d/1000)$  for  $V_g > 0.5$  and  $V_d > 0$   
assume input =  $1000\Omega$ ,  $V_{max} = 10V$ ,  $V_{min} = 0V$ , and  $I_{max} = 1A$

Maximum Power Design,  $R_L = 10$

 

Power =  $5 \cdot 0.5 / 2 = 1.25 \text{ W}$   
 Eff = 50%  
 Gain =  $5 \text{ W} / 0.125 \text{ mW} = 40 \text{ dB}$


Maximum Gain Design,  $R_L = 1000$

 



Power =  $5 \cdot 0.005 / 2 = 12.5 \text{ mW}$   
 Eff = 5%  
 Gain =  $12.5 \text{ mW} / 0.6 \text{ uW} = 56 \text{ dB}$
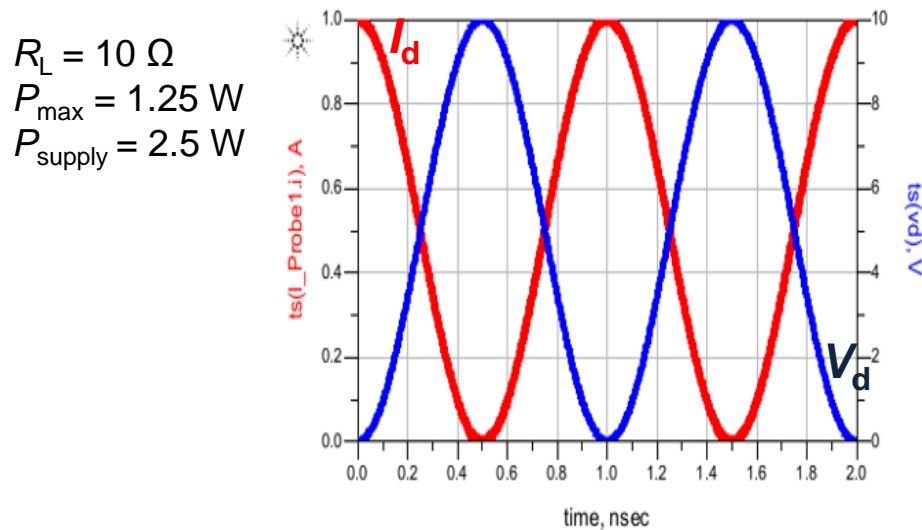
# PA Load-Pull Contours (1/2)


- ❑ The previous example shows the maximum power is achieved with a unique  $Z_L$
- ❑ Ideally, PA power saturates when the drain voltage or current reaches the maximum



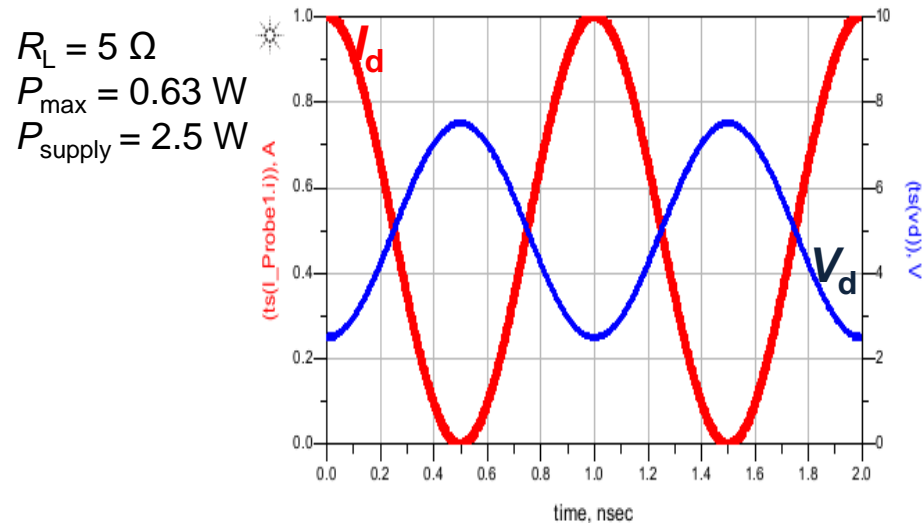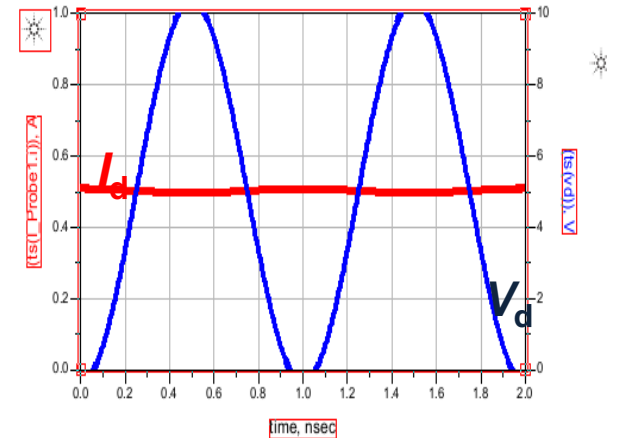$R_L = 1\ \text{k}\Omega$   
 $P_{\max} = 12.5\ \text{mW}$   
 $P_{\text{supply}} = 2.5\ \text{W}$




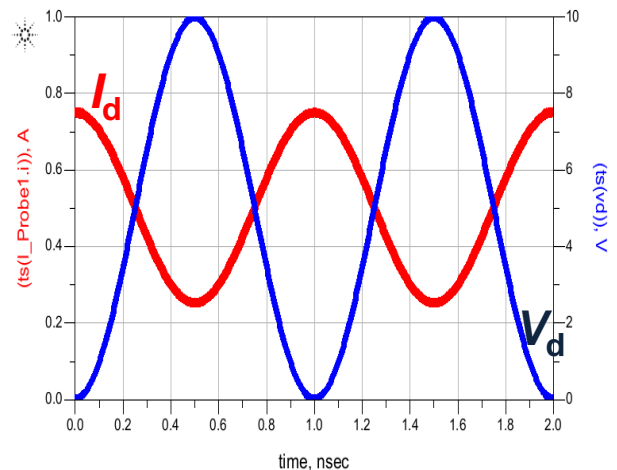$R_L = 20\ \Omega$   
 $P_{\max} = 0.63\ \text{W}$   
 $P_{\text{supply}} = 2.5\ \text{W}$


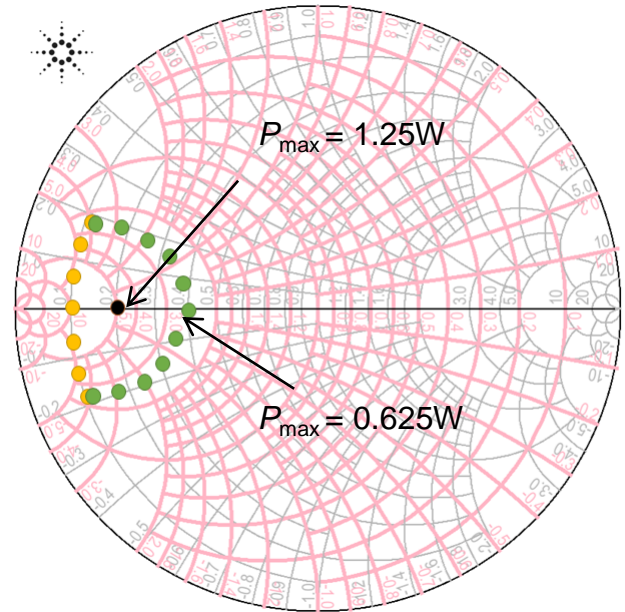
# PA Load-Pull Contours (2/2)

- ❑ Only a unique load impedance (e.g.  $10\Omega$ ) achieves  $P_{\max} = 1.25W$
- ❑ The other (lower)  $P_{\max}$  can be achieved by multiple load impedances
- ❑ Constant- $P_{\max}$  contours can be drawn on Smith Chart to help PA designs



Ex. Load Impedances for maximum power 3-dB lower than 1.25W ( $P_{\max} = 0.625W$ )

**If current-limited:**

$$0.5 \cdot \text{Real}\{0.5A \times 0.5A \times (R+jX)\} = 0.5 \times 1.25 W$$

$$\Rightarrow R = 5$$

$$0.5A \times |Z| < 5 V \Rightarrow |Z| < 10$$

**If voltage-limited:**

$$0.5 \cdot \text{Real} [5V \times 5V / (R+jX) ] = 0.5 \times 1.25 W$$

$$\Rightarrow \text{Real} [1/(R+jX) ] \equiv G = 0.05$$

$$0.5A \times |Z| > 5 V \text{ or } |Y| < 0.1$$


**The two branches form a closed loop!!!**




# PA Design Example (1/2)

Design a pseudo-differential PA with ideal differential-to-single-ended transformer at 2.4 GHz under 0.9 V supply using 32 nm PTM model. Satisfy the following specifications: (1) Power Gain > 15 dB, (2) **Output P1dB = +20 dBm**. (3) Drain Efficiency at Output P3dB > 30%.

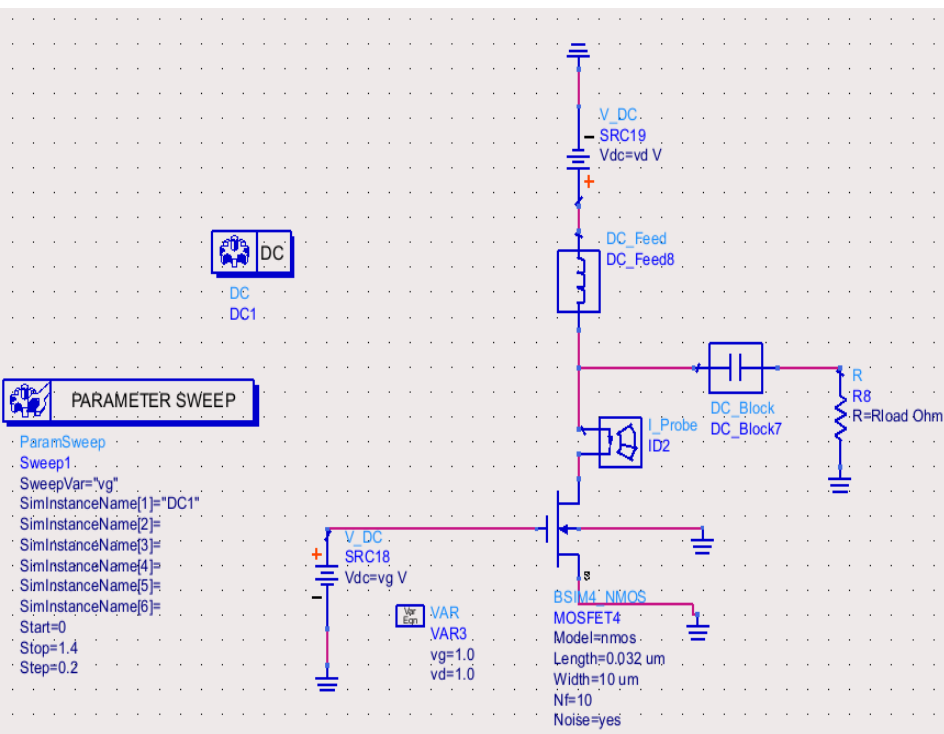**First Step: Estimate the required device size, bias, and load resistance**




Test Device Size = 10 μm

 


# PA Design Example (2/2)

$|S_{11}|$  vs input power

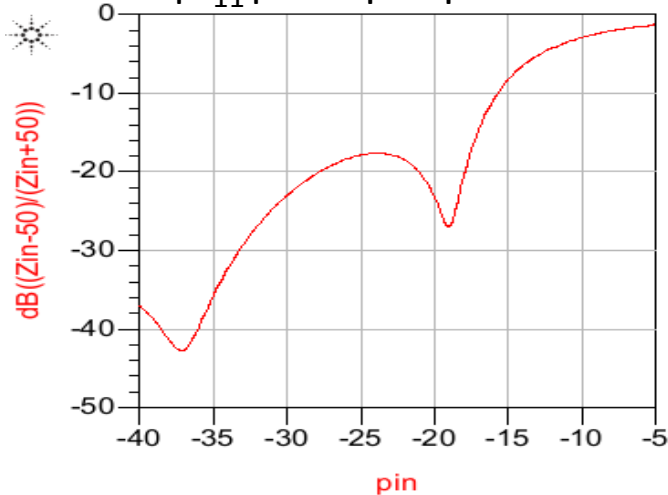

The device is sized (with the load impedance) to generate the required power

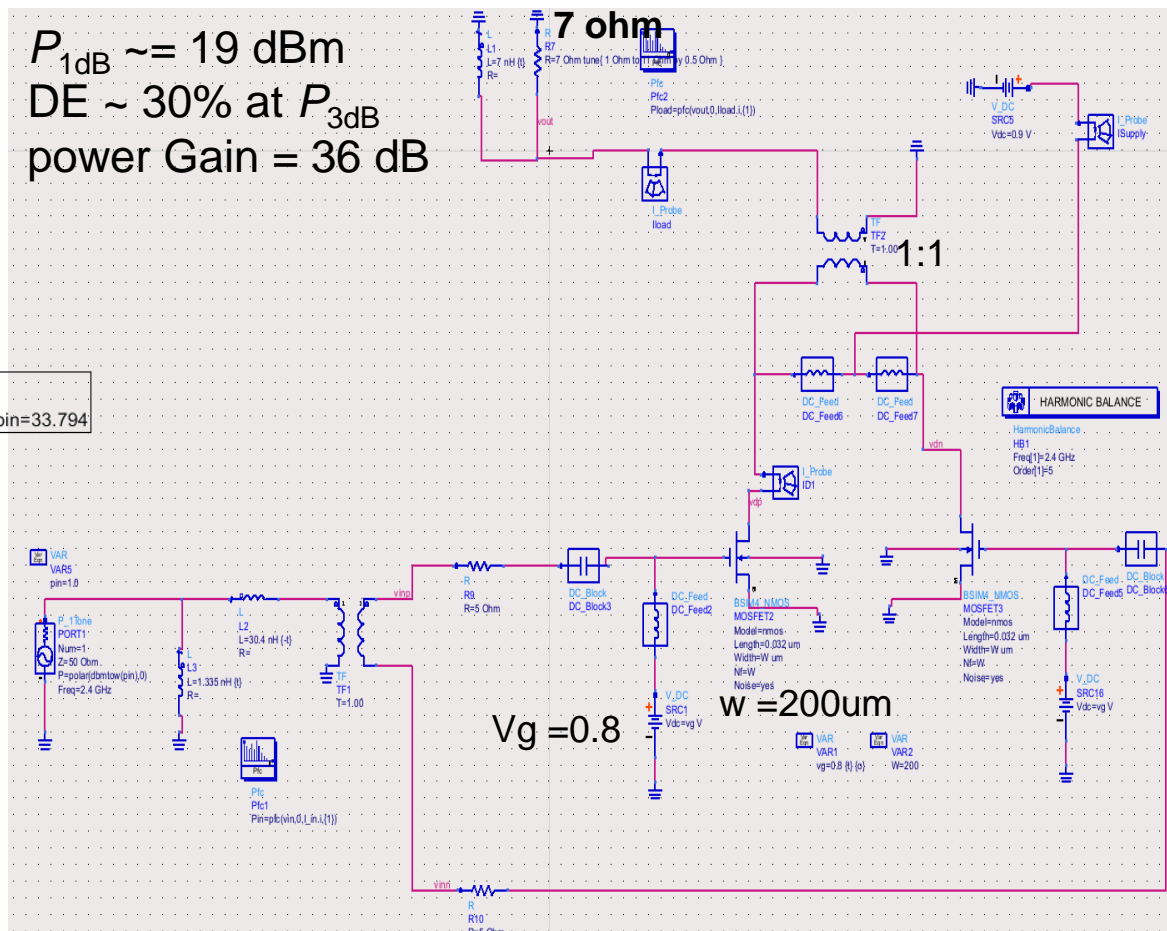
$P_{1dB} \approx 19 \text{ dBm}$   
 $DE \sim 30\% \text{ at } P_{3dB}$   
 power Gain = 36 dB



m2  
pin=-40.000  
10\*log(Pload\*1000)-pin=36.793

m6  
pin=-17.000  
10\*log(Pload\*1000)-pin=35.661

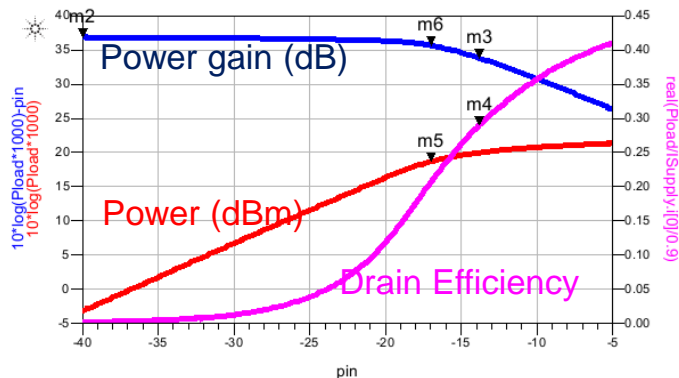m3  
pin=-13.800  
10\*log(Pload\*1000)-pin=33.794



m5  
pin=-17.000  
10\*log(Pload\*1000)=18.661

m4  
pin=-13.800  
real(Pload/Supply.i[0]/0.9)=0.290

# DE and PAE

- ❑ Drain Efficiency = Output Power/ Supply Power
- ❑ Power Added Efficiency (PAE)  
= (Output Power – Input Power)/ (Supply Power)  
= DE × (1- Power Gain<sup>-1</sup>)
- ❑ PAE is more important than DE  
in most cases

The most important figure in a PA work

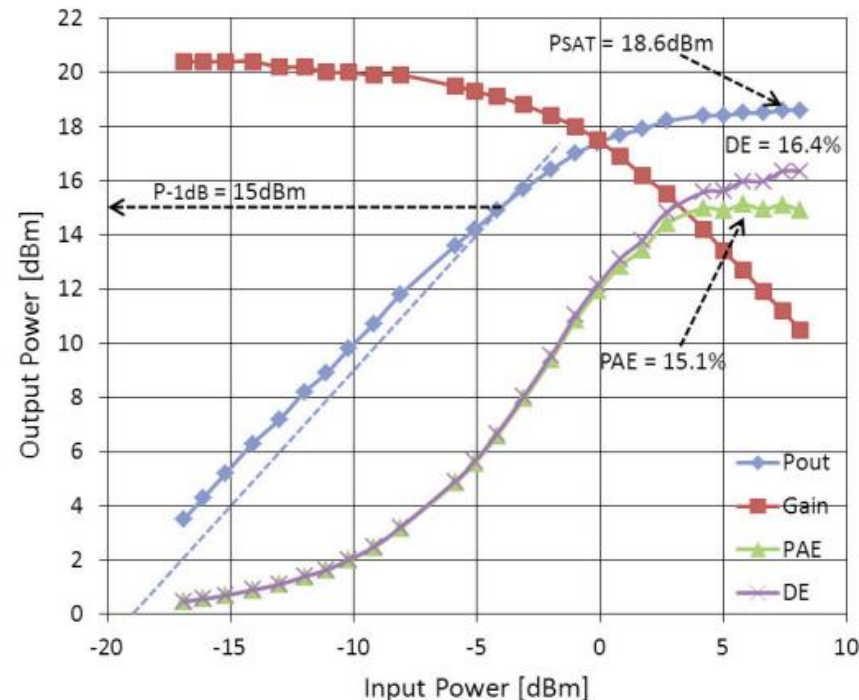





Figure 24.5.4: Measured PA output power, gain, drain efficiency and PAE.

# Thermal Issue in Designs

1.8 GHz magnetic loop

Power dissipation increases temperature

Many high-temperature issues follow

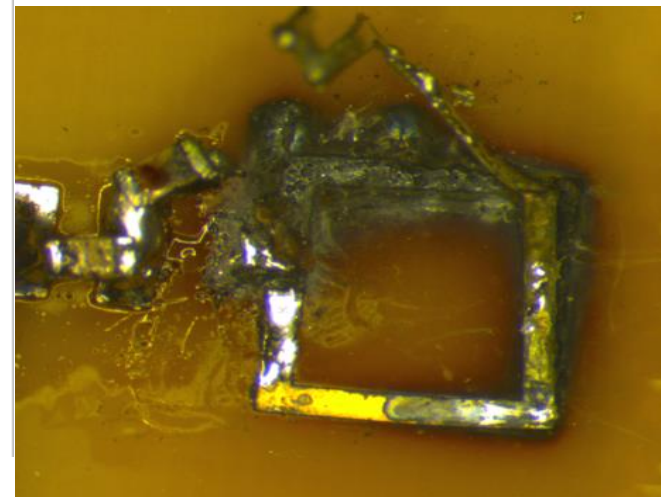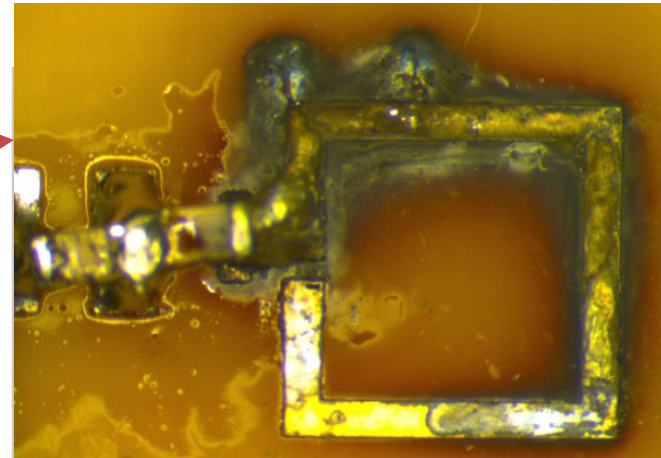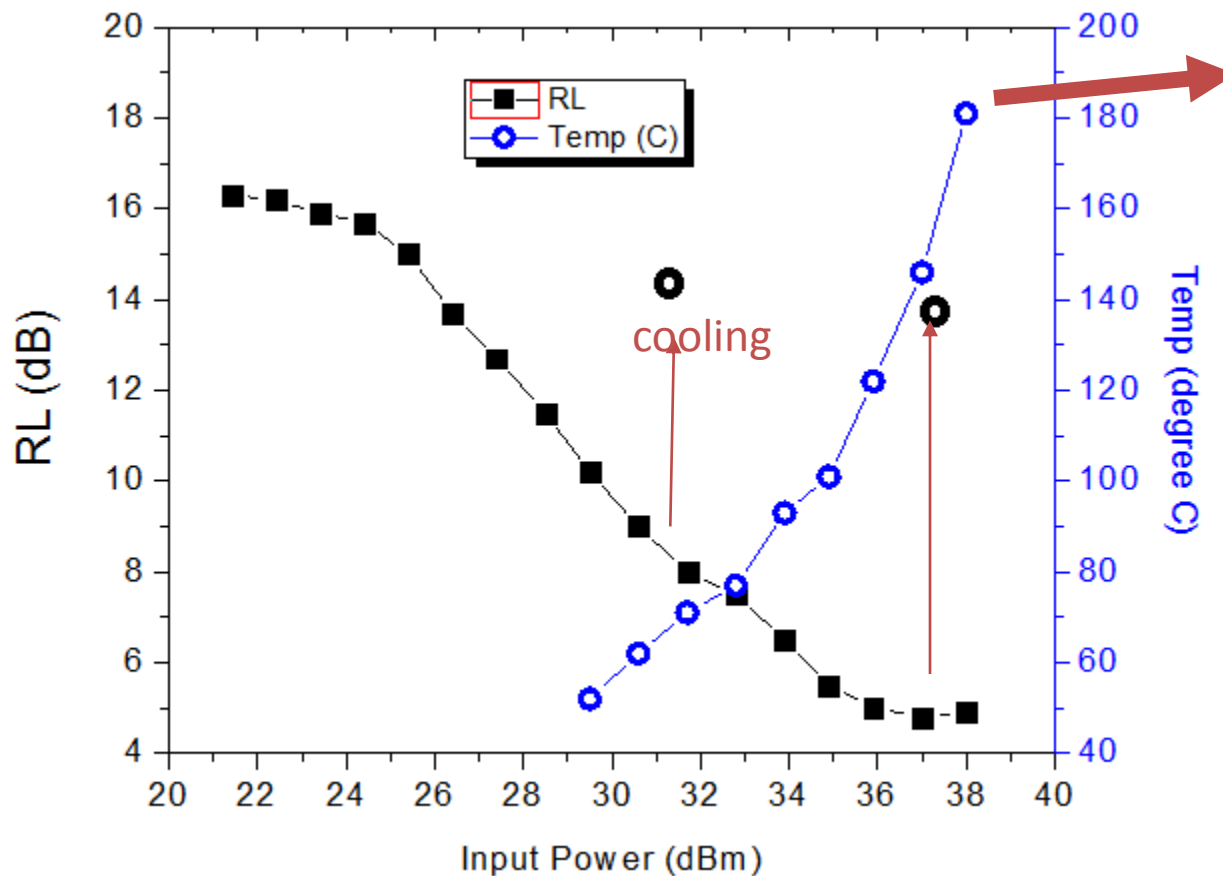

**5 W (37 dBm) is the maximum input power into the PCB**