

Today's Agenda (Oct.4 2017)

Review Homework Problems

- HW#5.2.(f) Single-stage T-line Matching Network
- HW#5.3 Multi-Stage Matching Network

Review Methods to Calculate Transfer Function

- Two-port method
- Feedback factor approximation
- Return ratio method (maybe next time)

Important Concepts on Two-port Stability


Final Remarks on Smith Chart:

Y chart and Z chart must tell the same story

(e.g. Upper plane => **Z** chart tells **X** is positive; **Y** chart tells **B** is negative

(e.g. $R+2j = 1/(G-0.5j) \Rightarrow R = 0$ and $G = 0$

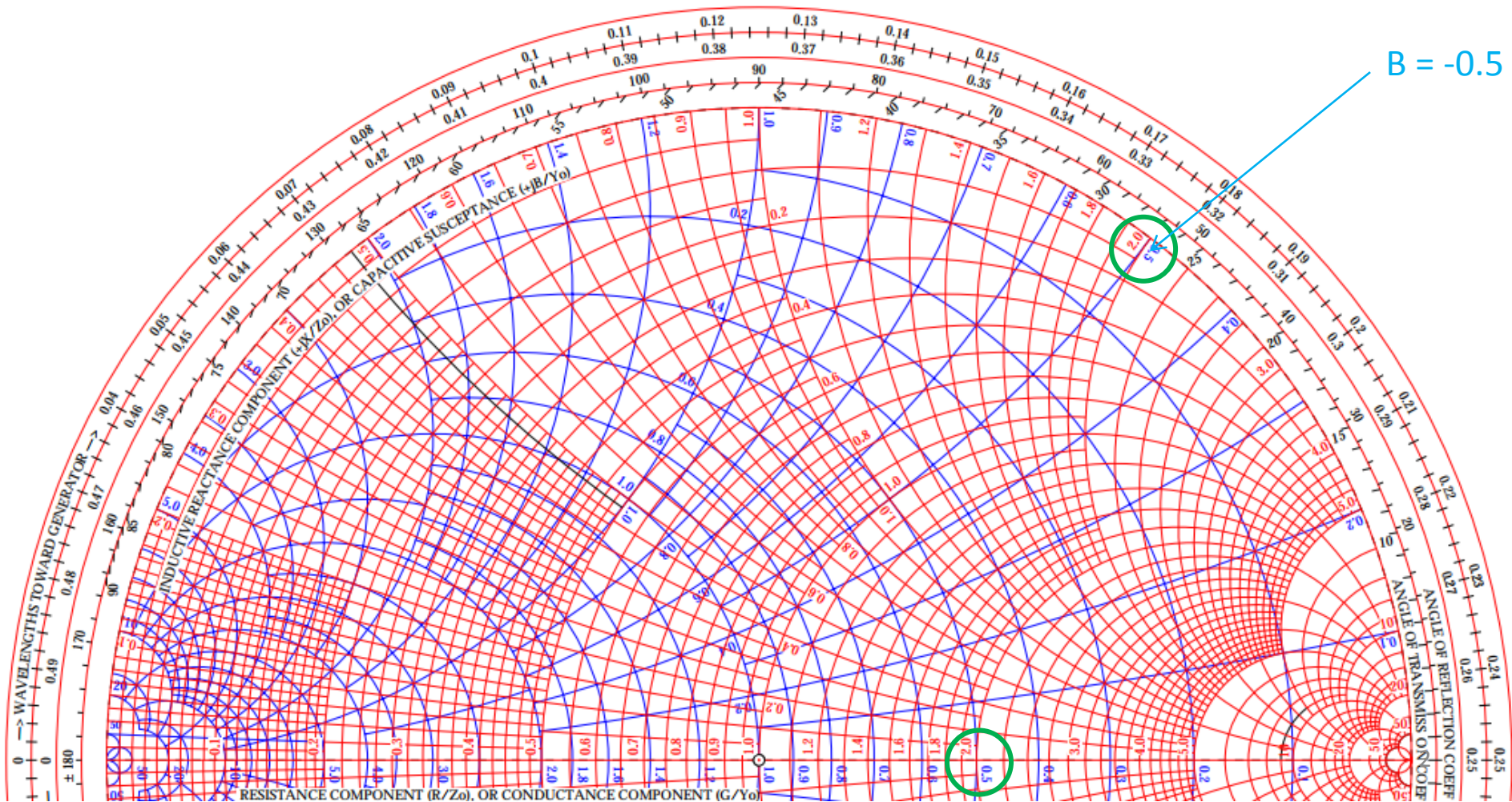
(e.g. $2+Xj = 1/(0.5+Bj) \Rightarrow X = 0$ and $B = 0$



2. For the following problems, you may use the Smith Chart. For lumped component calculations, use equations and compare to the accuracy of using the Smith Chart.

(f) Design a matching network to match 50 ohm to $Z_L = 25 + j90$ ohm using transmission lines.


Series line first

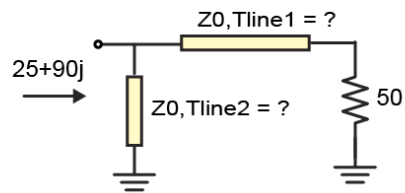


Series $\lambda/4$ T-line with $Z_0 \sim 141\Omega$

Add $B = -0.52 * 0.02 = -0.0104$

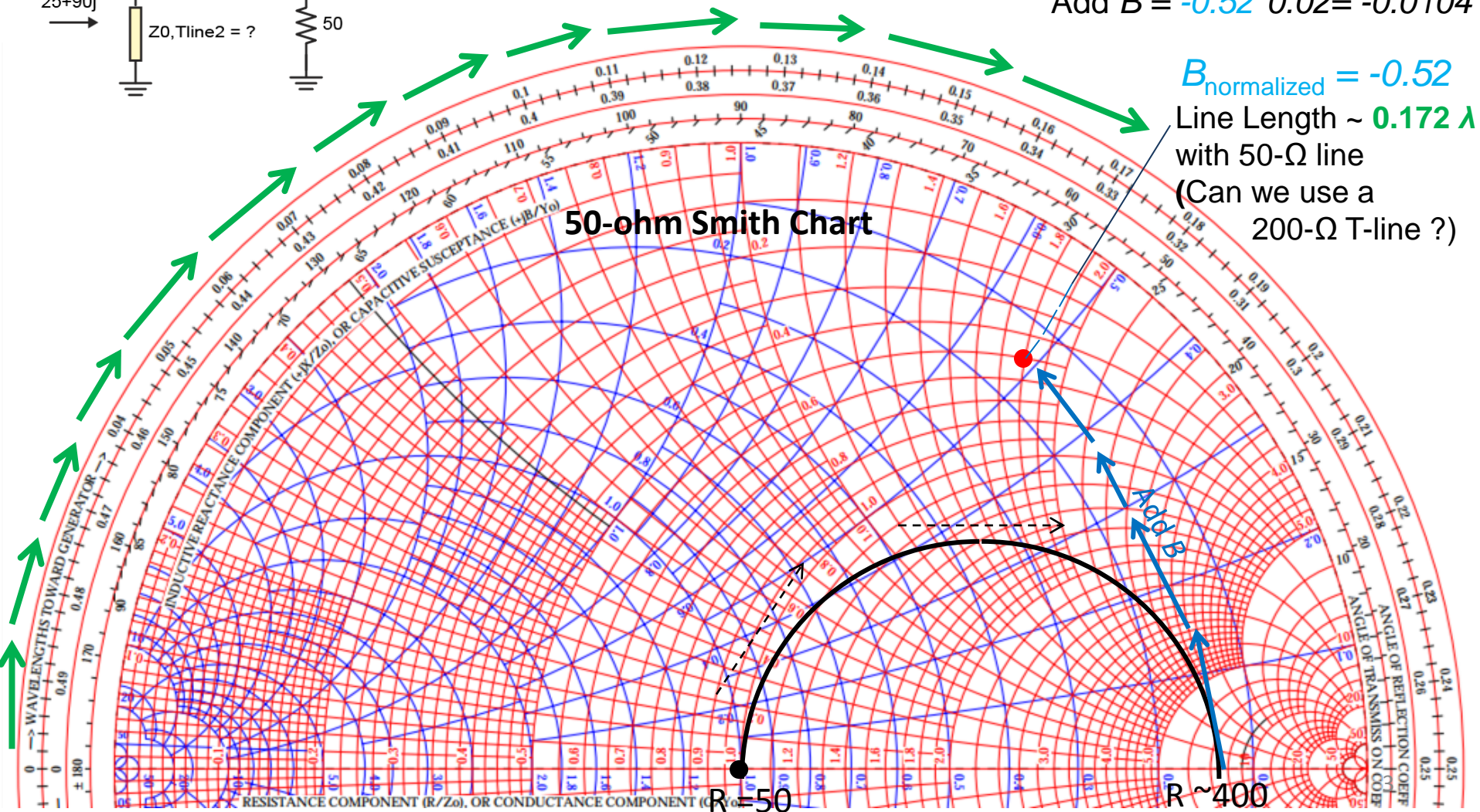$B_{\text{normalized}} = -0.52$
 Line Length $\sim 0.172 \lambda$
 with 50- Ω line
 (Can we use a 200- Ω T-line ?)




Parallel line first

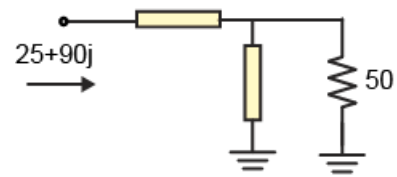

$$B_{\text{normalized}} = -2.5$$

Parallel line length $\sim 0.054 \lambda$
with $50\text{-}\Omega$ line
(can the line be open-circuited ?)




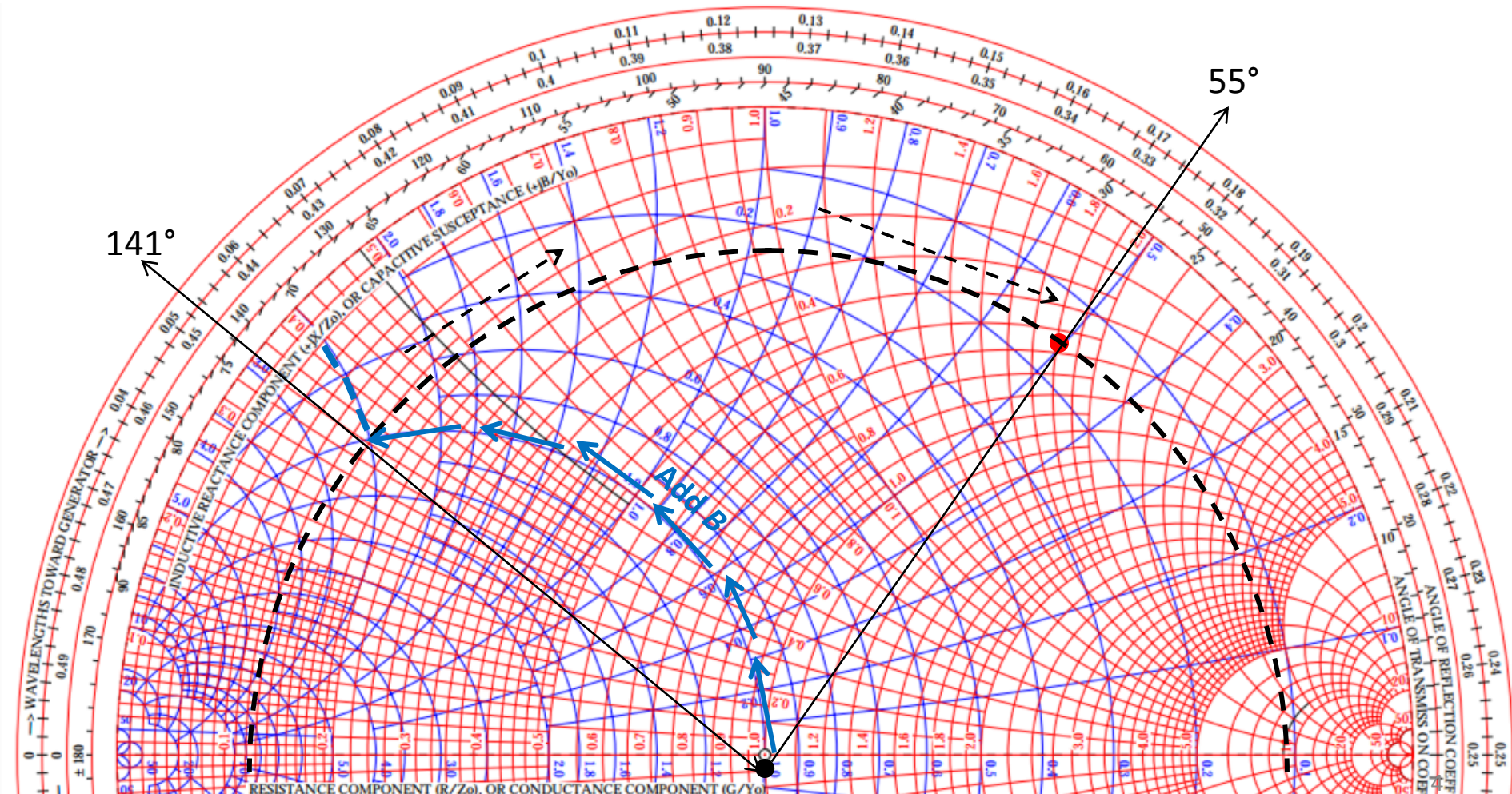
Series line length of
 $(141^\circ - 55^\circ) / 180^\circ * 0.25\lambda \sim 0.12 \lambda$



50-ohm Smith Chart

Have you already noticed the Reciprocity?

If
then

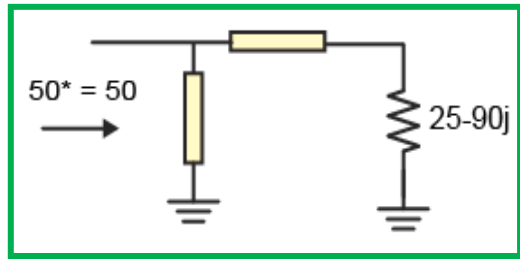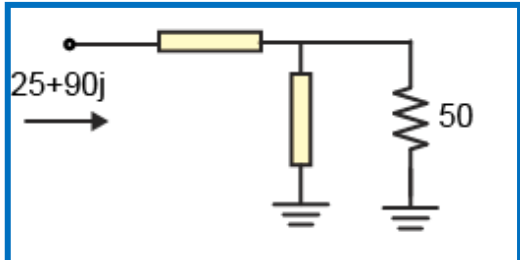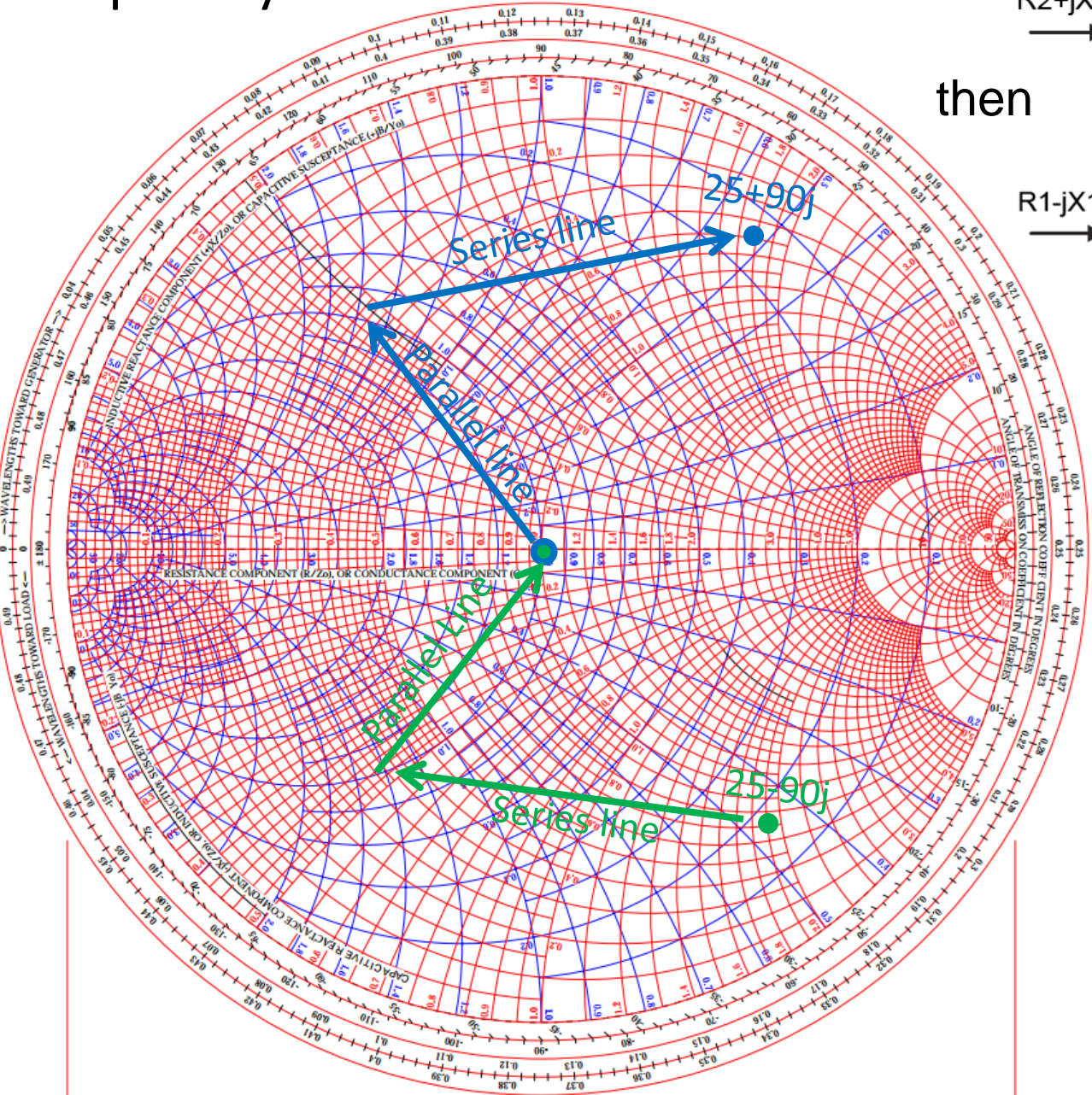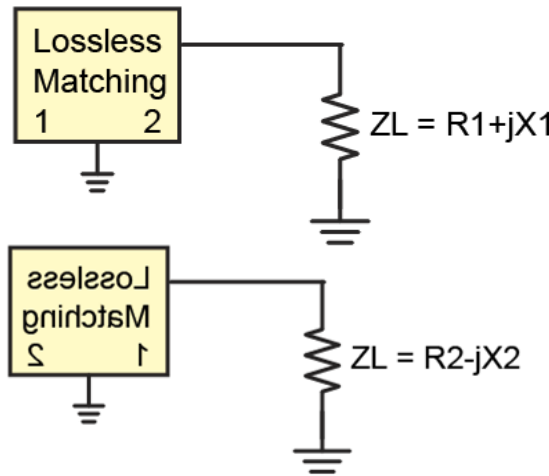

- 3.(a) Design a π matching network between a 1000Ω load impedance and a 50Ω source impedance at 1 GHz. The inductor and capacitor quality factors are 20. The target bandwidth for $|S_{11}| < -10$ dB is 5%. Calculate the insertion loss and verify your design using ADS or Cadence. Check in ADS if the relation $|S_{11}|^2 + |S_{21}|^2 = 1$ holds.

Can a 1-stage matching work? No!





$$m = 1000/50=20; Q = \sqrt{m-1} = 4.4$$

$$\text{Shunt } C: X = 1000/4.4 = 227 \Rightarrow C = 0.7 \text{ pF}$$

$$\text{Series } L: X = 227/(1+1/4.4^2) = 215 \Rightarrow L = 34.2 \text{ nH}$$

$$\text{Parallel } L: X = 1000/4.4 = 227 \Rightarrow L = 36.1 \text{ nH}$$

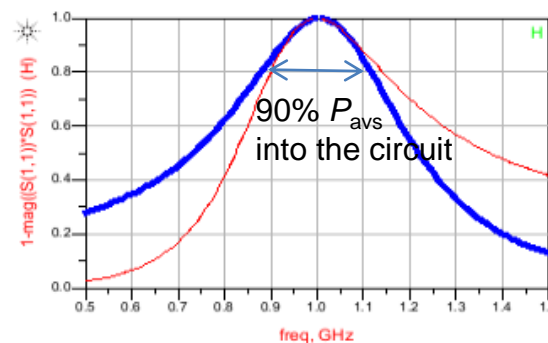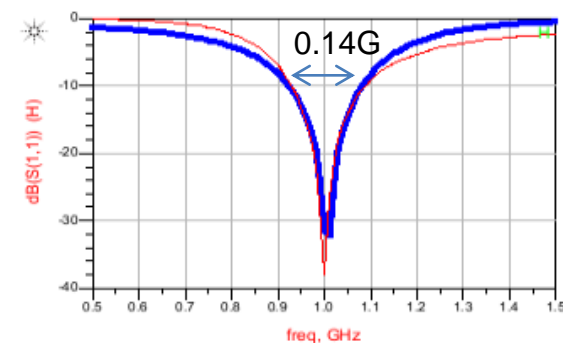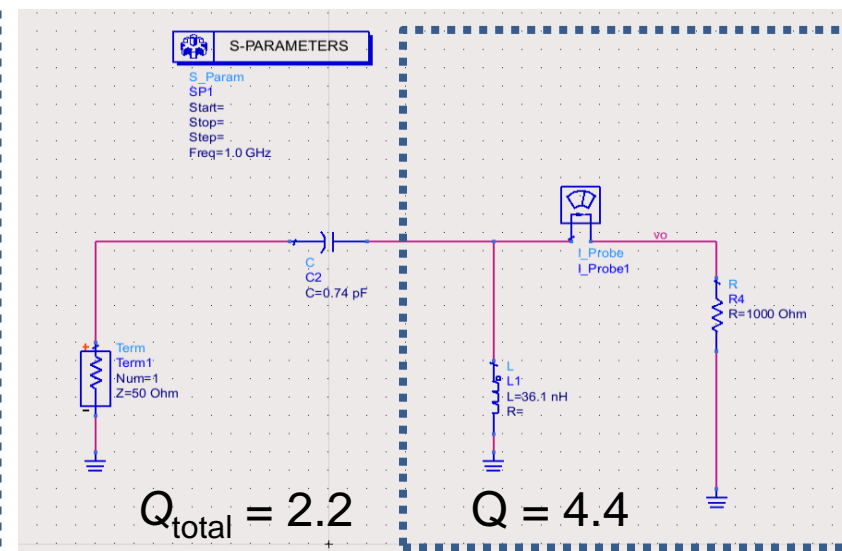
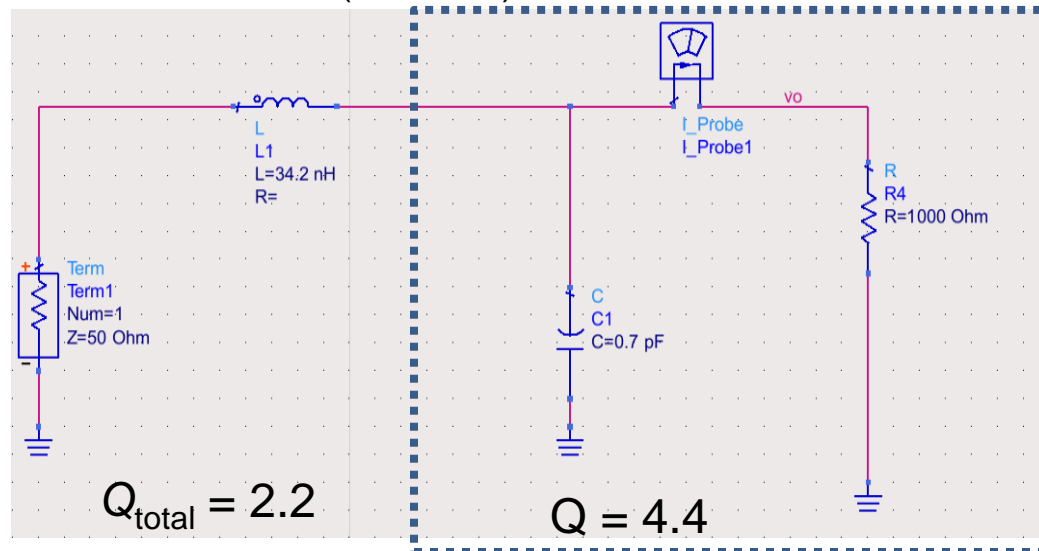
$$\text{Series } C: X = 227/(1+1/4.4^2) = 215 \Rightarrow C = 0.74 \text{ pF}$$





$$|S_{11}| < -10 \text{ dB Bandwidth} = 0.14 \text{ GHz}/1 \text{ GHz} = 0.14 \approx 1/3 Q_{\text{total}}$$

With lossy components: $IL = 1/(1+Q/Q_{cap}+Q/Q_{ind})$

This is the L-matching shown earlier

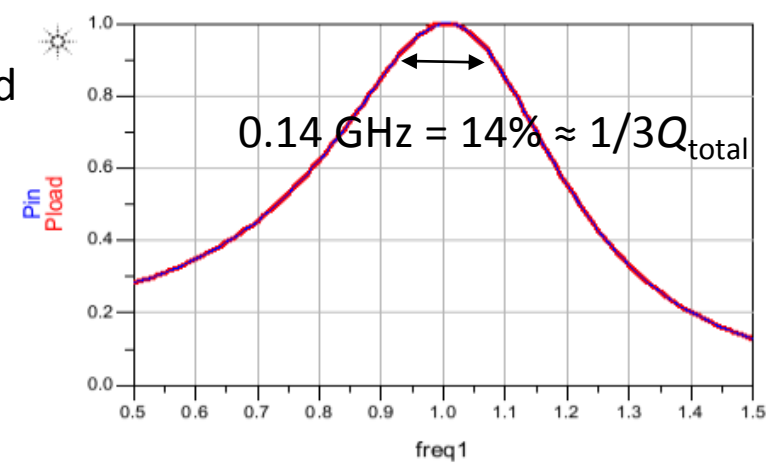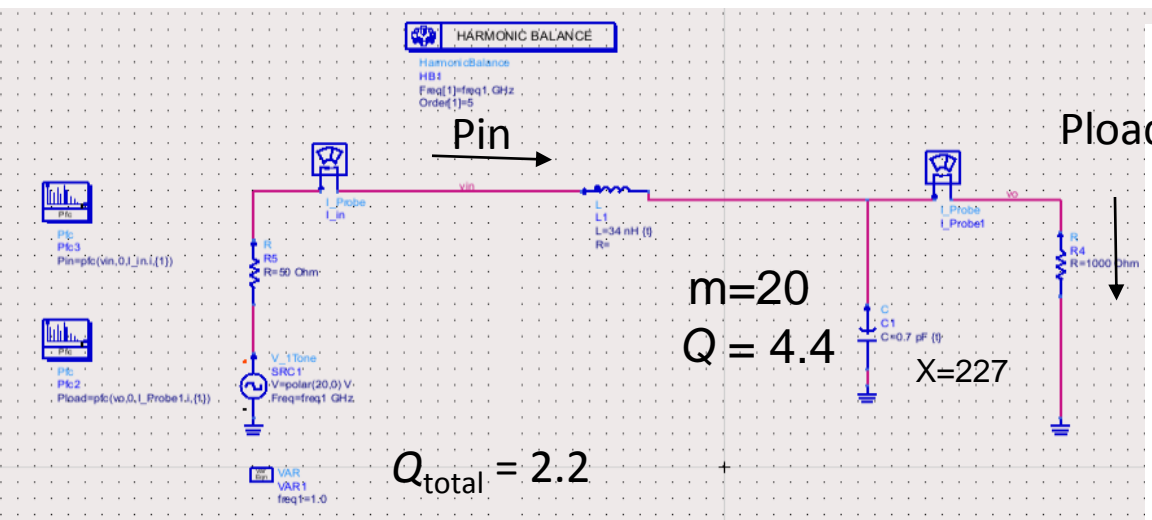


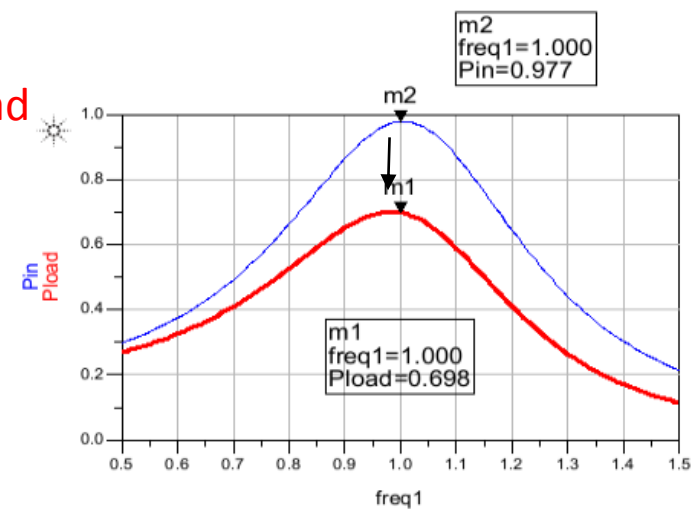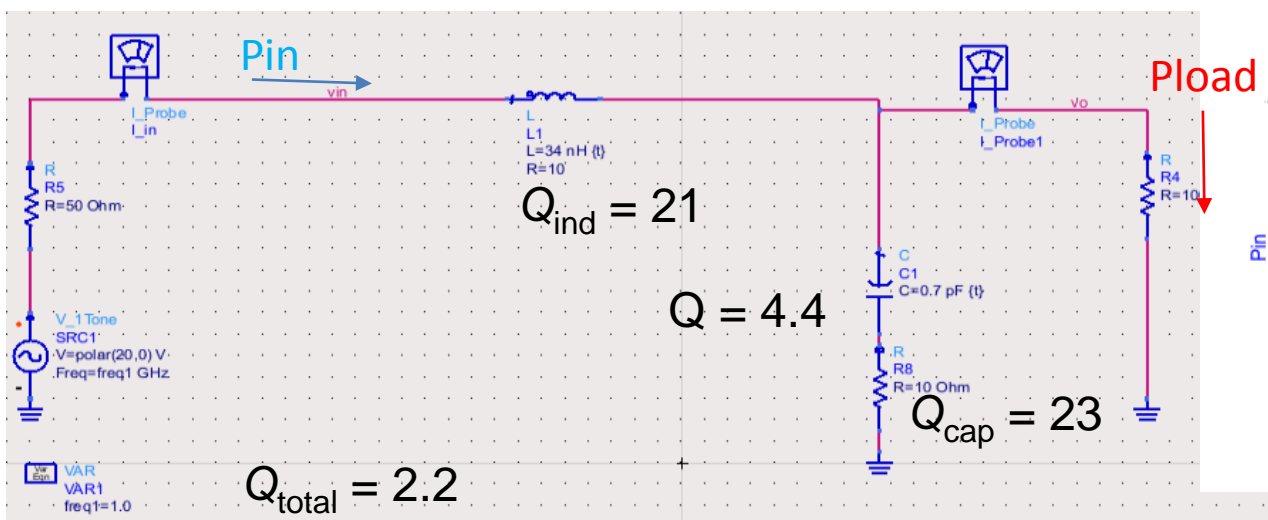Introduce finite-Q inductor and capacitor




$$IL \sim P_{load}/P_{in} = 1/(1+4.4/21+4.4/23) = 0.71$$



Pi-matching

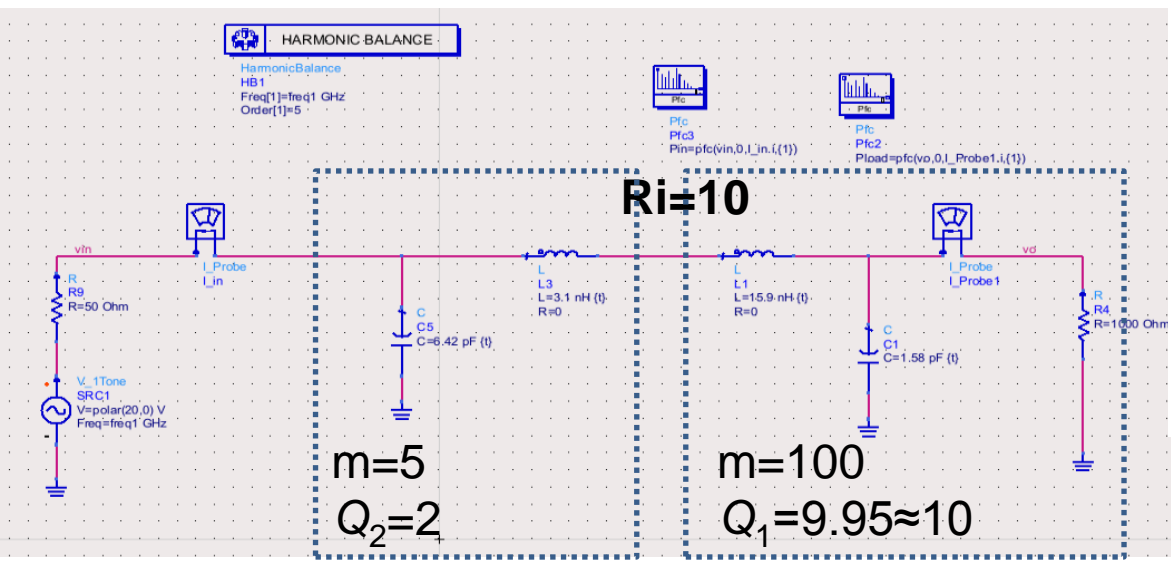

$Q_{total} = (2+10)/2 = 6$

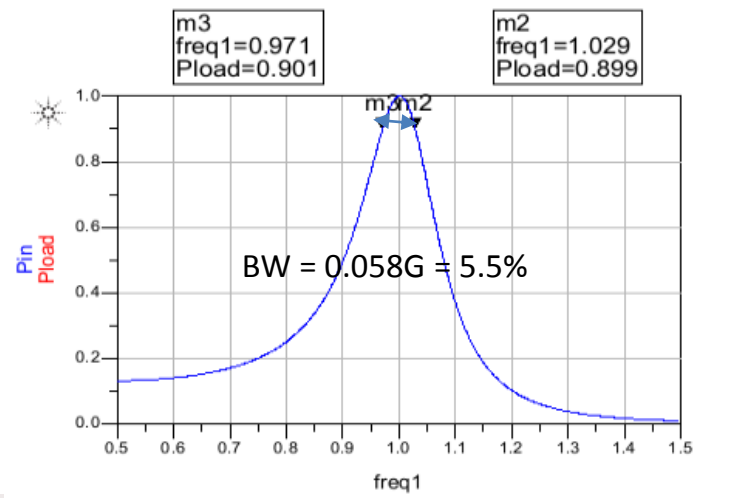


$BW \approx 1/3 Q_{total} = 5.5\%$

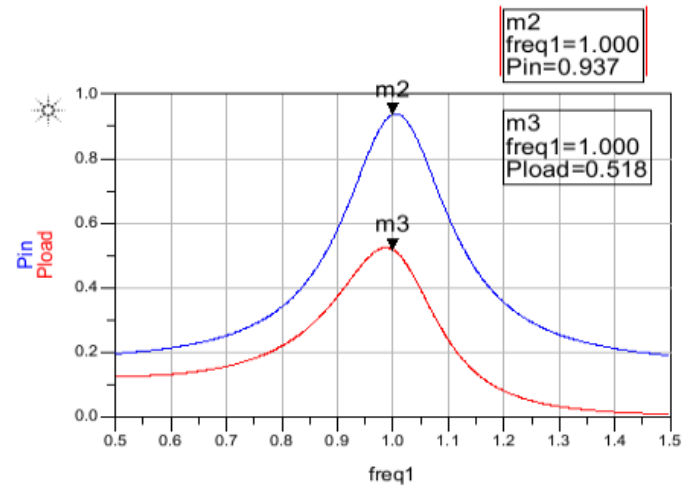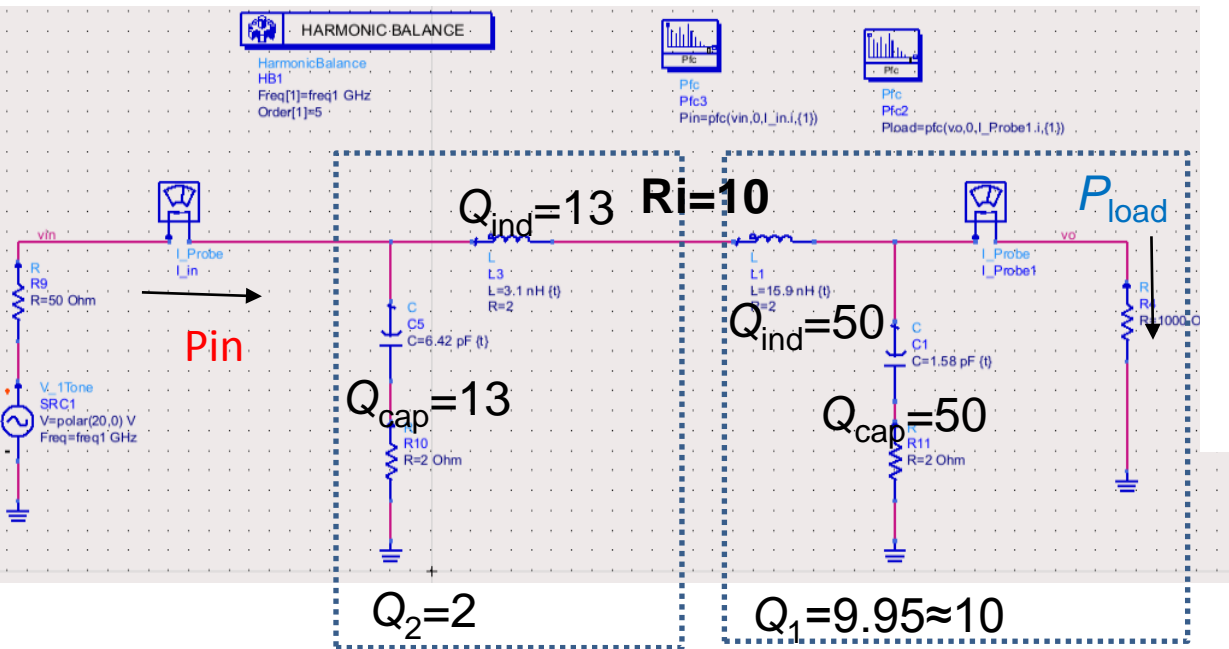

$IL = P_{load}/P_{in}$
 $= 1/(1+10/50+10/50+2/13+2/13)$
 $= 0.59$

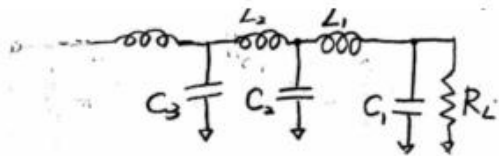- (b) Design a matching network between a 1000Ω load impedance and a 50Ω source impedance at 1 GHz. The inductor and capacitor quality factors are 20. The design goal is to achieve the lowest insertion loss. Calculate the insertion loss and verify your design using ADS or Cadence.




$$IL = \frac{1}{1 + \frac{N}{Q_u} \sqrt{\left(\frac{R_{hi}}{R_{lo}}\right)^2 - 1}}$$

$$Q_u = Q_{cap} \parallel Q_{ind} = 10, \quad R_{hi} = 1000, \quad R_{lo} = 50.$$

$$IL = \frac{1}{1 + \frac{N}{10} \sqrt{20^2 - 1}} \quad \text{When } N=2, \text{ IL reaches the max value.}$$

The matching network should be two-stage.
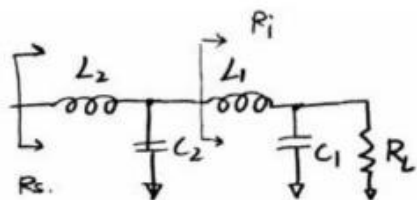
$$Q = \sqrt{\sqrt{20} - 1} = 1.863, \quad IL_{max} = \frac{1}{1 + \frac{2}{10} \sqrt{20 - 1}} = 0.729$$




$$\begin{aligned} X_{p1} &= \frac{R_L}{Q} \\ X_{s1} &= \frac{X_{p1}}{1 + Q^2} \end{aligned} \quad \left\{ \begin{array}{l} C_1 = 296 \text{ fF} \\ L_1 = 66.4 \text{ nH} \end{array} \right.$$

$$\begin{aligned} X_{p2} &= \frac{R_i}{Q} \\ X_{s2} &= \frac{X_{p2}}{1 + Q^2} \end{aligned} \quad \left\{ \begin{array}{l} C_2 = 1.32 \text{ pF} \\ L_2 = 14.8 \text{ nH} \end{array} \right.$$

Designs are verified in ADS.
(see attachments)

$$\text{Eqn } il = P_{fc2} / P_{fc1}$$

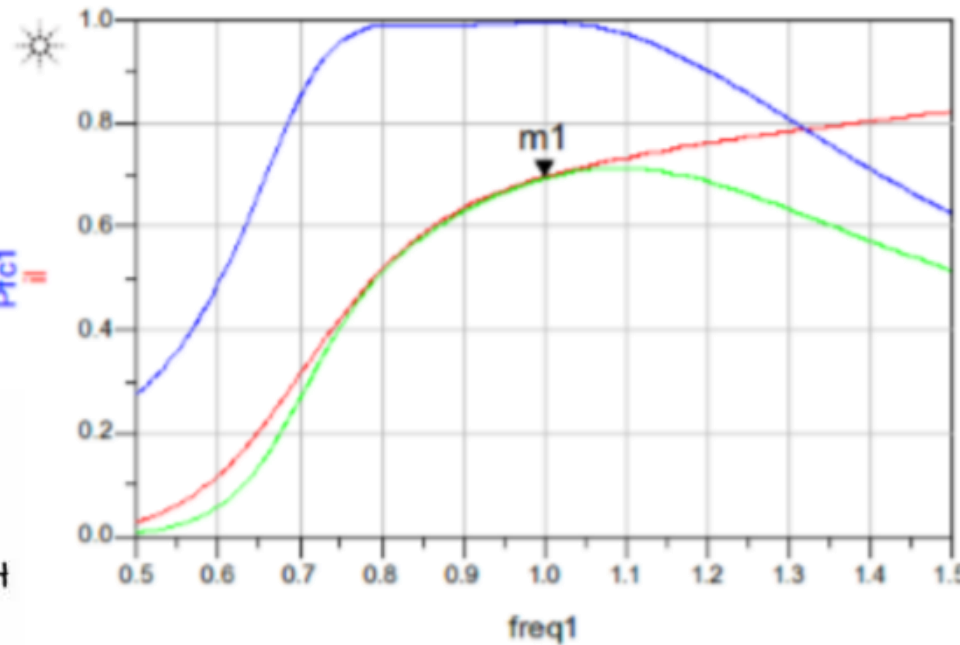
$$\begin{aligned} m1 \\ \text{freq1} &= 1.000 \\ il &= 0.697 \end{aligned}$$




Review methods to calculate circuit close-loop transfer function

- KCL
- Two-port method
- Feedback factor approximation
- Return ratio method (maybe next time)


Calculate V_o/V_i

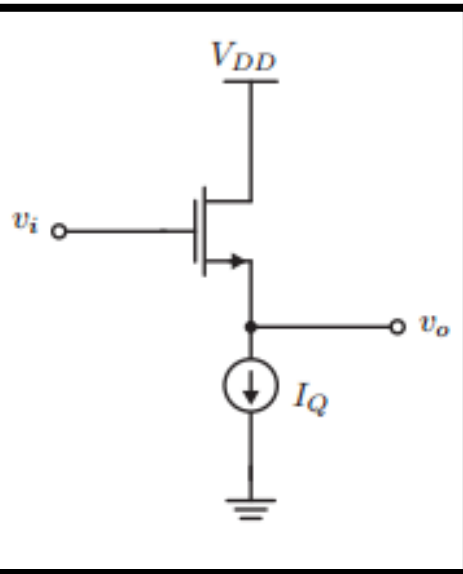

Draw the small-signal schematic

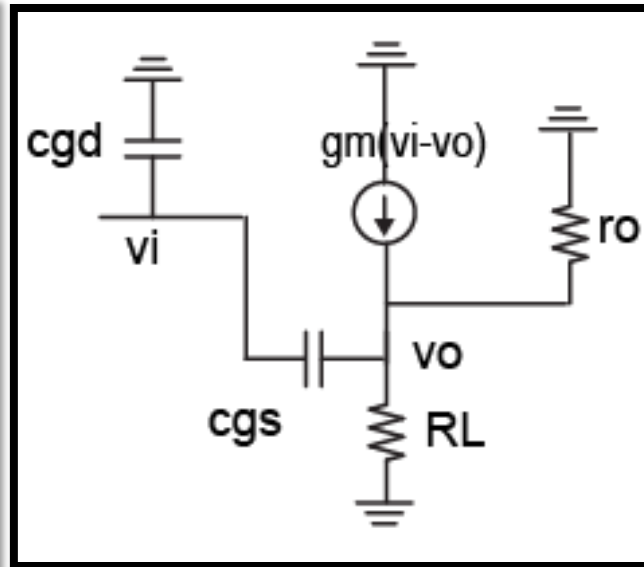


Use some imagination

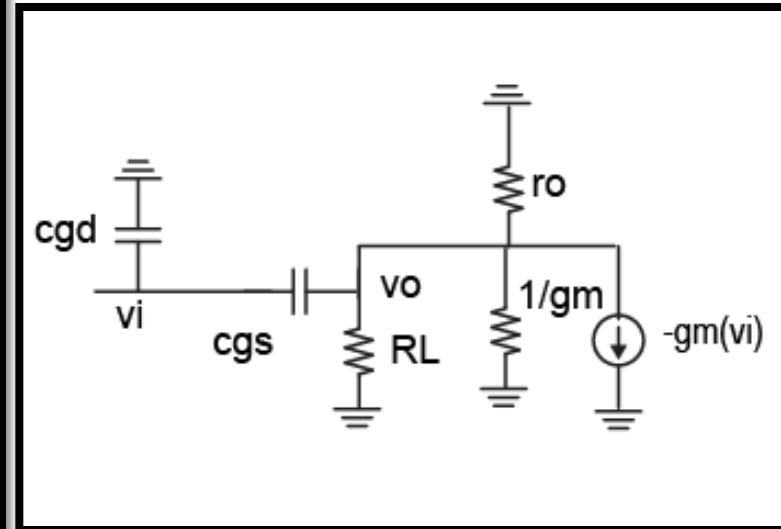

- You can always apply KCL to solve V_o/V_i
- It looks appropriate to describe the circuit with two-port Y matrix!

Two-port Method: Y-Matrix Approach

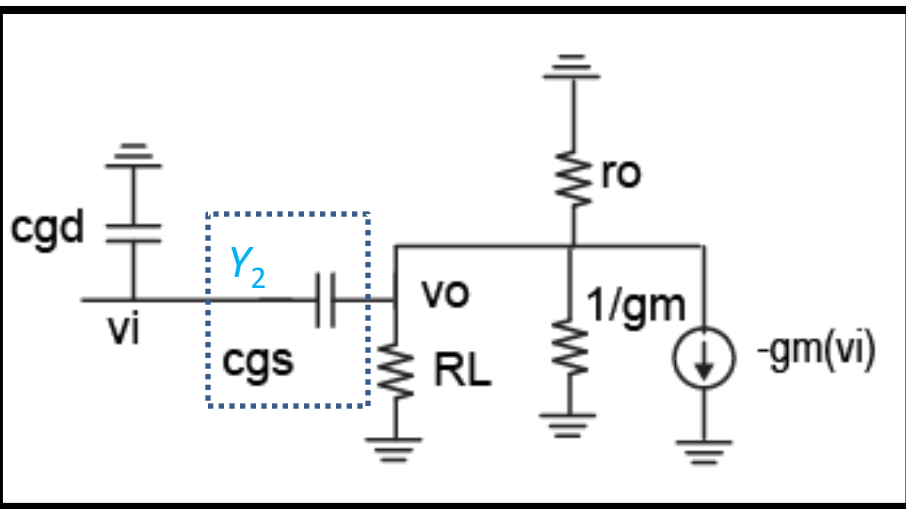


$$Y_1 = \begin{bmatrix} j\omega C_{gd} & 0 \\ -g_m & g_m + (1/R_L) + (1/r_o) \end{bmatrix}$$

$$Y_2 = \begin{bmatrix} j\omega C_{gs} & -j\omega C_{gs} \\ -j\omega C_{gs} & j\omega C_{gs} \end{bmatrix}$$

$$Y = \begin{bmatrix} j\omega C_{gd} + j\omega C_{gs} & -j\omega C_{gs} \\ -g_m - j\omega C_{gs} & g_m + (1/R_L) + (1/r_o) + j\omega C_{gs} \end{bmatrix}$$

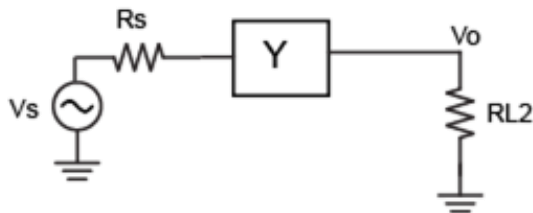Can you get the G,H or Z matrix easier than Y Matrix?




$$\frac{V_o}{V_s} = \frac{-Y_{21} * Y_s}{(Y_s + Y_{11})(Y_{L2} + Y_{22}) - Y_{12}Y_{21}}$$

Substitute $Y_s = \infty$, $Y_L = 0$, and Y-parameters into the formula
 $\Rightarrow V_o/V_s = -Y_{21}/Y_{22} = (g_m + j\omega C_{gs}) / (g_m + 1/R_L + 1/r_o + j\omega C_{gs})$



Feedback Factor Method:

Approximation introduced in many textbooks (e.g., Smith, G&M, Ravazi)

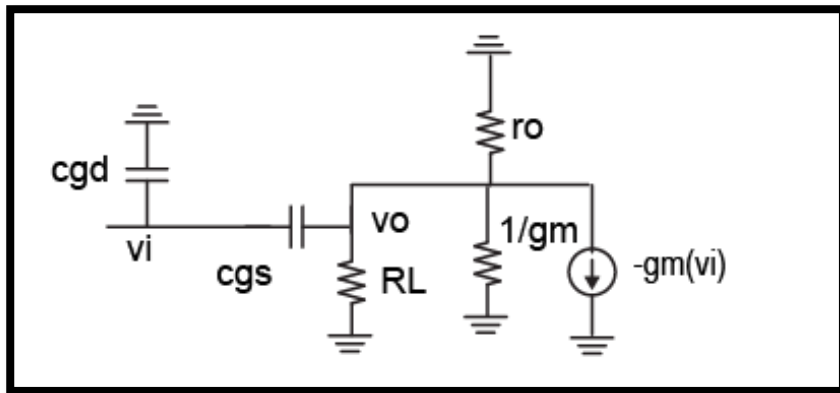- (1) Distinguish the circuit as a shunt-shunt feedback (2) It is a current-voltage amp



- (3) Open loop gain calculation

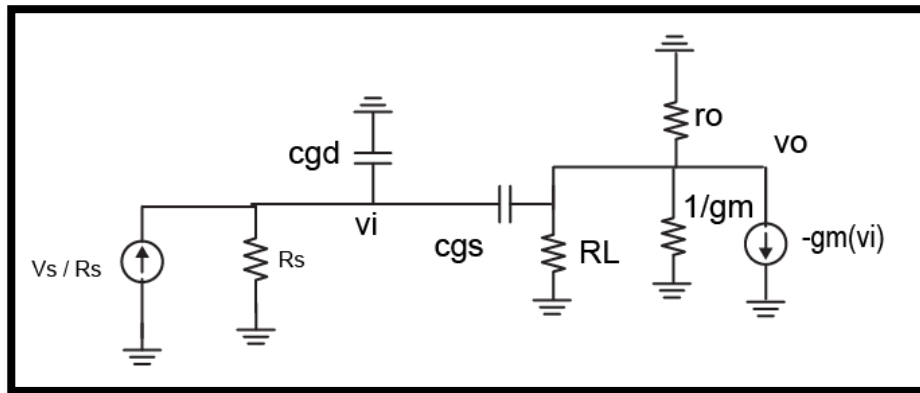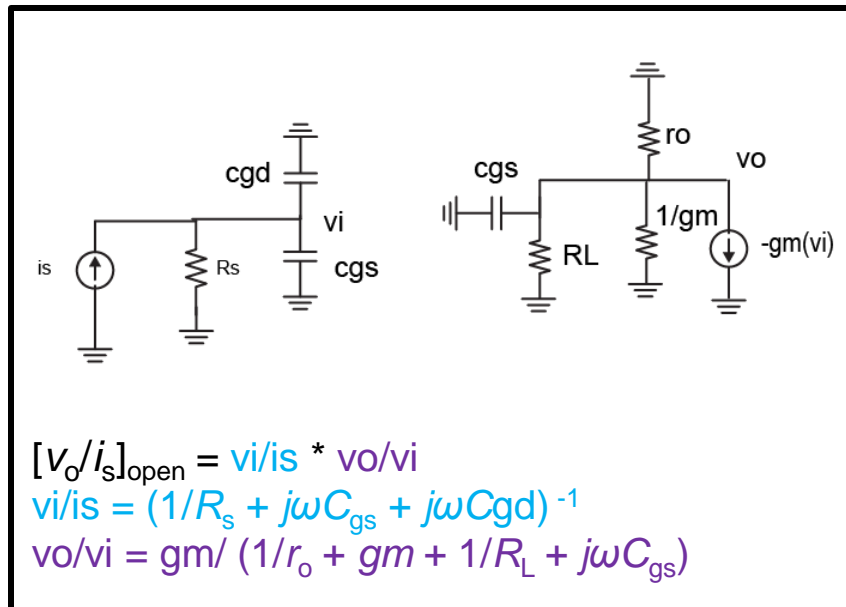

- (4) Close-loop gain calculation

Feedback factor = $j\omega C_{gs}$

$$[v_o/i_s]_{\text{close}} = [v_o/i_s]_{\text{open}} / \{1 + j\omega C_{gs} [v_o/i_s]_{\text{open}}\}$$



$$v_s = i_s R_s$$

$$[v_o/v_s]_{\text{close}} = 1/R_s * [v_o/i_s]_{\text{open}} / \{1 + j\omega C_{gs} [v_o/i_s]_{\text{open}}\}$$



$$R_s = 0$$

$$[v_o/v_s]_{\text{close}} = g_m / (g_m + 1/R_L + 1/r_o + j\omega C_{gs})$$

Comparison (1/2)


True (2-port approach)

$$v_o/v_s = (gm + j\omega C_{gs}) / (gm + 1/R_L + 1/r_o + j\omega C_{gs})$$

Approximated (feedback factor approach)

$$v_o/v_s = gm / (gm + 1/R_L + 1/r_o + j\omega C_{gs})$$

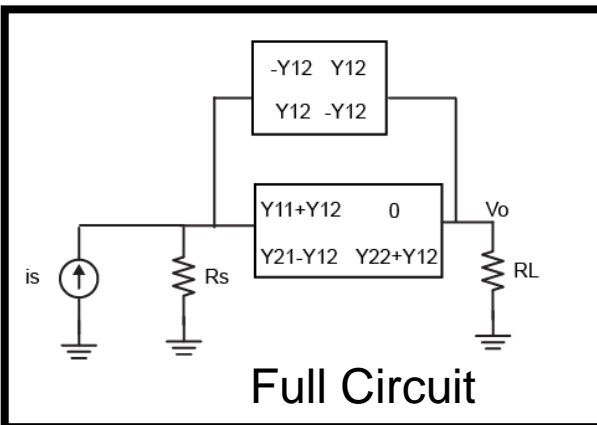- The two methods do not match
- Use the feedback factor approach on a Y -matrix to see what is neglected (no loss of generality)



$$[v_o/i_s]_{\text{open}} = -(Y_{21} - Y_{12}) / [(Y_s + Y_{11})(Y_{22} + Y_L)]$$

Close-loop gain calculation

$$\text{Feedback factor} = -Y_{12}$$


$$[v_o/i_s]_{\text{close}} = [v_o/i_s]_{\text{open}} / \{1 + -Y_{12}[v_o/i_s]_{\text{open}}\}$$

$$\downarrow \quad v_s = i_s R_s$$

$$[v_o/v_s]_{\text{close}} = 1/R_s * [v_o/i_s]_{\text{open}} / \{1 + -Y_{12}[v_o/i_s]_{\text{open}}\}$$

$$\downarrow \quad R_s = 0$$
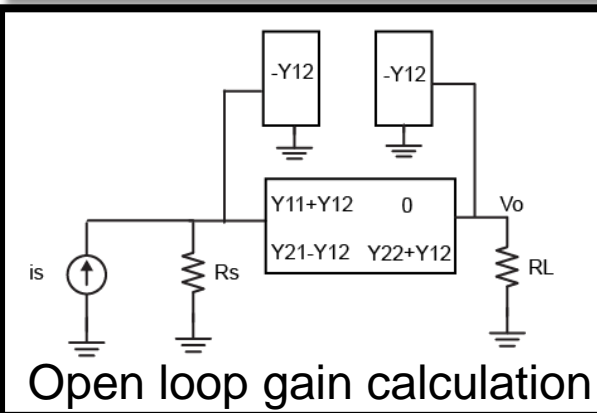
$$[v_o/v_s]_{\text{close}} = -Y_s(Y_{21} - Y_{12}) / [(Y_s + Y_{11})(Y_L + Y_{22}) + Y_{12}(Y_{21} - Y_{12})]$$



Comparison (2/2)

True

$$\frac{V_o}{V_s} = \frac{-Y_{21} * Y_s}{(Y_s + Y_{11})(Y_L + Y_{22}) - Y_{12}Y_{21}}$$

Approximated

$$v_o/v_s = -Y_s(Y_{21} - Y_{12}) / [(Y_s + Y_{11})(Y_L + Y_{22}) + Y_{12}(Y_{21} - Y_{12})]$$

In the approximation (feedback factor approach), we replace Y_{21} by $Y_{21} - Y_{12}$, which is usually acceptable

Similarly, applying feedback factor approach to a series-series feedback assumes $Z_{21} - Z_{12} \sim Z_{21}$

Important Concept on Two-port Stability

- The two-port network is unstable if it supports non-zero currents/voltages with passive terminations

$$\begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{pmatrix} \begin{pmatrix} v_1 \\ v_2 \end{pmatrix}$$

- Since $i_1 = -v_1 Y_S$ and $i_2 = -v_2 Y_L$

$$\begin{pmatrix} y_{11} + Y_S & y_{12} \\ y_{21} & y_{22} + Y_L \end{pmatrix} \begin{pmatrix} v_1 \\ v_2 \end{pmatrix} = 0$$

- The only way to have a non-trivial solution is for the determinant of the matrix to be zero at a particular frequency



$$Y_S + Y_{in} = 0$$

- Or equivalently

$$Y_L + Y_{out} = 0$$

Or equivalently,
a system pole is on the imaginary axis
(not stable and could oscillate)

Two-port Unconditionally Stable

For all passive Y_L and Y_S

$$\Re(Y_{in}) = \Re\left(y_{11} - \frac{y_{12}y_{21}}{Y_L + y_{22}}\right) > 0$$

$$\Re(Y_{out}) = \Re\left(y_{22} - \frac{y_{12}y_{21}}{Y_S + y_{11}}\right) > 0$$


Impossible to be unstable

In RF circuits, we usually only control the impedances (e.g. Y_L) at the in-band frequency


Important Concept on Two-port Stability

If a passive (Y_L , Y_S) creates $\text{Re}(Y_S + Y_{IN}) < 0$, is this circuit stable?

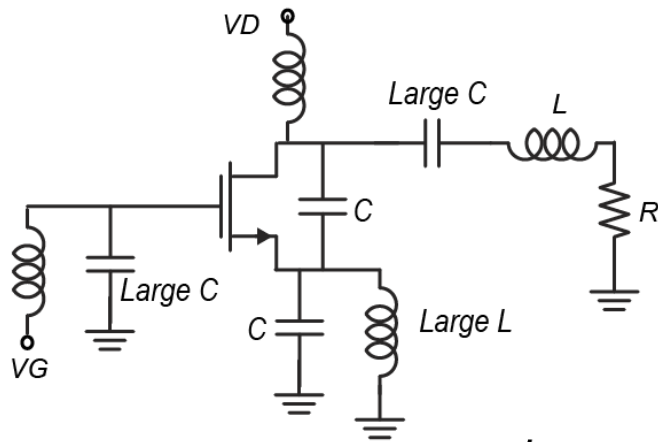
"I don't know" because I do not know the system pole locations according to the give condition



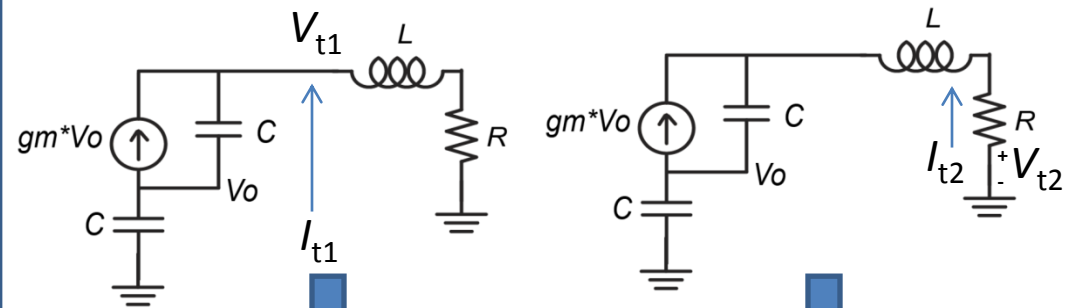System Pole = pole of V_{t1}/I_{t1} or pole of I_{t2}/V_{t2}



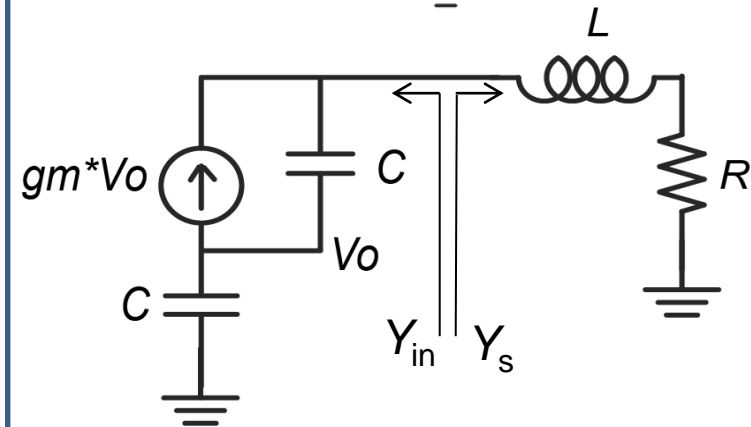System Pole at roots of
 $s^3LC^2 + s^2RC^2 + s2C + gm = 0$



$$Y_{in} = s^2C^2/(2sC + gm); Y_s = 1/(R+sL)$$

$g_m = 0.01$

$L = 1\text{e-}9$

$C = 1\text{e-}12$

$R = 5$

Three system poles at:

$1.0\text{e+}10^*$
 $-2\text{e-}16 + 4.4721i$
 $-2\text{e-}16 - 4.4721i$
 -0.5000

Still stable

