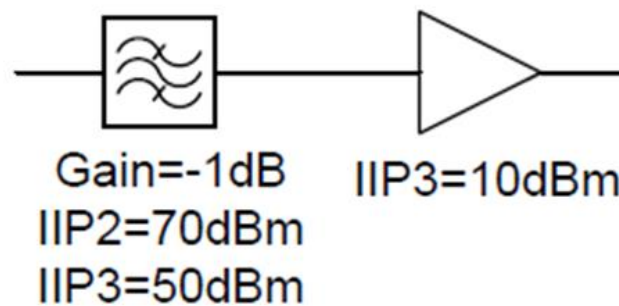



Problem Set 8
Submit through bCourses

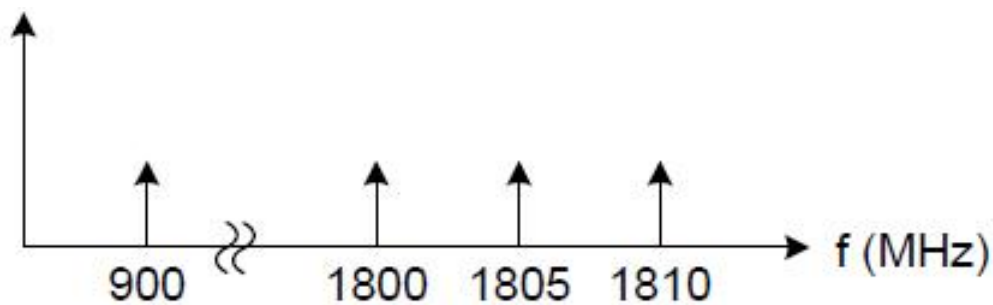1. System Analysis

A wireless receiver front-end is shown below:




We would like to receive the channel at 1800MHz, while we have additional channels at 900MHz, 1805MHz and 1810MHz:




The minimum detectable signal at 1800MHz is -100dBm. The required signal to distortion ratio at the front-end output is 9dB.

- If the signal power at the 1810MHz channel is -33dBm, what is the maximum allowed power at the 1805MHz channel?
- What is the required spec for the amplifier IIP2 if the signal power at the 900MHz channel can be as high as -30dBm?

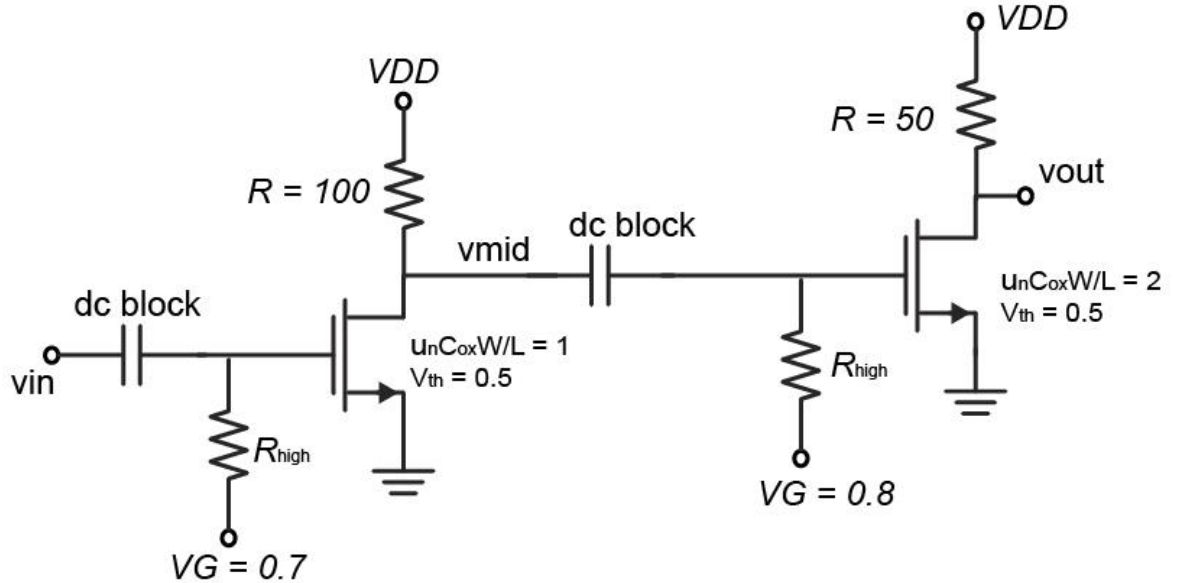2. In this problem you will do distortion analysis for a frequency-independent amplifier.



- For the above amplifier, derive a power series to express the small-signal output voltage (v_{out}) as a function of the small-signal input voltage (v_{in}). Assume the transistors are long-channel devices.
 - Calculate IIP3 for the first stage (v_{in} to v_{mid}), the second stage (v_{mid} to v_{out}), and the overall cascade two-stage amplifier.
 - Find IIP2 for the first stage, the second stage, and the cascade two-stage amplifier.
 - Apply the cascade IIP3 and IIP2 formula introduced in the lecture. Explain if the results are different from that obtained via your analysis in part(b) and (c).
 - Calculate HD2 and HD3 of this two-stage amplifier?
 - Use Harmonic-balance in ADS or SpectreRF to simulation IIP2, IIP3, HD2, and HD3 of this two-stage amplifier.
3. To achieve a higher output voltage swing, the two load resistors in the previous problem are replaced by two LC-tanks, as illustrated in the below figure. Now you will do distortion analysis for a tuned amplifier. Keep in mind that in the passband of the amplifier (resonance), the memoryless assumption is valid.

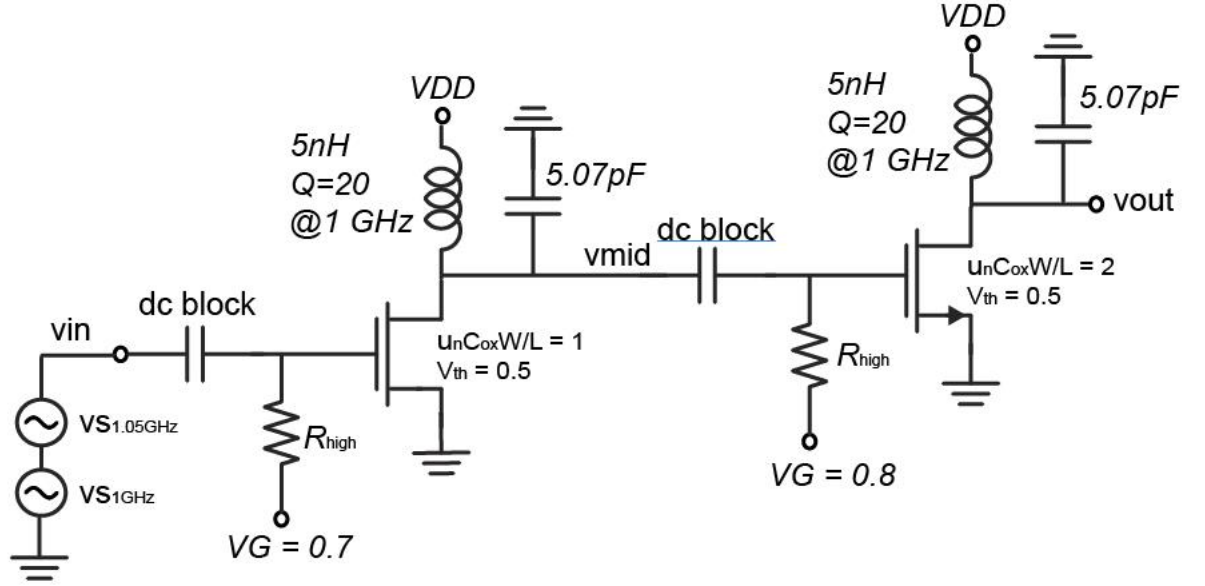

- Under a two-tone excitation at 1.0 and 1.05 GHz with $vs_{1.0GHz} = vs_{1.05GHz} = 1$ mV (zero-to-peak voltage), estimate via hand calculation the voltage components at 0.05, 0.95, 1, 1.05, 1.10, 2.0, and 3.0 GHz, at both v_{mid} and v_{out} .
- Redo part(a) with $vs_{1.0GHz}$ reduced from 1 mV to 0.1 mV.
- What are the IIP3 and IIP2 of this two-stage amplifier (under this two-tone excitation at 1.0 and 1.05 GHz)? Notice that the upper-band IIP3 and IIP2 are no longer the same to the lower-band IIP3 and IIP2, respectively.
- Again, use ADS Harmonic-balance simulation to verify your calculated results.